



Another EMC resource  
from EMC Standards

Join us for an Exclusive Workshop

*Helping you solve your EMC problems*

# GaN/SiC Transistors— Fight or Flight?

Getting EMC ready for the next generation of power electronics devices



# About Us

---




Dr. Yegi Bonyadi currently works as Electronics Team Leader at Lyra Electronics Ltd (<https://www.lyraelectronics.com>), where she focuses on the design of automotive high-power DC-DC converters, on-board chargers and cost-effective EMC design. Her interests include power converter design, automotive power inverters, Hybrid/electric vehicles, power electronics modelling, and Wide-Bandgap semiconductor power devices.



Dr. Min Zhang is the founder and principal EMC consultant of Mach One Design Ltd ([www.mach1design.co.uk](http://www.mach1design.co.uk)), a UK-based engineering firm that specializes in EMC consulting, troubleshooting, and training. His in-depth knowledge of power electronics, digital electronics, electric machines, and product design has benefitted companies worldwide. Zhang can be reached at [info@mach1design.co.uk](mailto:info@mach1design.co.uk)

# Outline of the Workshop

---

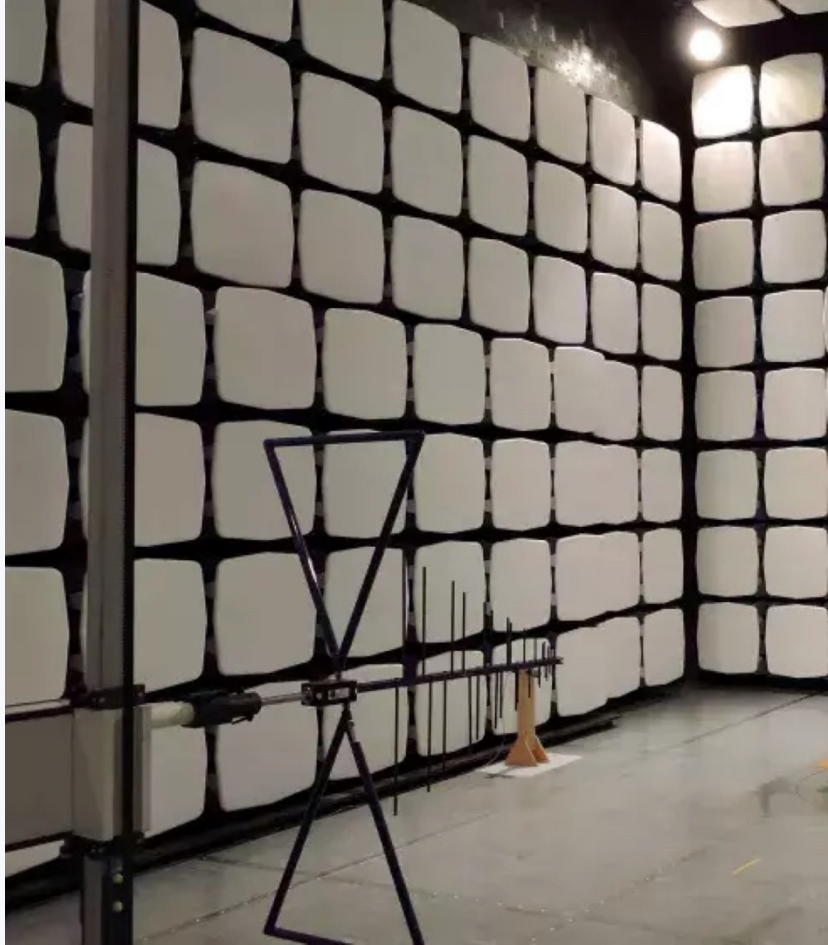

- EMI Challenges Unveiled
- Demystifying EMC Part 1: Finding Your “Ground”
- Demystifying EMC Part 2: Paritics & Coupling
- Effective EMC Testing Part 1: The Benchttop Approach
- Effective EMC Testing Part 2: The Chamber Approach
- Design Strategies for Achieving EMC Compliance
- A case study
- Q & A Session

# GaN & SiC Transistors – Typical Applications



GaN Charger 108W, Belkin, Source: Apple.com

- Mobile phone/Laptop chargers
- Home appliance motor drive applications
- Wireless charging for phones/laptops
- LIDARs
- RF Amplifiers



Lyra's 22kW SiC Bi-directional On-board Charger



- Industrial/EV motor drive applications
- Solar inverters
- High power & high-temperature applications
- RF and microwave applications (typically, Military applications)

# New Challenges

Overshoot voltage depends on the design



$V_{BAT}$ , typically 400V-800V

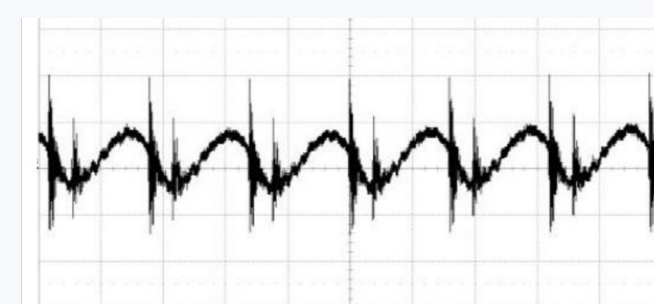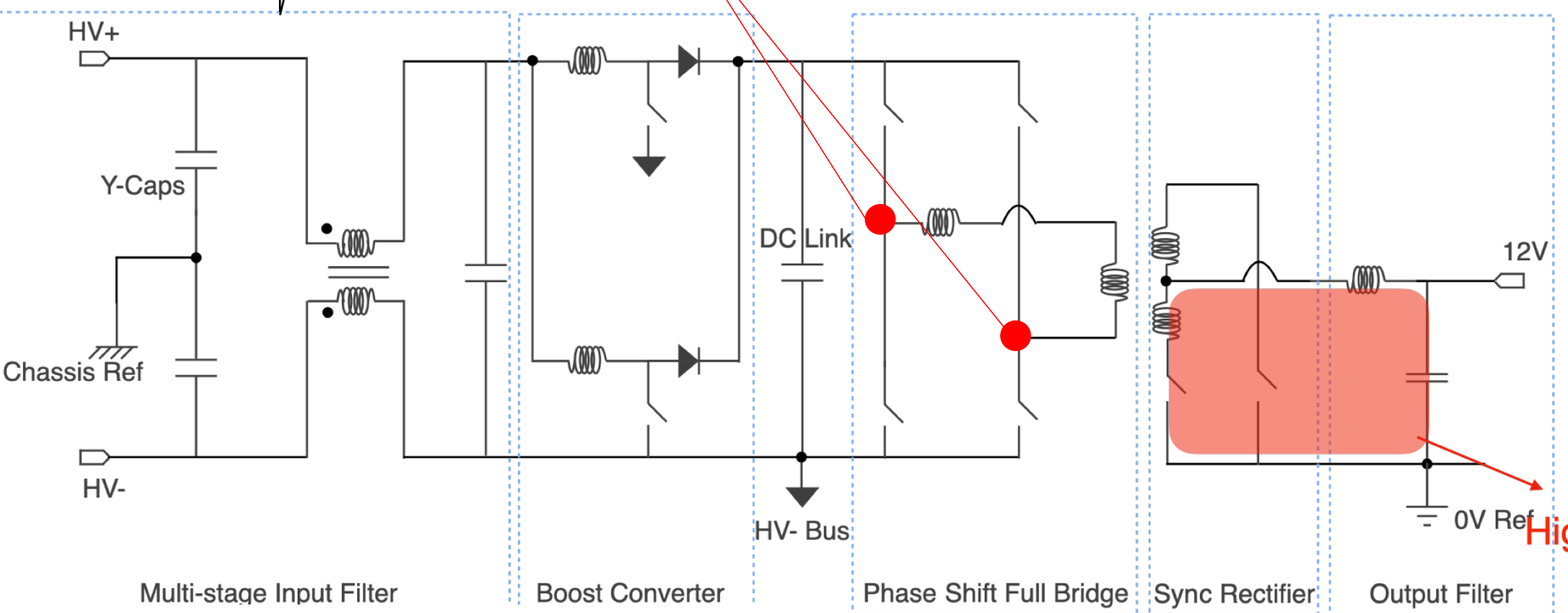- High  $dV/dt$  noise, for example, motor drives, DC-DCs, and On-board-chargers
- High  $di/dt$  noise loop, e.g. motor drives, DC-DCs
- Galvanic isolation provides a safety feature, but the transformer cannot block high-frequency radio frequency (RF) signals




Simplified Schematics of a DC-DC Converter

# Need for Speed?

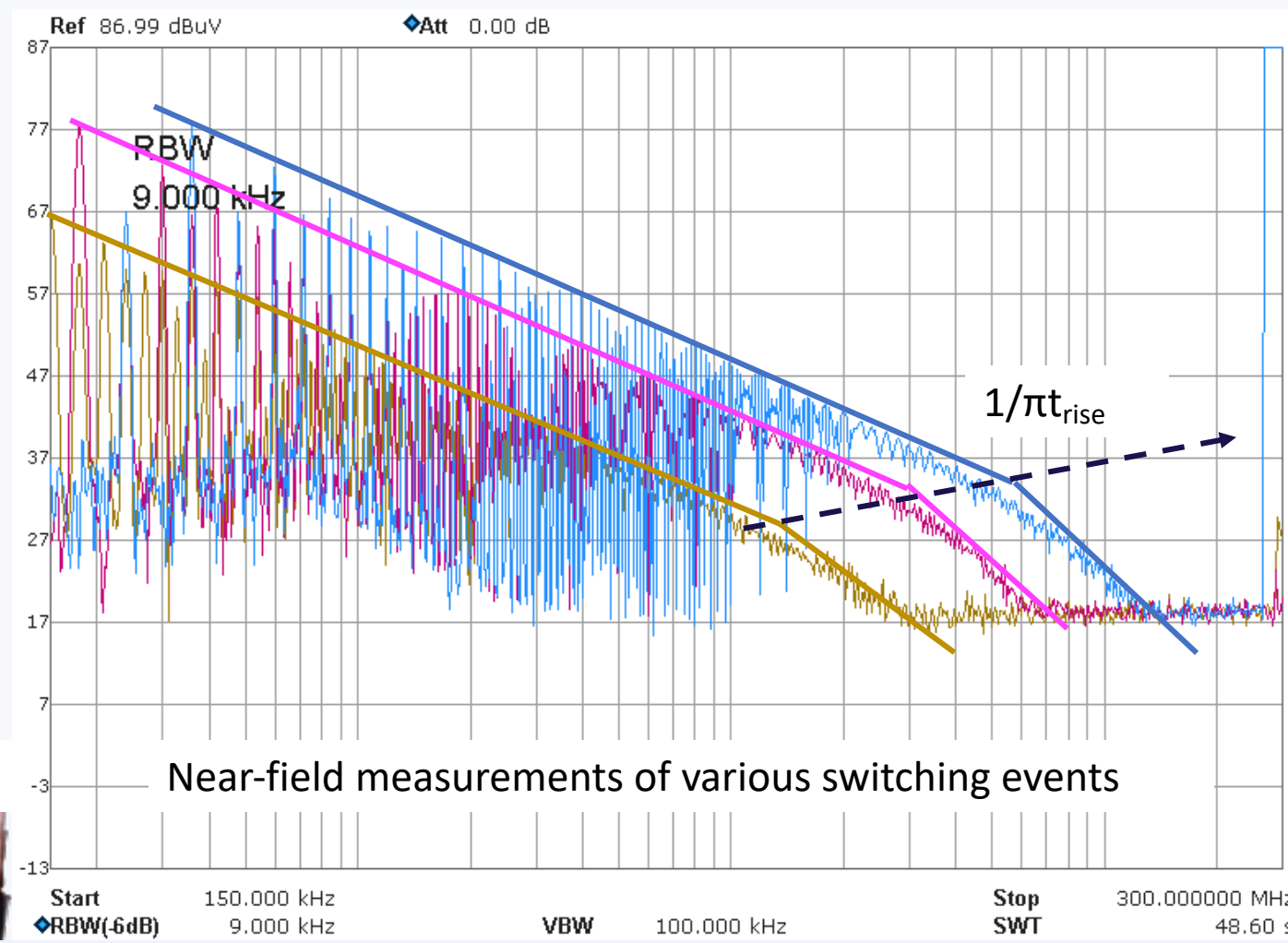
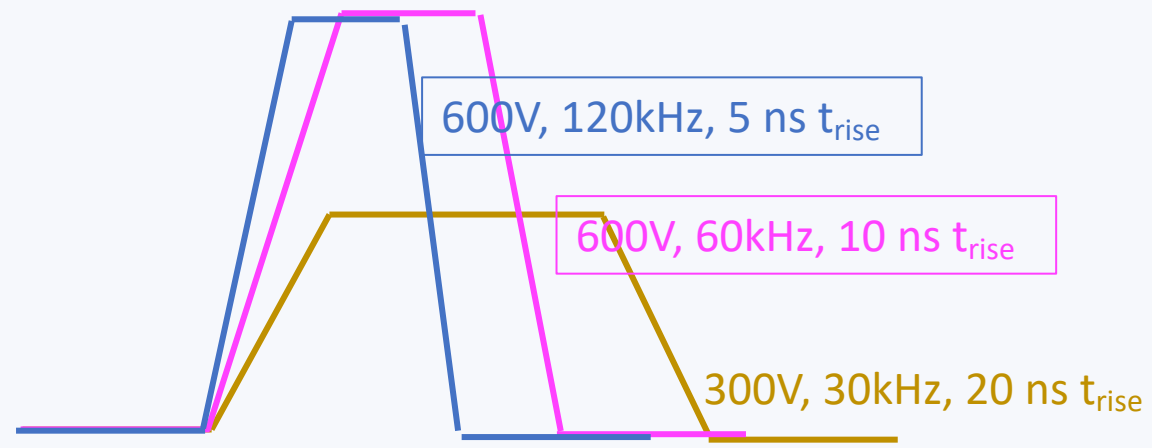


# Conducted Emissions - The 10-30 MHz "Hump"



Common mode equivalent circuit

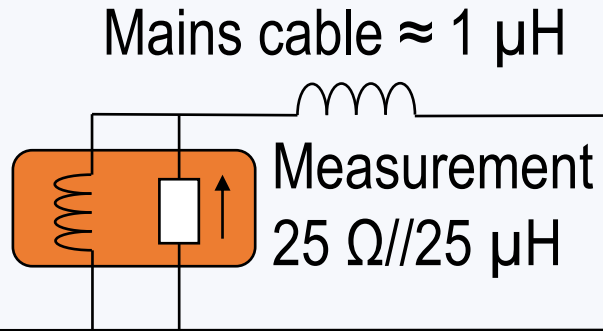

Choke self capacitance

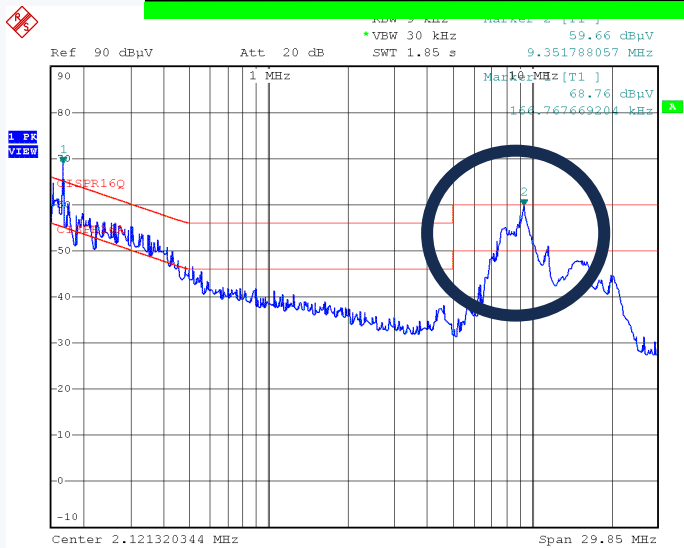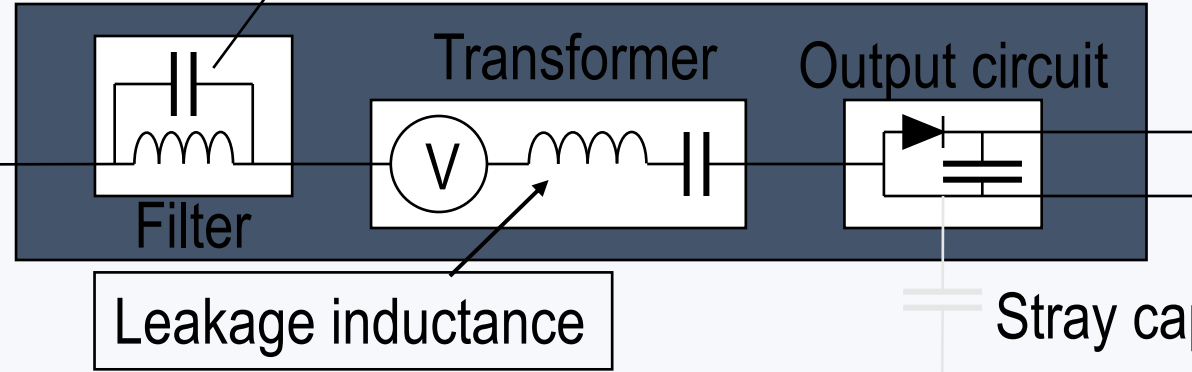



Resonance

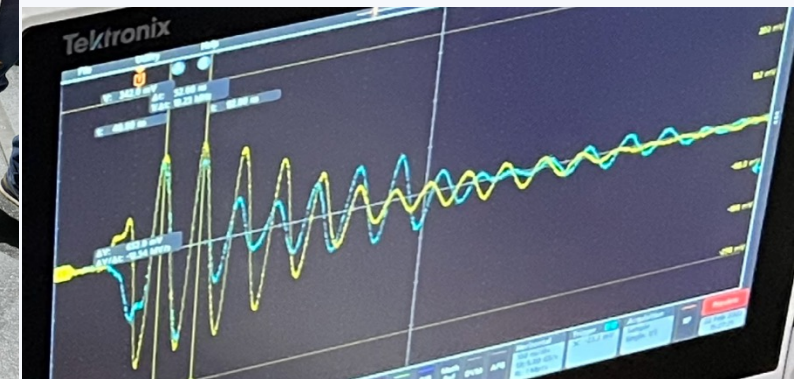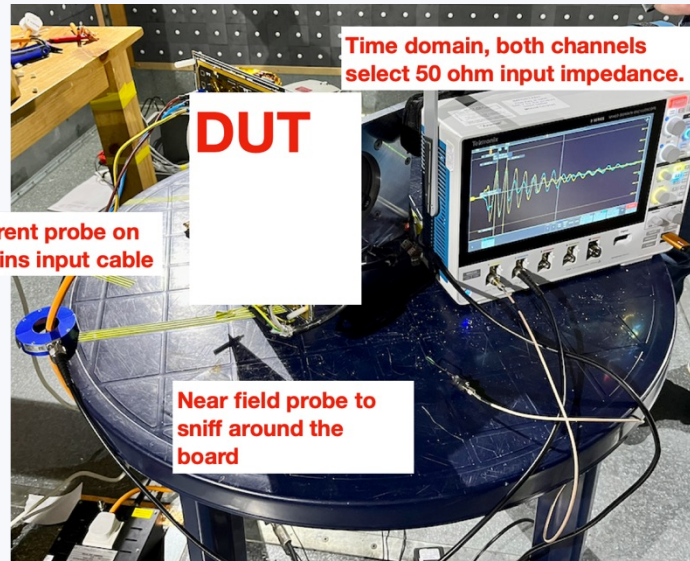


Conducted Emission Test Result of a SiC PFC Circuit



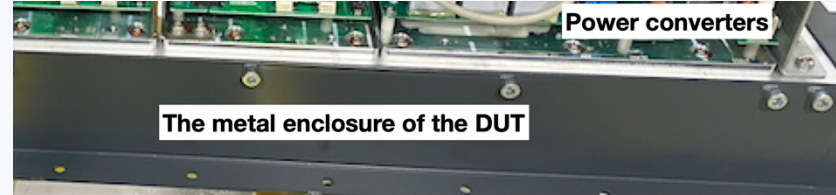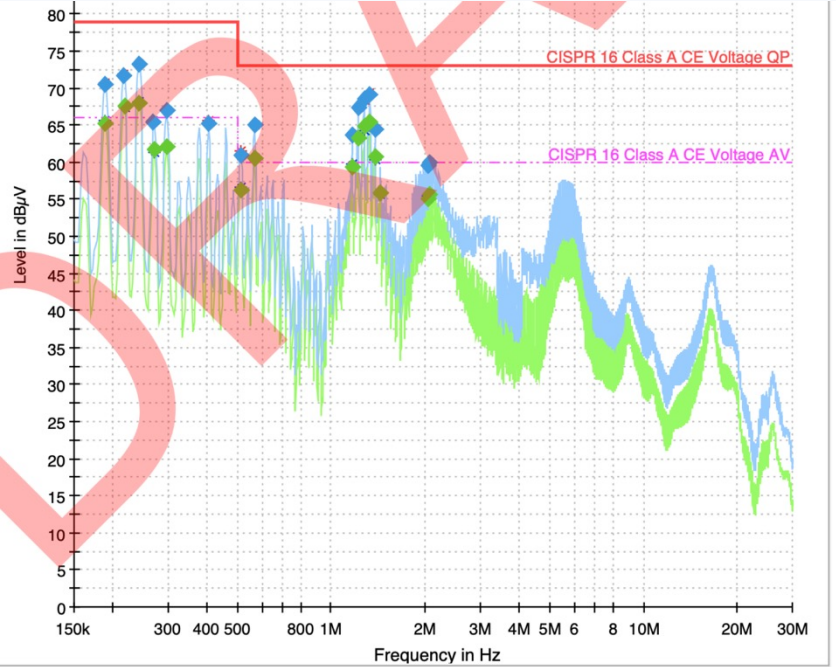
# Conducted Emissions - Low-frequency Common Mode Noise





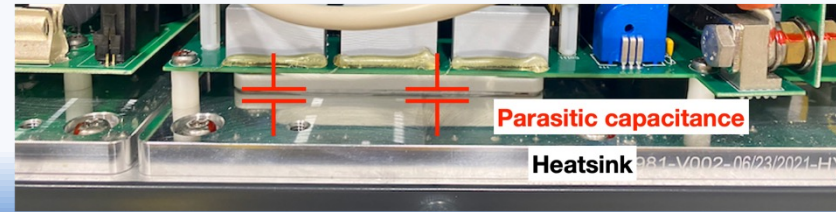
(a) the power converters are bolted to the heat sink which is earthed



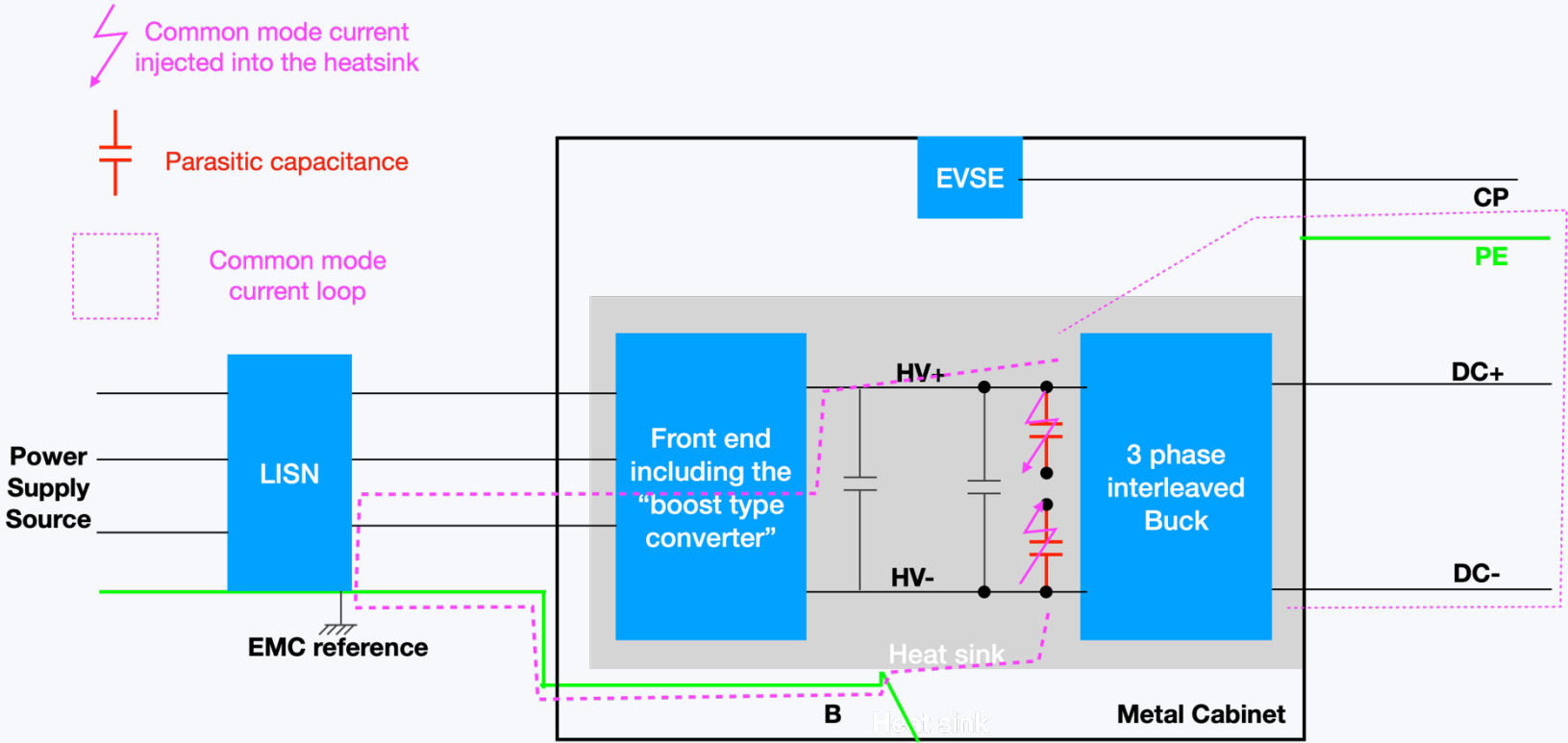
(b) A detailed view between the power switches and the heatsink


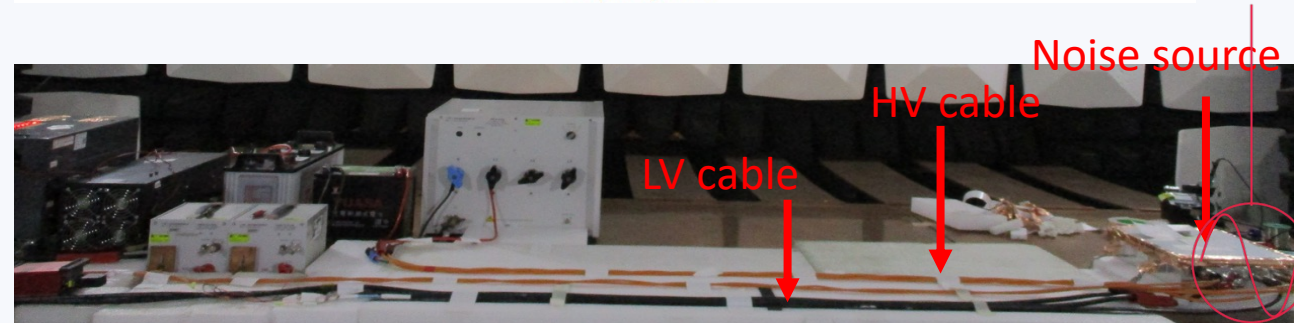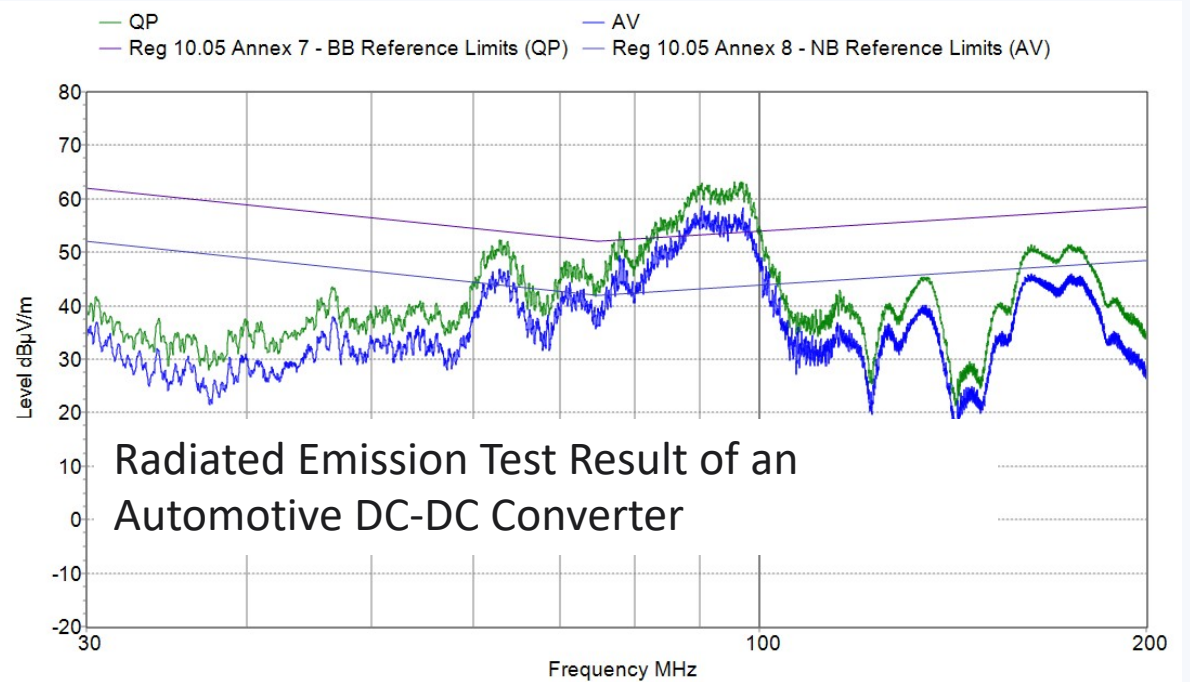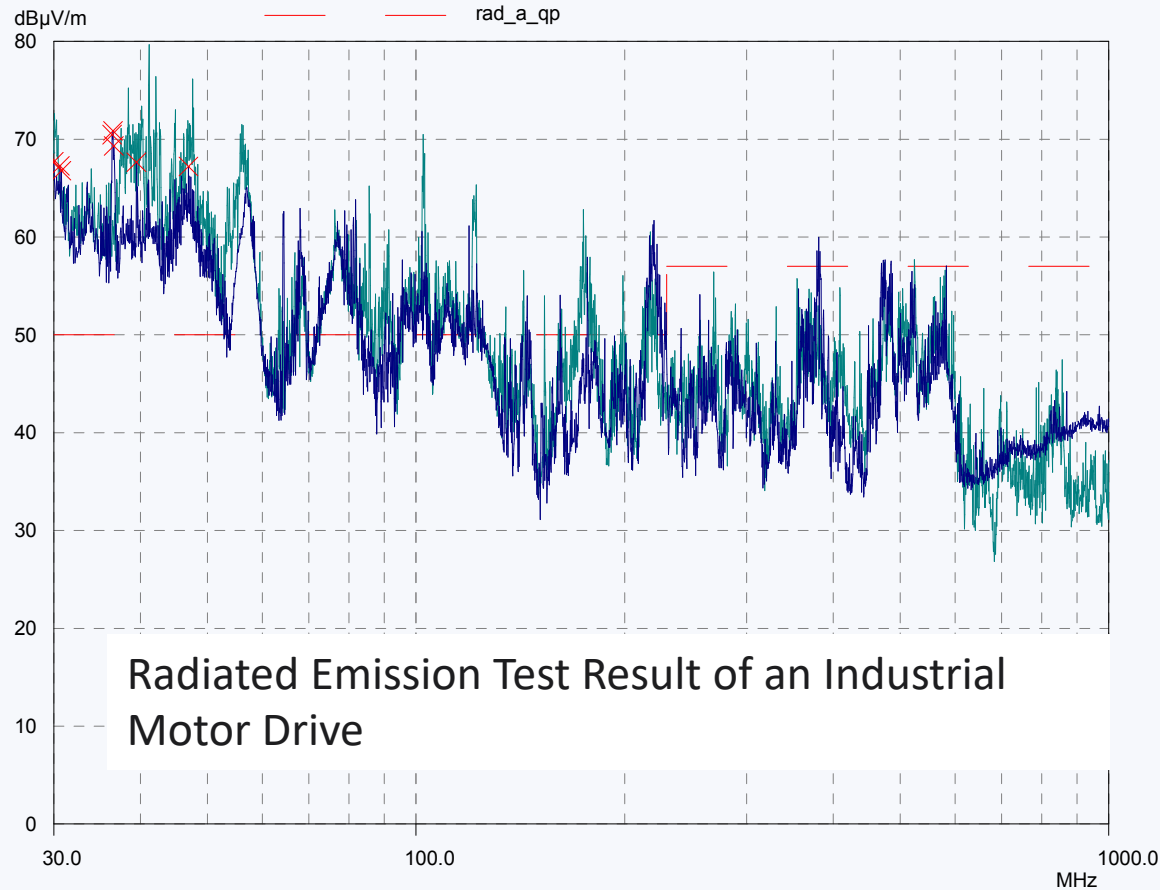
# Radiated Emissions – Cables as the Main Radiators


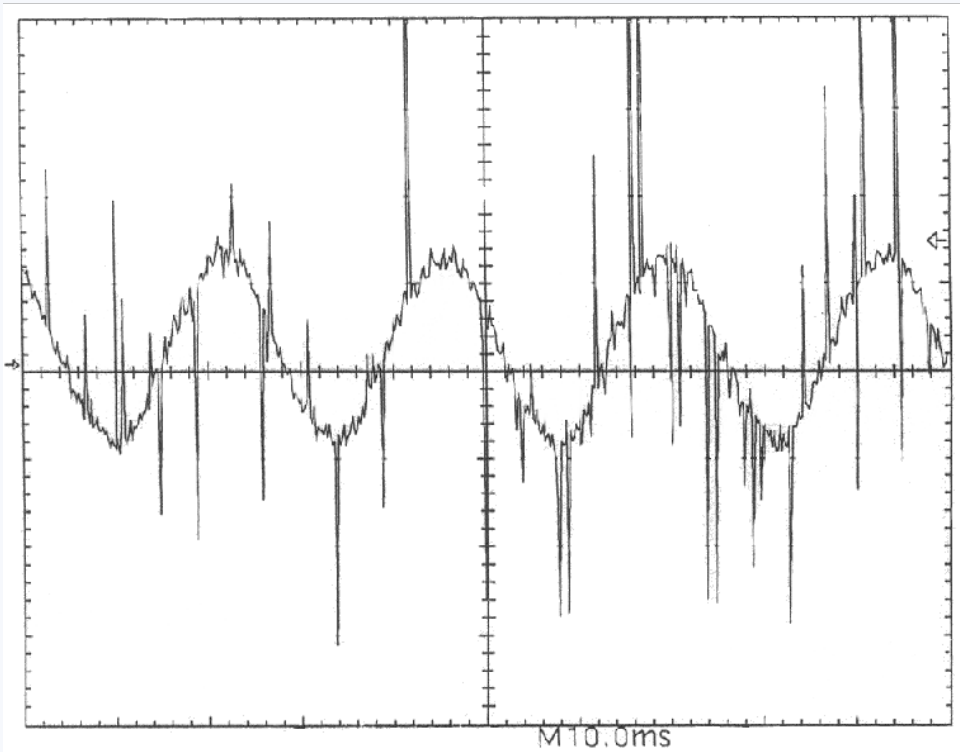
# Going Beyond Meeting Regulatory Requirements



A highly distorted current waveform of a motor  
(sources: Rockwell Automation)

$$I_{ph} = I_{fundamental} + I_{harmonics} + I_{switching} + I_{transient}$$


- The fundamental content depends on the motor speed.
- Low-frequency noise (kHz - 10s of kHz range) arises from the lower harmonics content of the current waveform.
- Broadband noise (30-300 MHz) is generated due to the fast rise time of the switching devices.
- High-frequency noise (>300 MHz) results from events such as reverse recovery charge of a body diode or occasional electrical breakdown caused by bearing current in an electric motor.

Insulation Breakdown, Bearing Lifetime, Sensor Inaccuracy, etc -> Functional Safety?


# What shall we do?



Design, Develop & Pray

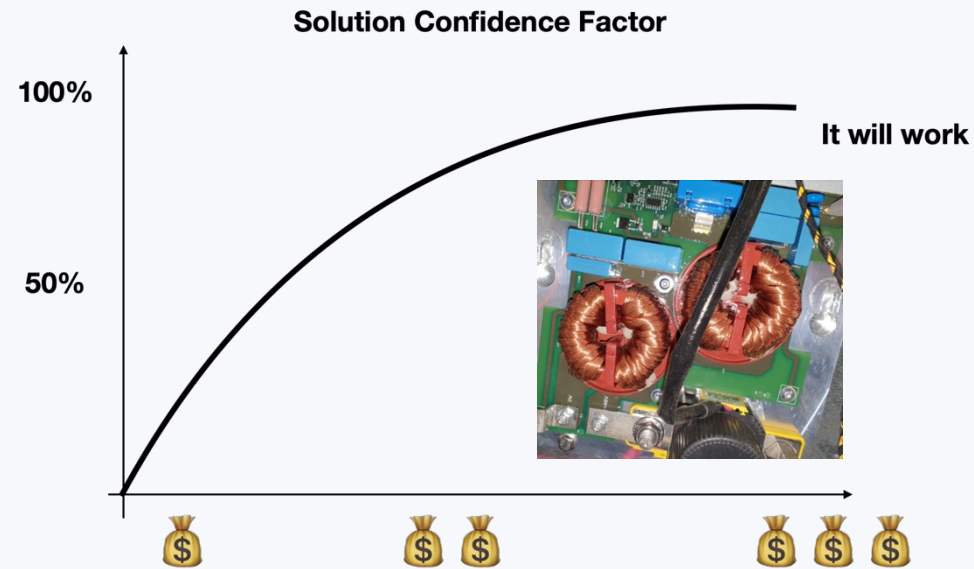


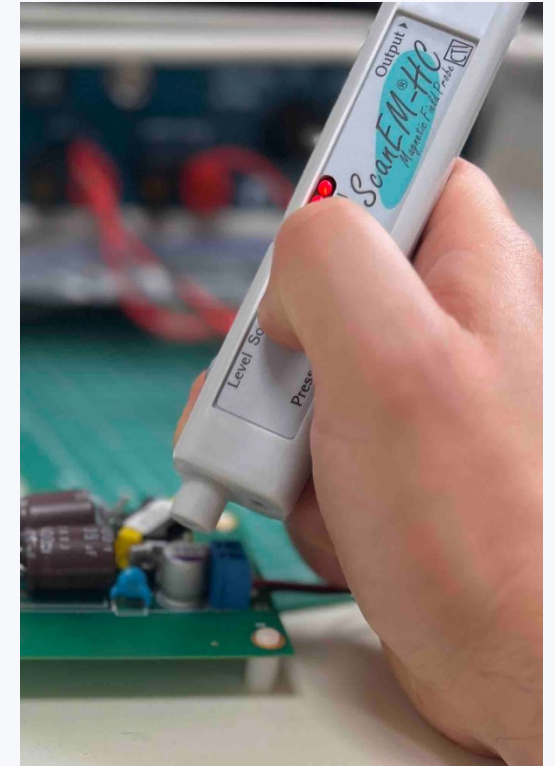Filtering & Shielding, the More, the Better.





Identify, Locate & Solve

# Demystifying "Ground"

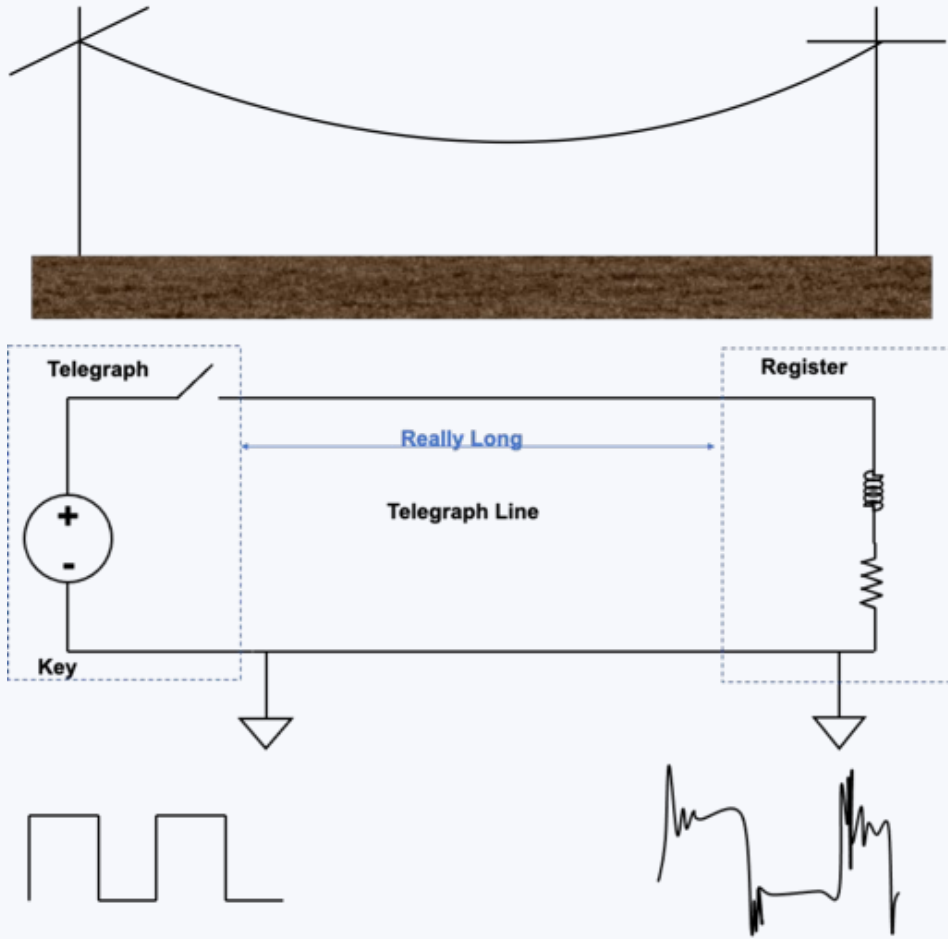

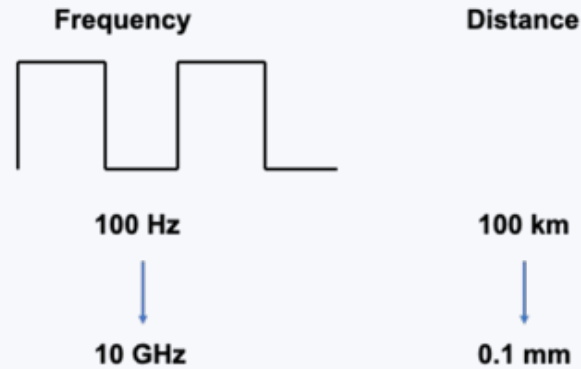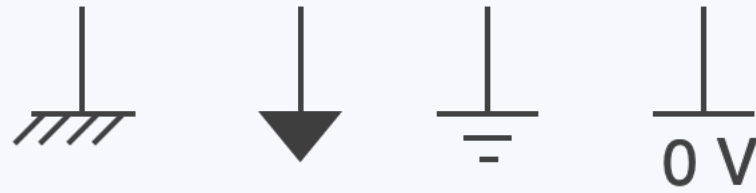A telegraph system that Samuel Morse built



Sending a GHz signal on a PCB is, electromagnetically speaking, almost like sending a Morse code across the country.

As a rule of thumb, if the device you are transmitting electric signals across is larger than 1/10 of a wave length, then you need to start thinking about transmission line theory.



An FPGA chip on the PCB

# Searching for a “Quiet Ground”





- Often referred to as “Reference Ground Plane”
- Made of copper, brass, bronze or galvanised steel, the ground plane is the top metallic surface on the test bench/table and electrically bonds to the walls or the floor of the shielded enclosure such that its DC resistance does not exceed 2.5 mΩ.
- Conducted emission is to measure the noise with respect to the “reference ground plane” or “Ground plane”.

Where is the “ground”?

- The quiet “ground” ?
- The RF reference point ?
- The earth?
- 0V, which?

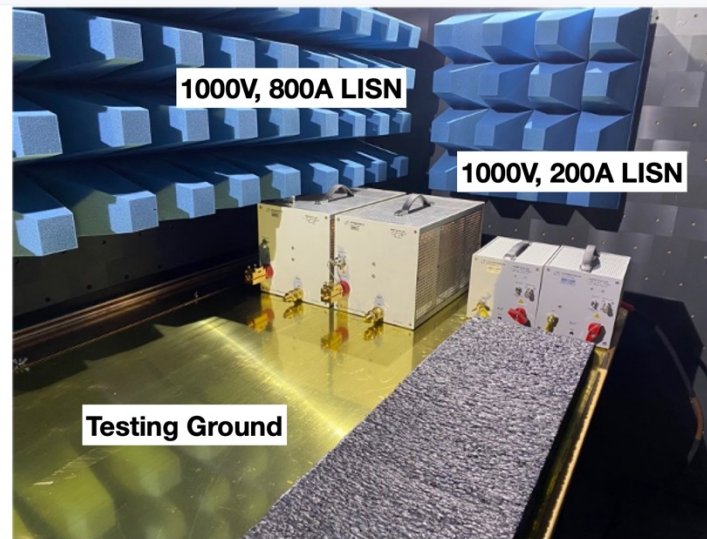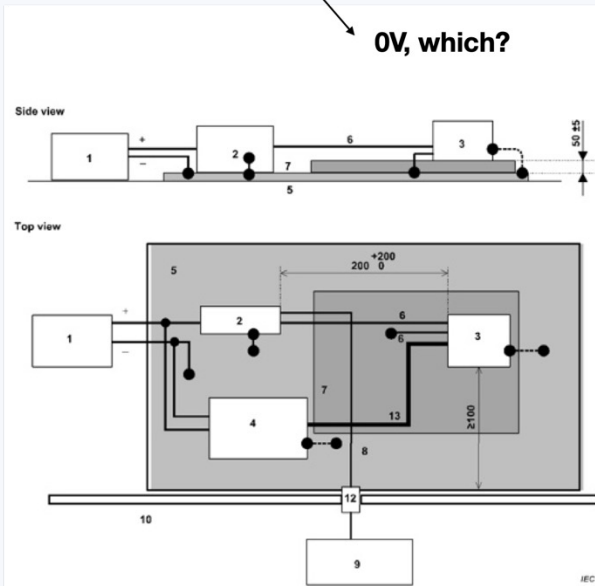For automotive applications, the “ground” is the negative end of the 12V battery, which is connected to the vehicle chassis.




Conducted emissions set-up - CISPR 25




A popular milli-ohmmeter used for checking the continuity of the ground plane and LISN connections


# The On-Board Charger “Ground” Puzzle

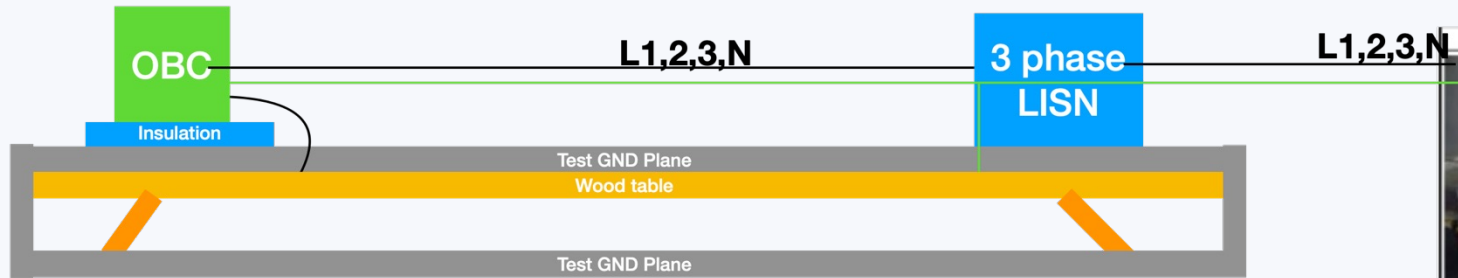



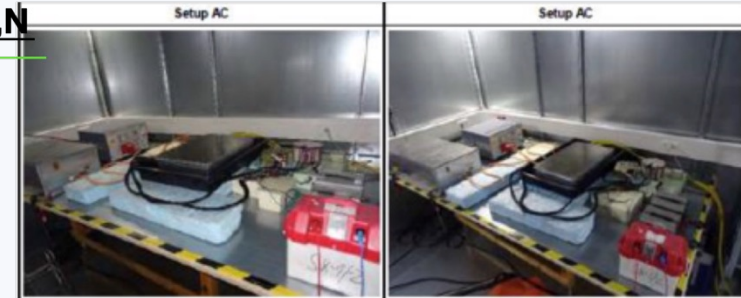
**Component test - The test ground plane is connected to the 3-phase LISN, with the PE wire connected; eventually, this ground plane is connected to Earth.**



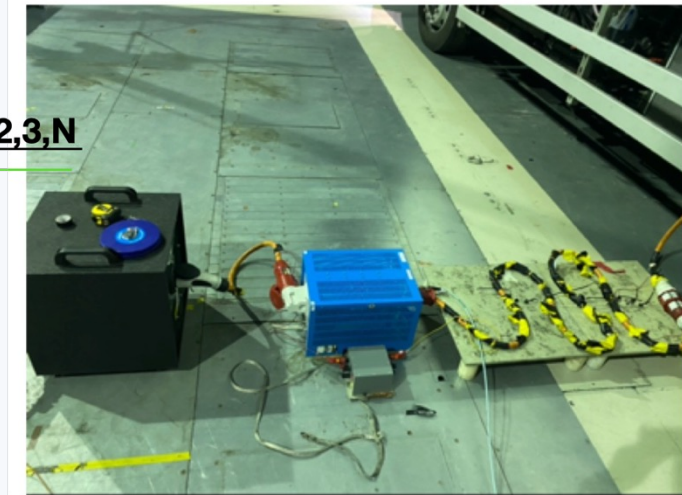**Vehicle test - Very similar to the component test, but there is no electrical connection between the vehicle chassis and the test ground plane. The vehicle chassis cannot be compared with a test ground plane (in terms of conductivity) either.**




# The Return Current Path

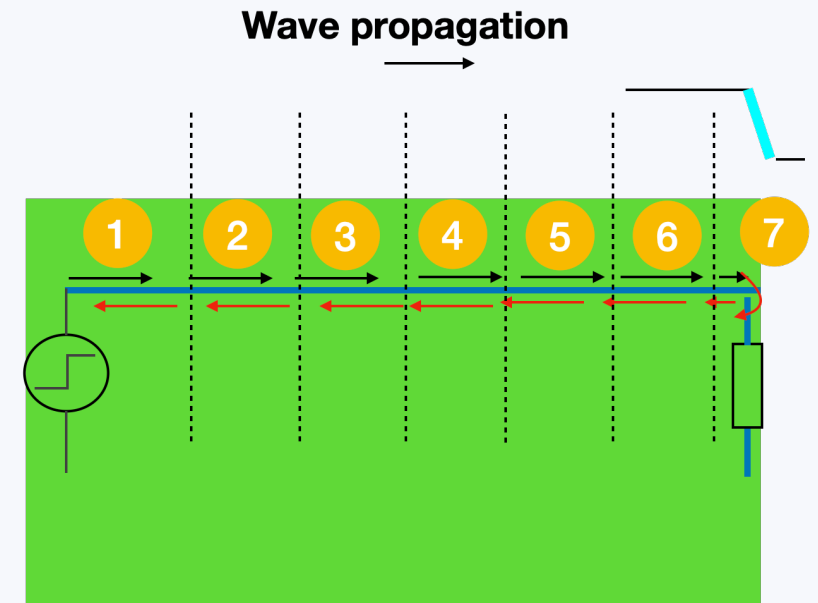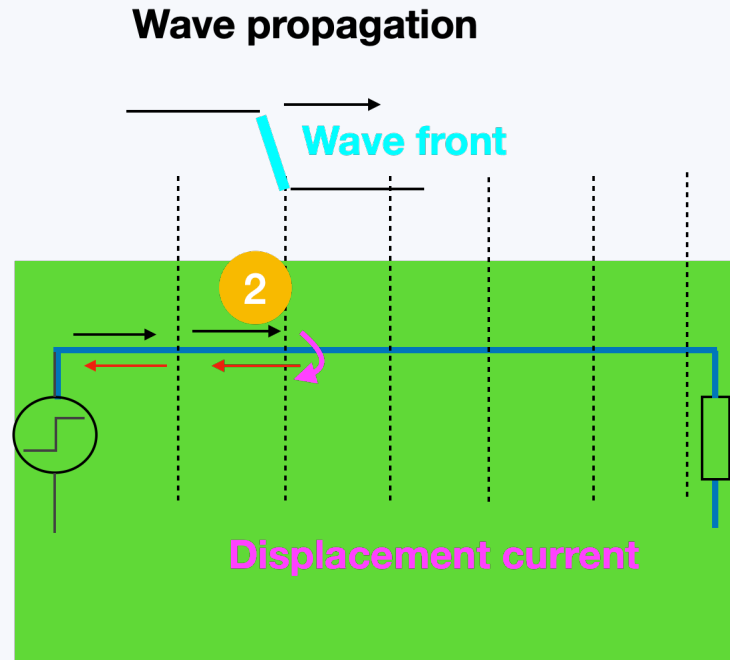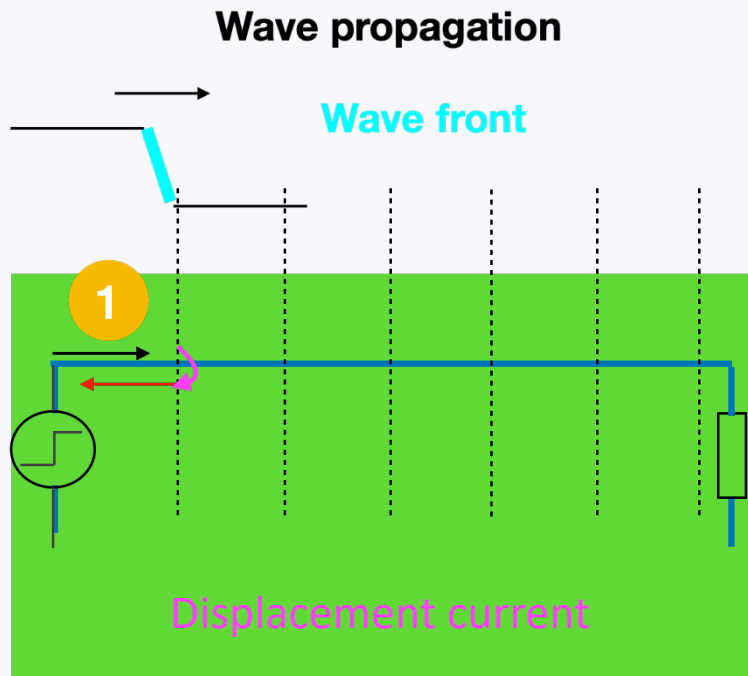





# Common “Ground” Issues

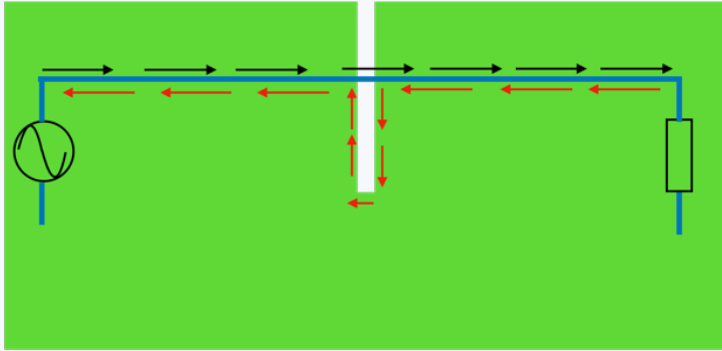

Ground plane break

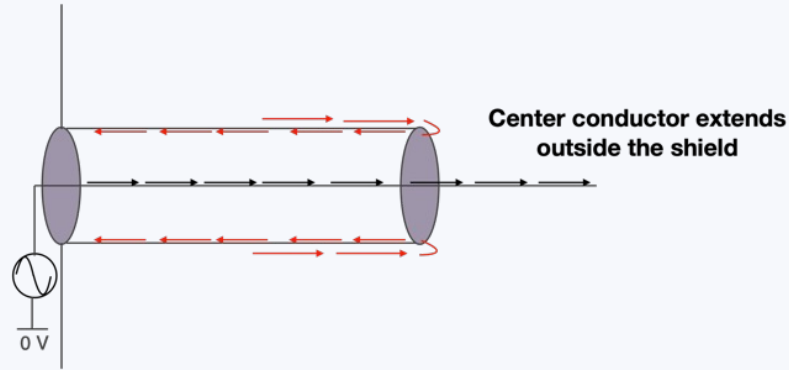





Conductor extends outside the shield

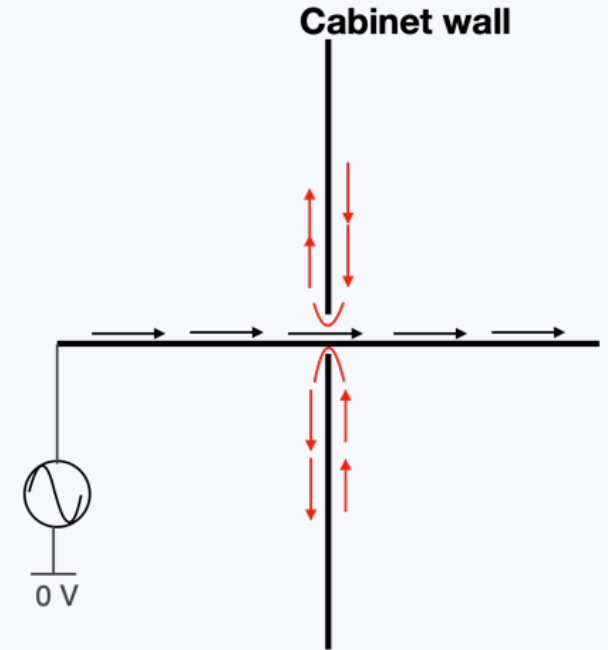


Wires penetrating into an enclosure

- Ferrite/Magnetic core has no improvement in emissions.
- Capacitors to chassis (common mode caps) make no difference/make things worse.
- “Balloon effect”
- Ineffective shielding
- Susceptible to immunity issues

# We Need One Ground and One Ground Only

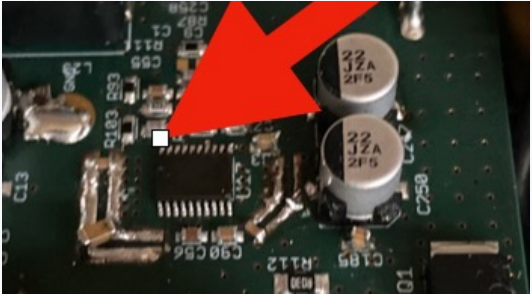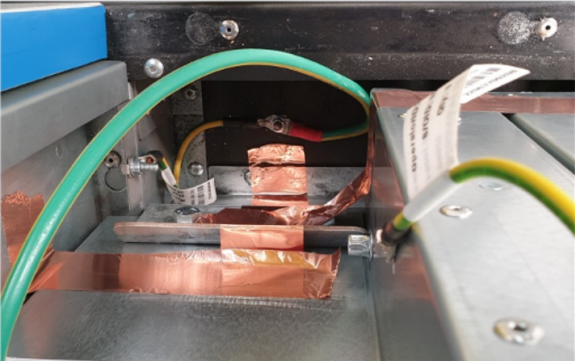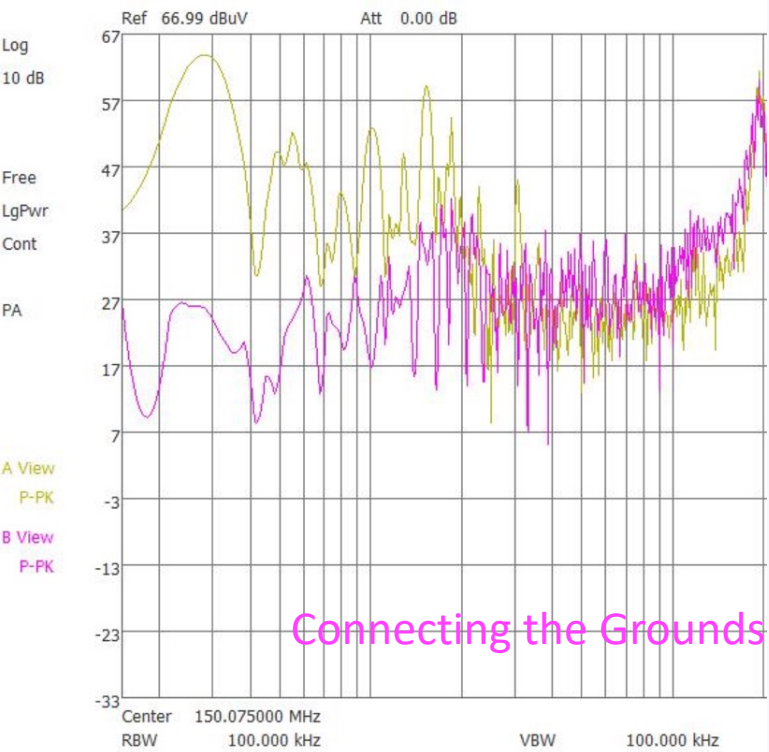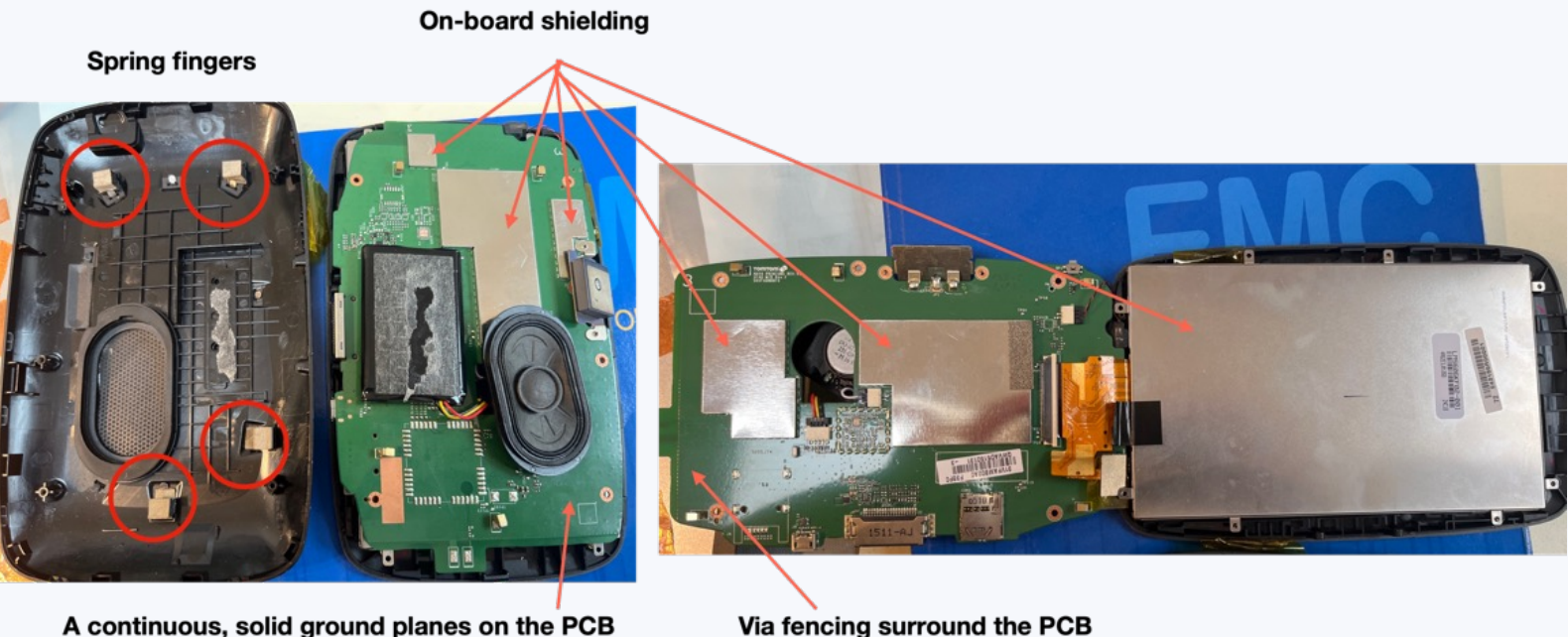


# Coupling Mechanism

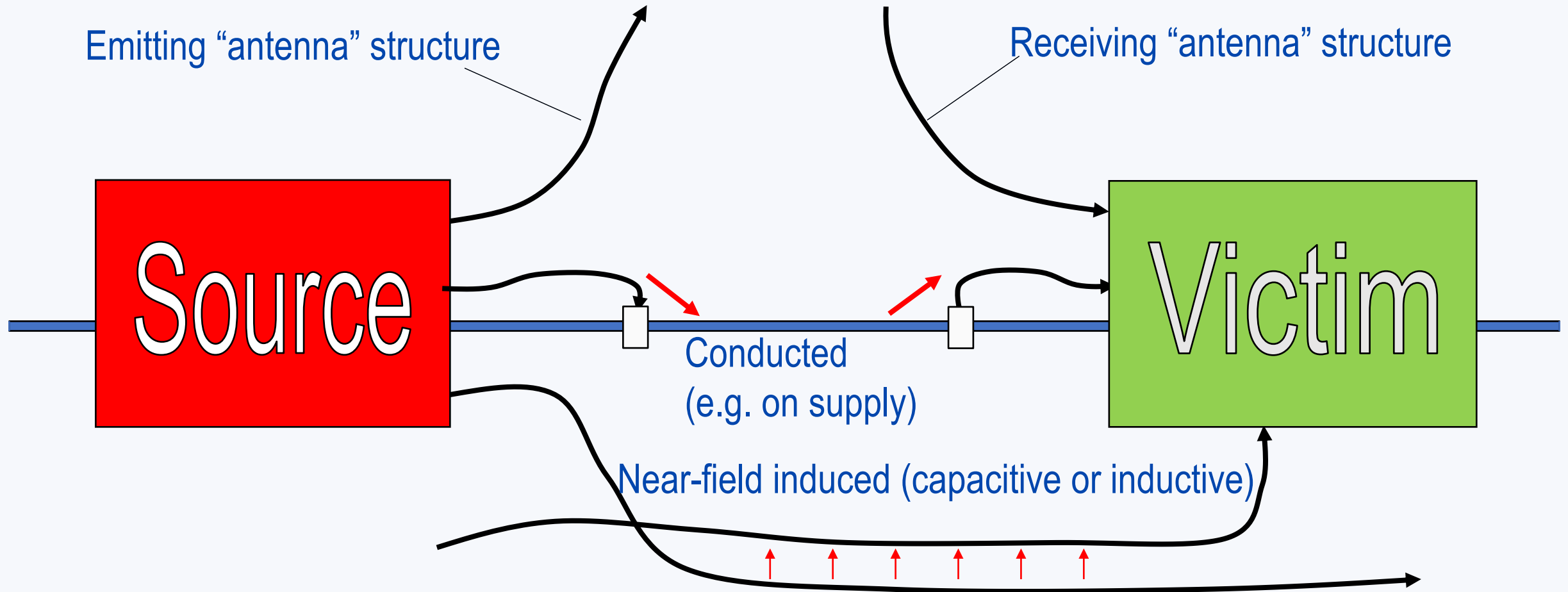


Source: T. Williams "EMC for Product Designers"
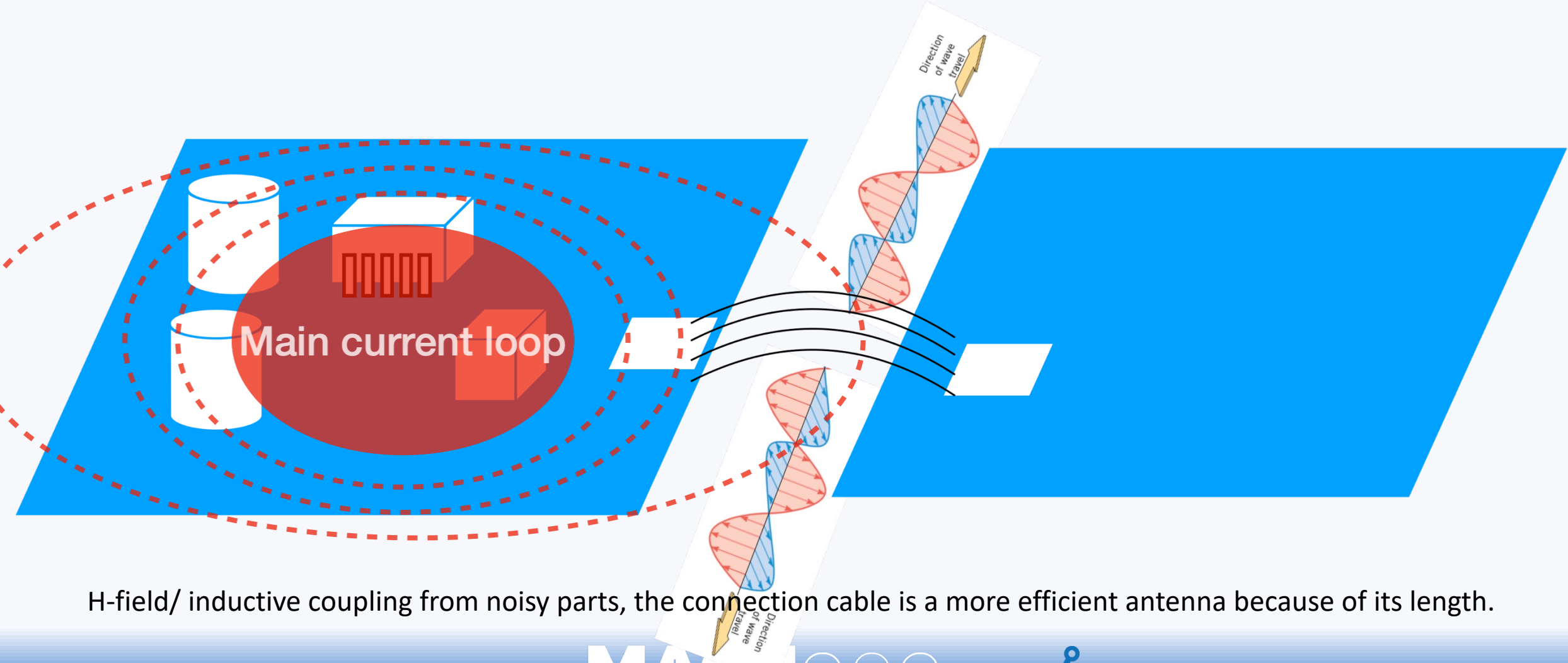
# Near-field coupling: Magnetic Field/Inductive Coupling



H-field/ inductive coupling from noisy parts, the connection cable is a more efficient antenna because of its length.

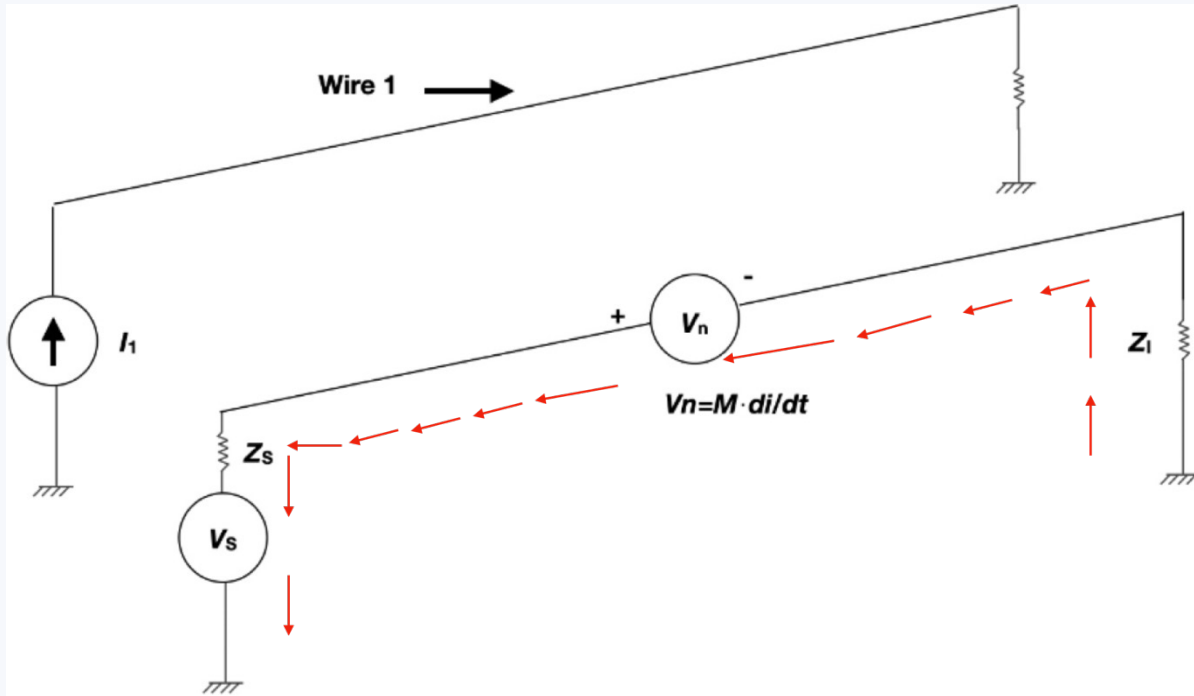
# Near-field coupling: Magnetic Field/Inductive Coupling



- Two conductors represent two parallel run wires, traces over a PCB, etc.
- Ignoring the capacitance effect in this example.
- $I_1$  represents the noise source, in this case, it is a current source.
- What is the induced interference voltage on  $Z_l$  ?


$$V_l = M \frac{dI_1}{dt} \frac{Z_l}{Z_s + Z_l}$$
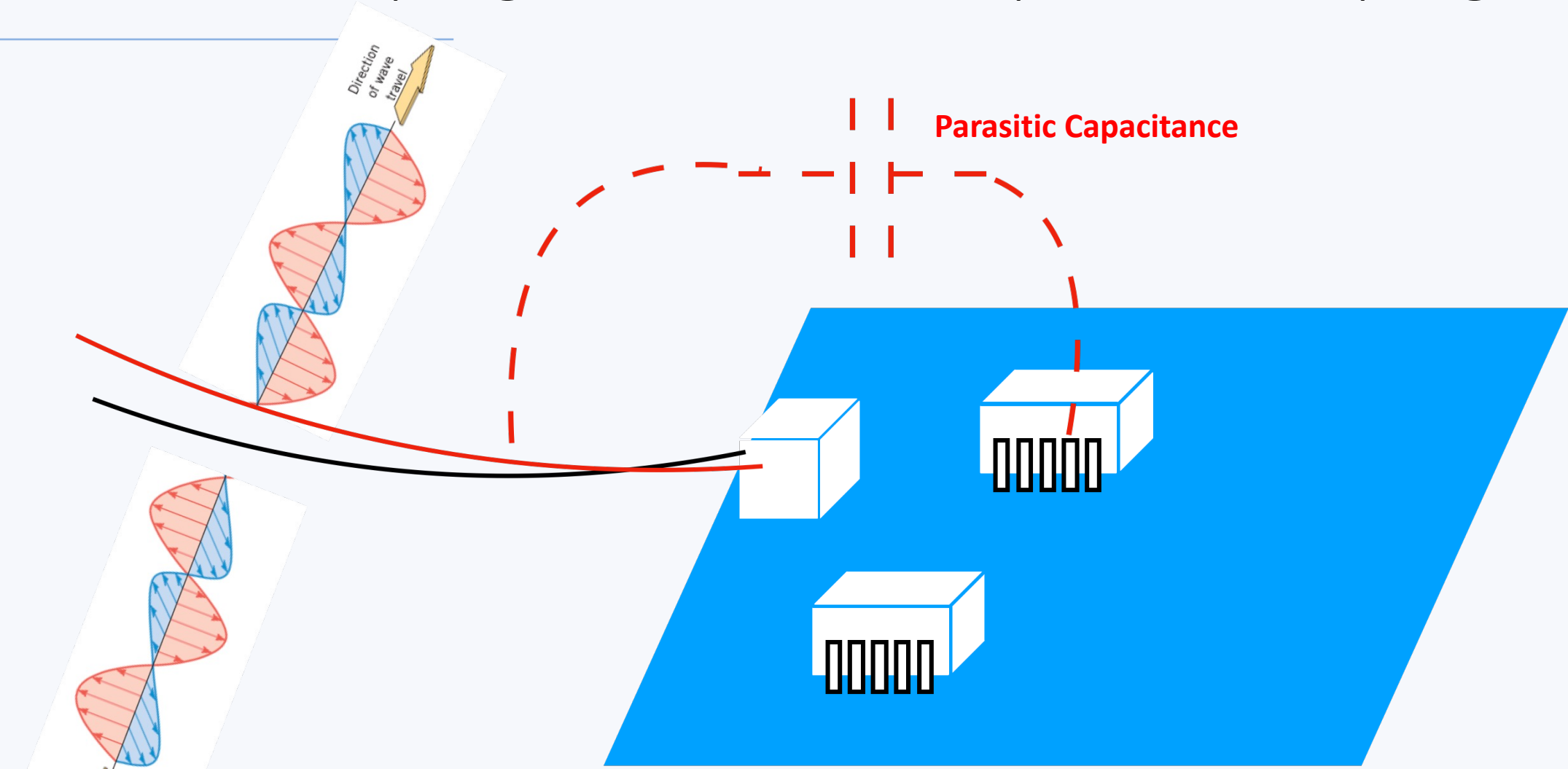
# Near-field coupling: Electric Field/Capacitive Coupling



E-field/ Capacitive coupling from noisy parts, the input cable is a more efficient antenna because of its length.

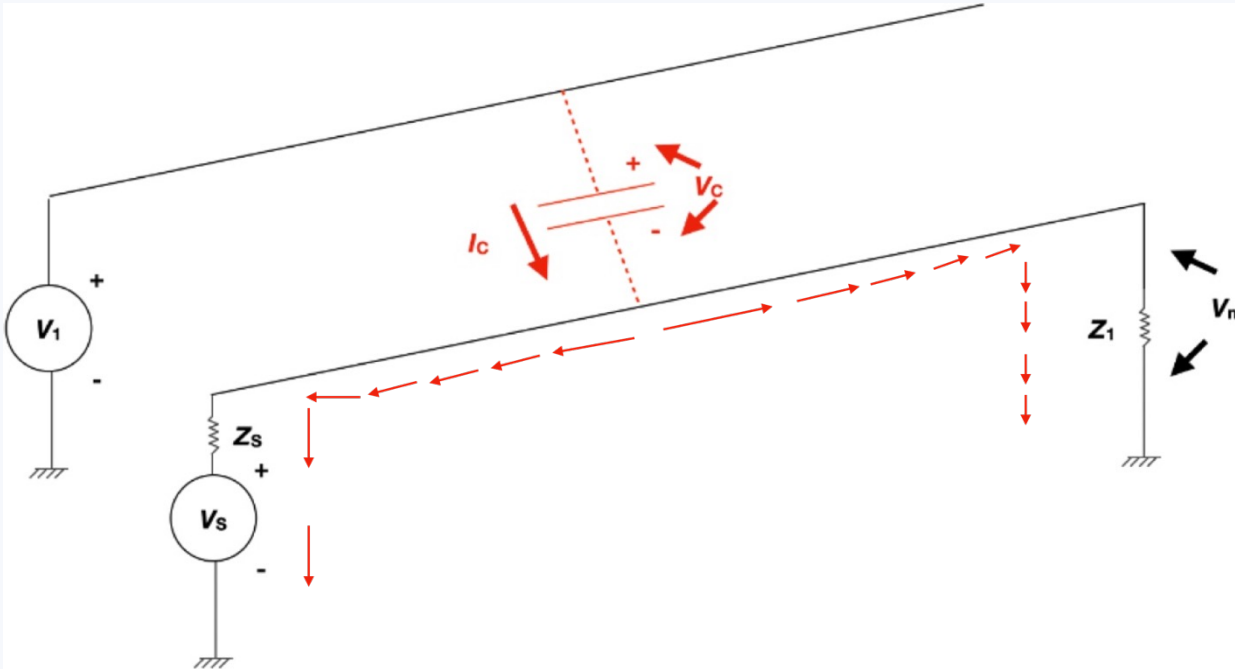
# Near-field coupling: Electric Field/Capacitive Coupling



- Two conductors represent two parallel run wires, traces over a PCB, etc.
- Ignoring the inductance effect in this example.
- $V_1$  represents the noise source.
- What is the induced interference voltage on  $Z_1$ ?


$$V_n = C \frac{dV_1}{dt} (Z_S || Z_l)$$

# Understanding Coupling and Parasitics


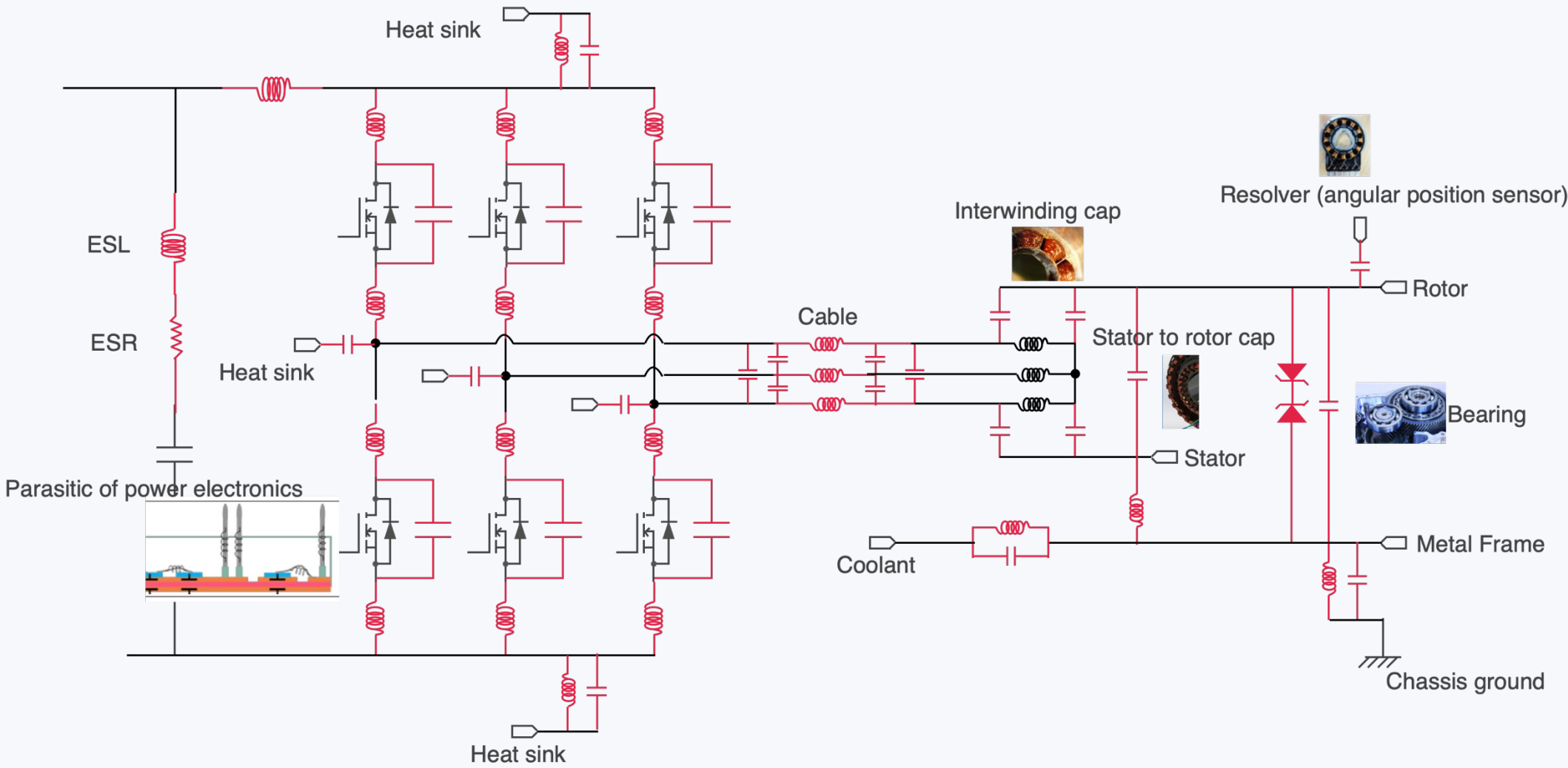





# Understanding Coupling and Parasitics:

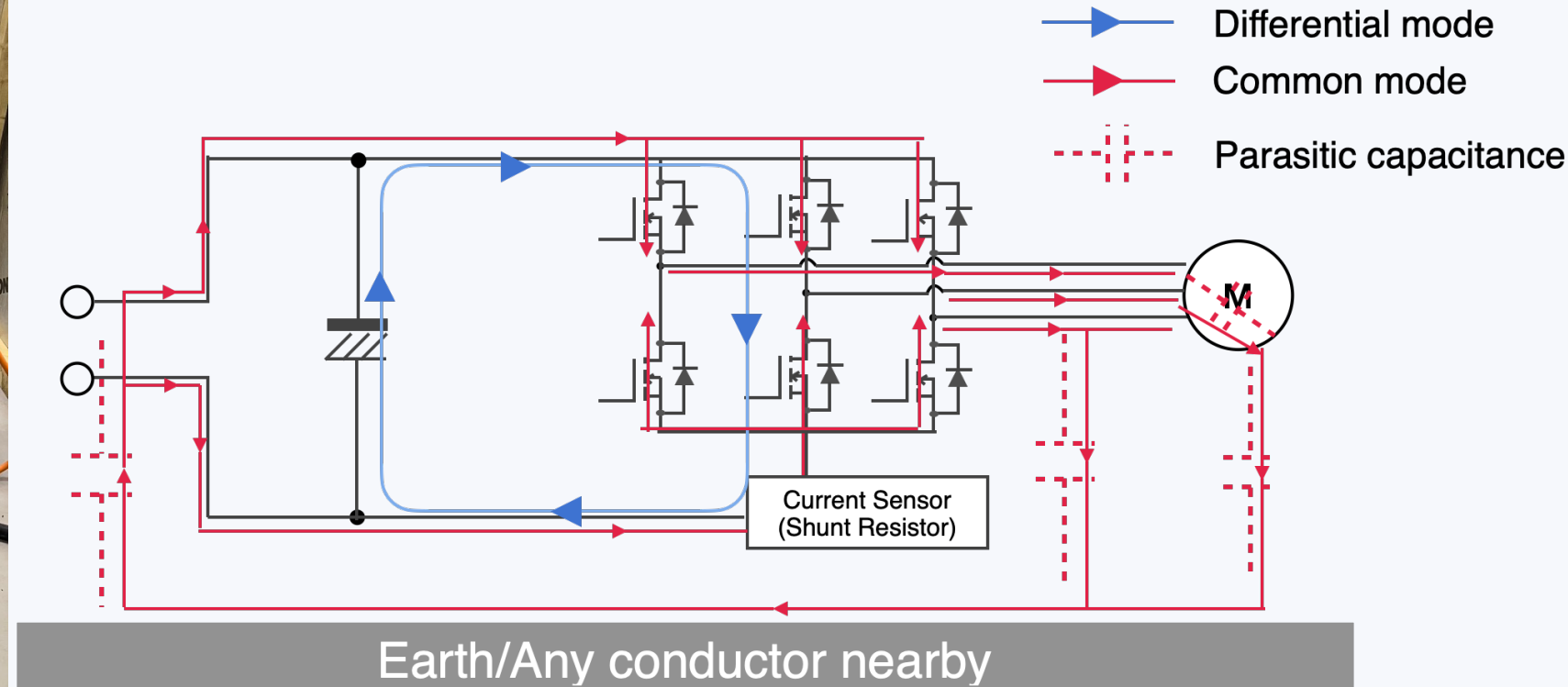

# Demystifying Common Mode Noise

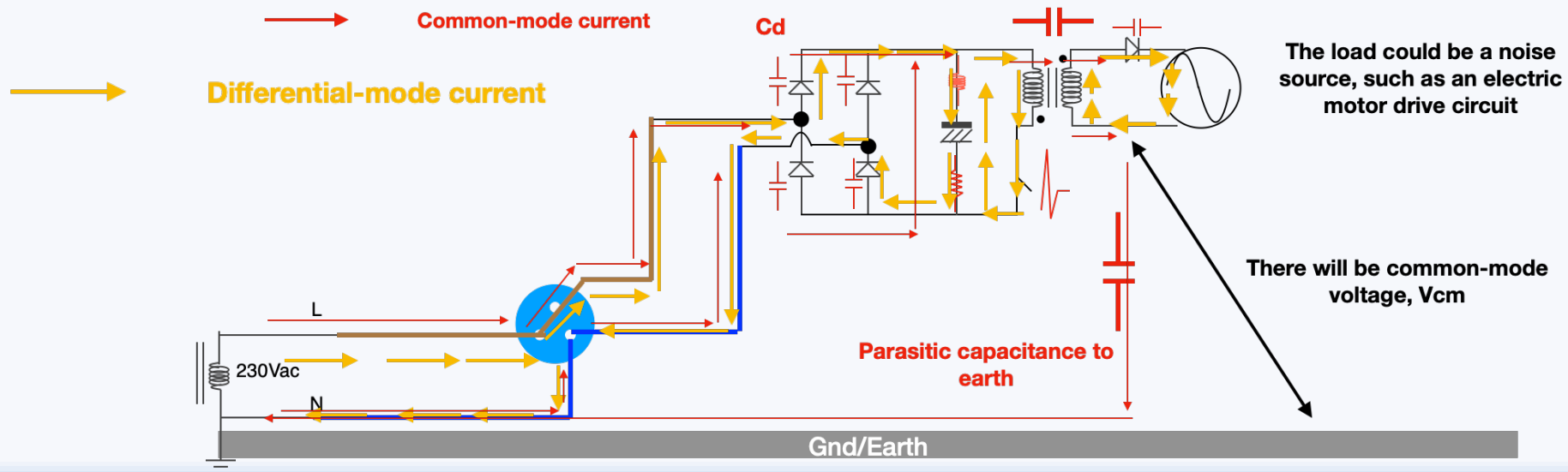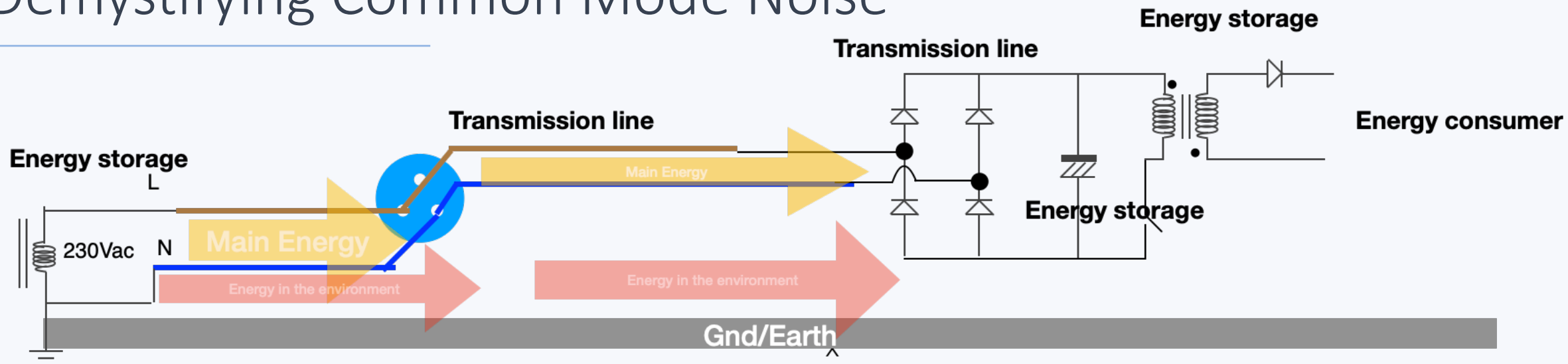

# Measuring the Common Mode Noise

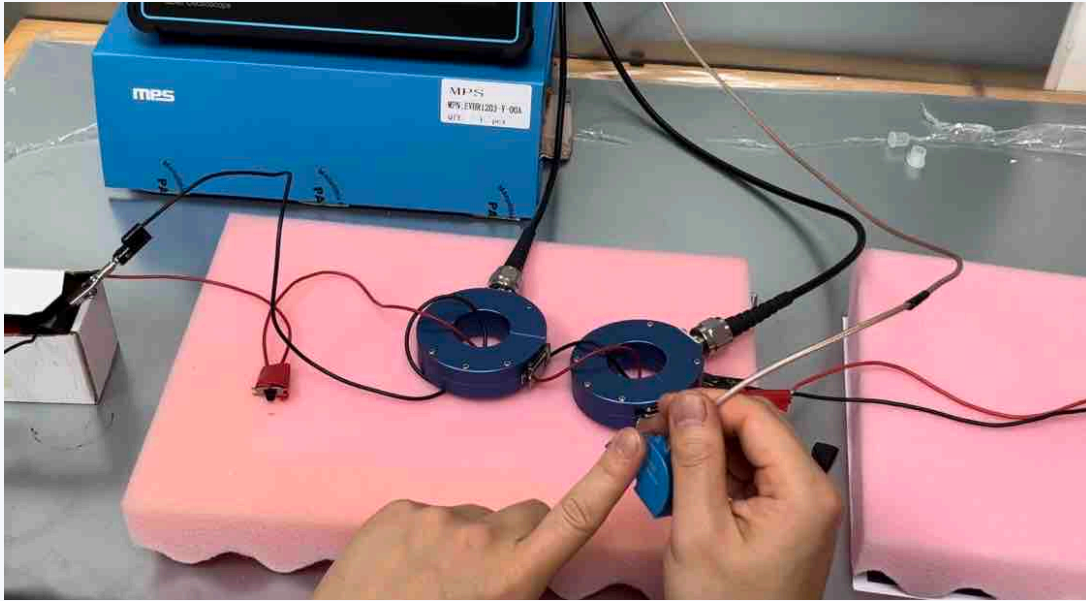

Using RF current probes





Forward common mode current and return current

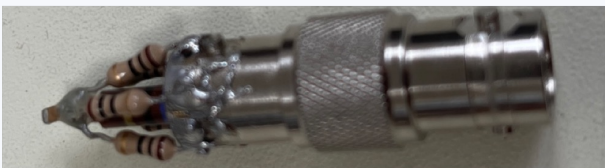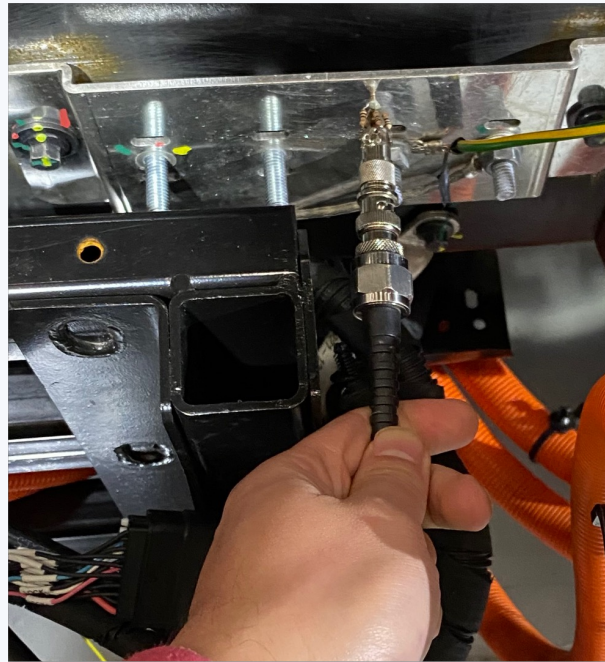
# Measuring the Common Mode Noise




Measuring surface currents on the vehicle chassis



A home-made resistive probe

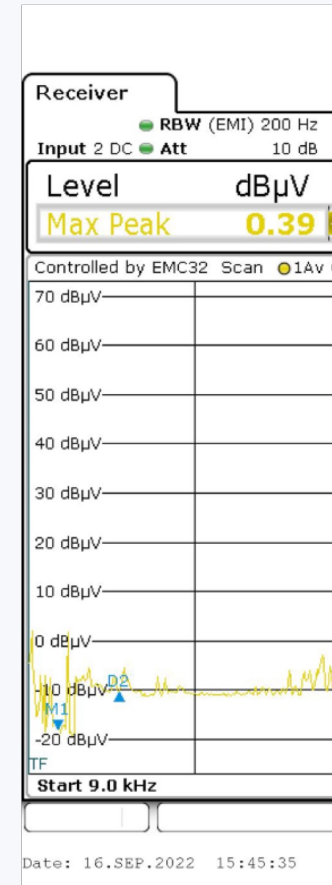


(a) when the OBC was off

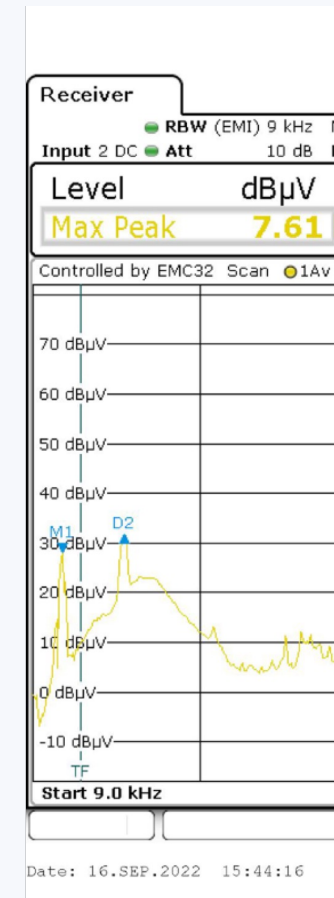

(b) when the OBC was on

The surface noise was measured in the low-frequency range

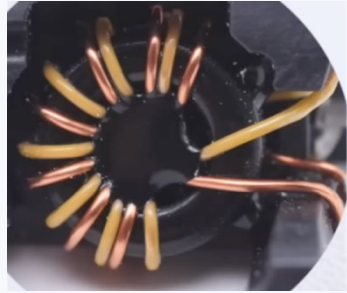
# Understanding Coupling and Parasitics: The Key to Designing EMC Filters




Bifilar winding on a toroidal core



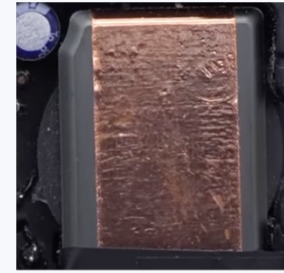Flat-wire winding on a sectional wound CMC



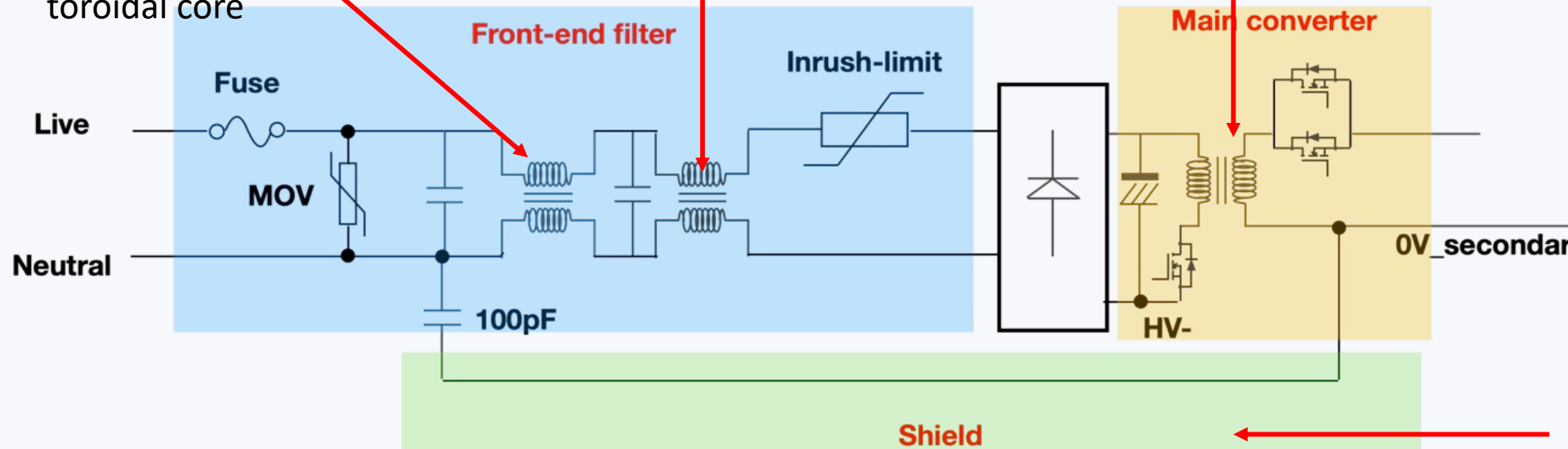A magnetic flux band around the transformer



A simplified isolated power supply circuit using GaN devices



# Benchtop EMC Testing

EMI can no longer be an after thought!

- CISPR 25 Automotive EMC standard
  - Conducted Emissions: 150kHz-108MHz
  - Radiated Emissions: 30MHz-2.5GHz



Lyra's 4kW SiC DC-DC Converter

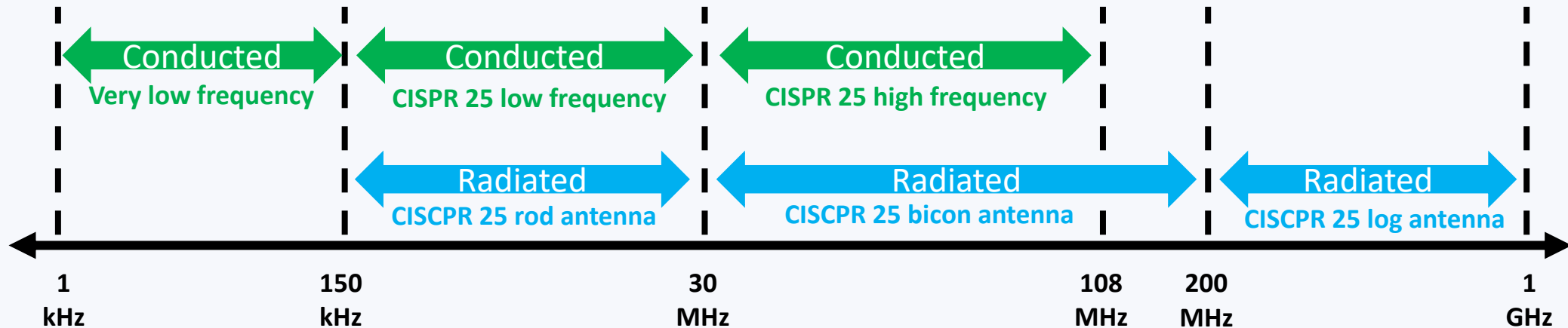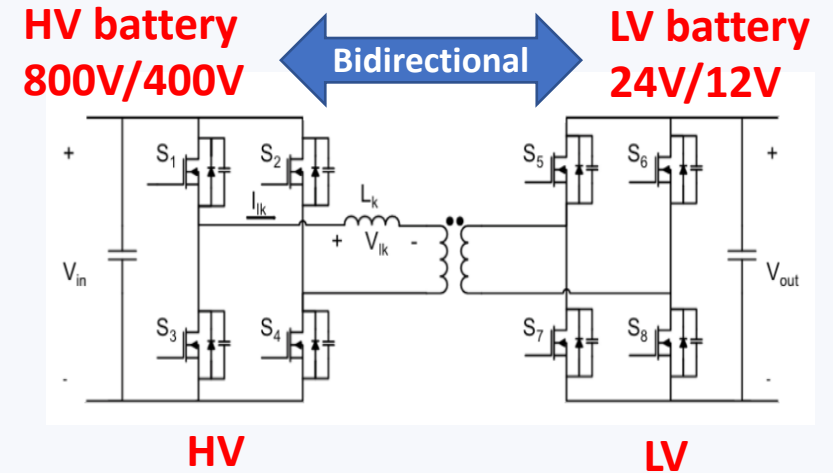


# CISPR 25 Testing Methods

- CISPR25 defines two methods for conducted emissions testing:
  - Current probe method
  - Voltage method.
- Both methods can be used to determine if the device under test (DUT) passes or fails the emission test limits.
- Test method is defined by the OEM requirements.


**Table 1. CISPR25 Class 5 Peak Limits for Voltage Method and Current Probe Method**

| Frequency (MHz) | Voltage Method (dB $\mu$ V) | Current Probe Method (Converted to dB $\mu$ V) |
|-----------------|-----------------------------|--|
| 0.15 to 30      | 70                          | 84   |
| 0.53 to 1.8     | 54                          | 60   |
| 5.9 to 6.2      | 53                          | 53   |
| 76 to 108       | 38                          | 38   |
| 26 to 28        | 44                          | 44   |
| 30 to 54        | 44                          | 44   |
| 68 to 87        | 38                          | 38   |

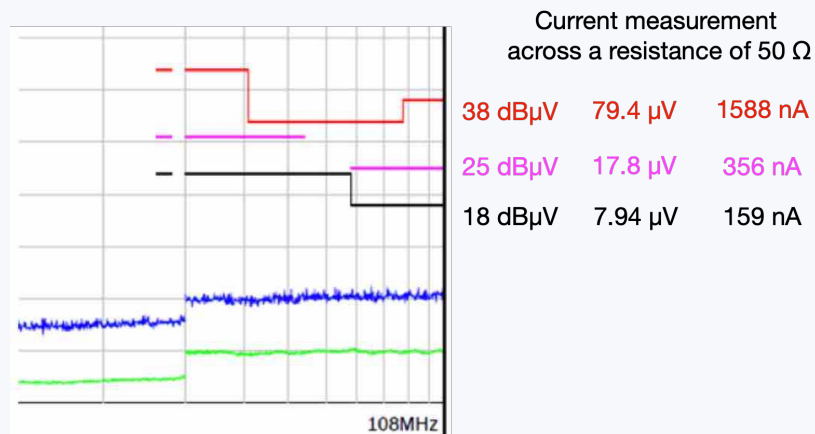

This is the limit for a 48-12V DC-DC which often has a power of 700W. But it is exactly the same limit for a 600V-12V DC-DC which has a power of 3kW, same limit for an electric motor whose power exceeds 250 kW.

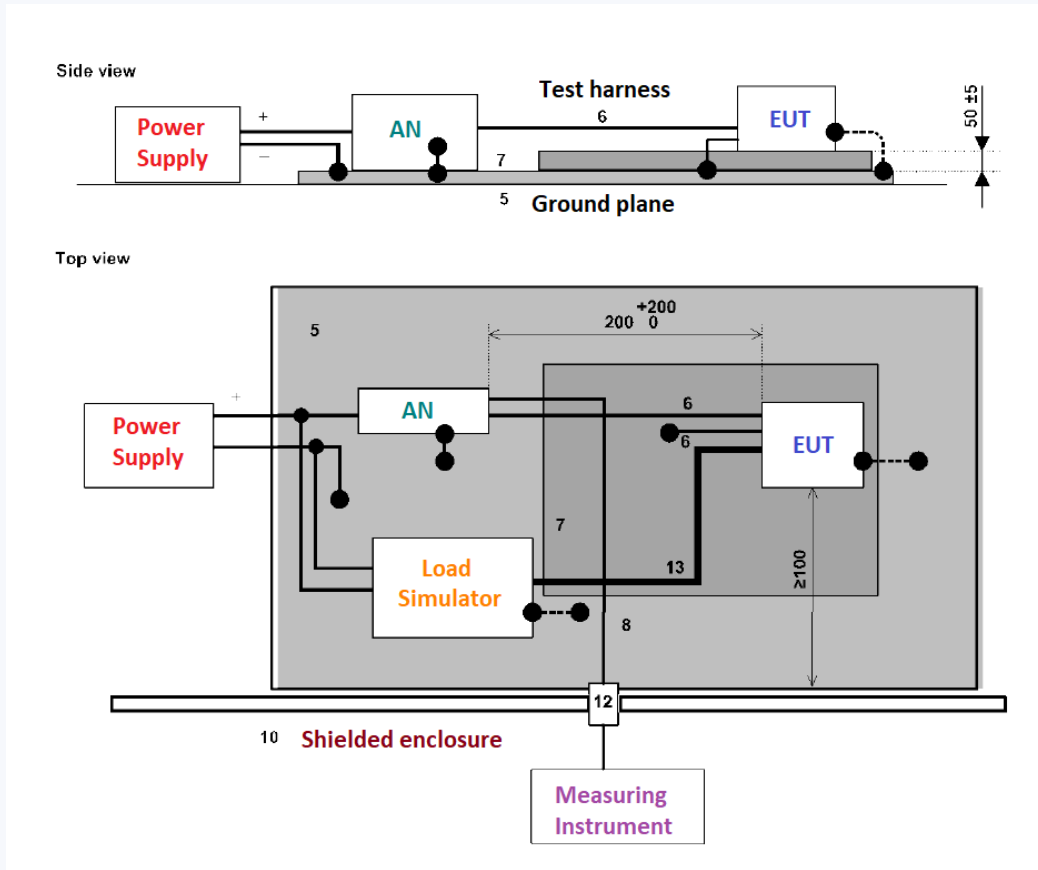
# CISPR 25 Conducted Emissions Test Setup



- 7 Low relative permittivity support ( $\epsilon_r \leq 1,4$ )
- 8 High-quality coaxial cable e.g. double-shielded (50  $\Omega$ )

EUT with power return line locally grounded

[1] CISPR 25:2016 © IEC 2016

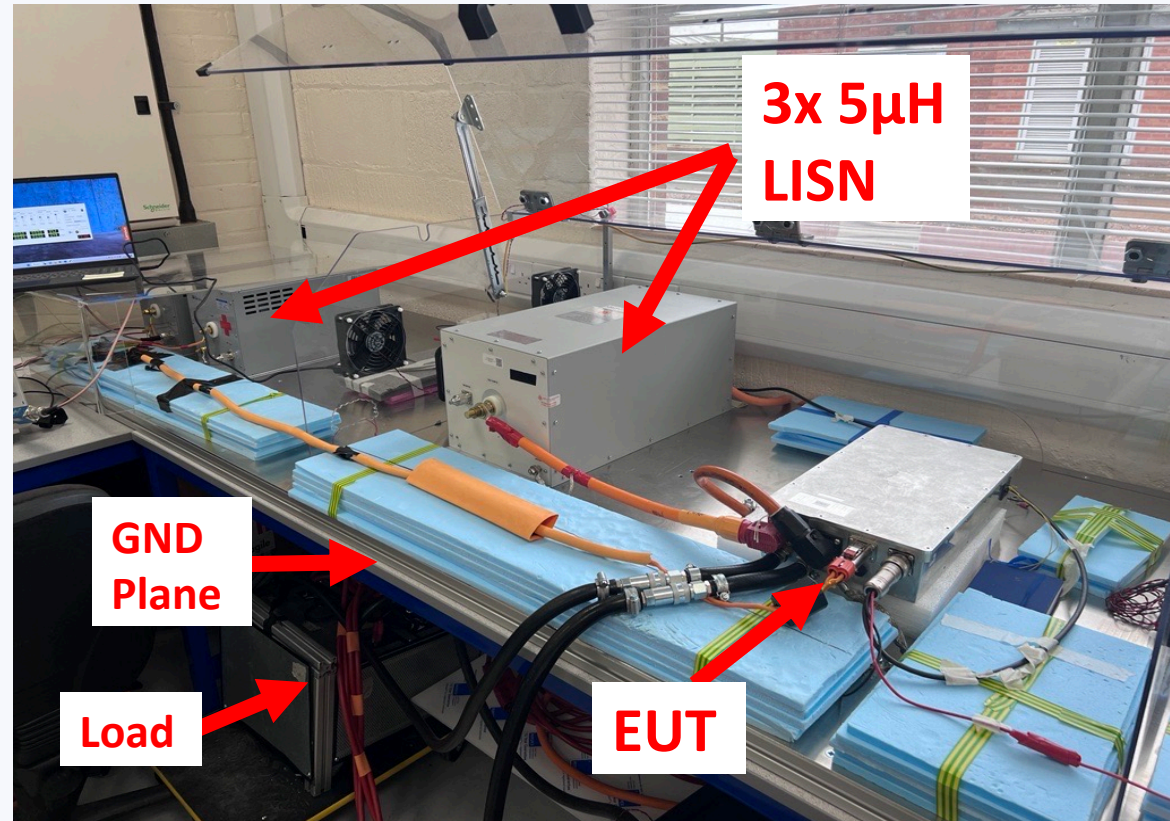



Test setup at Lyra




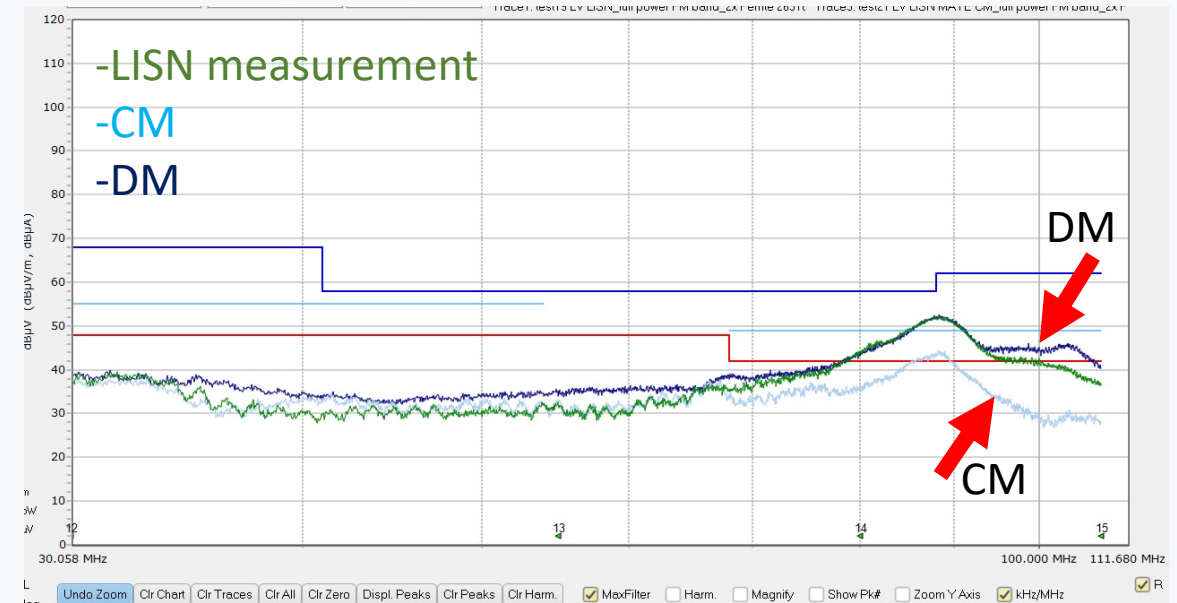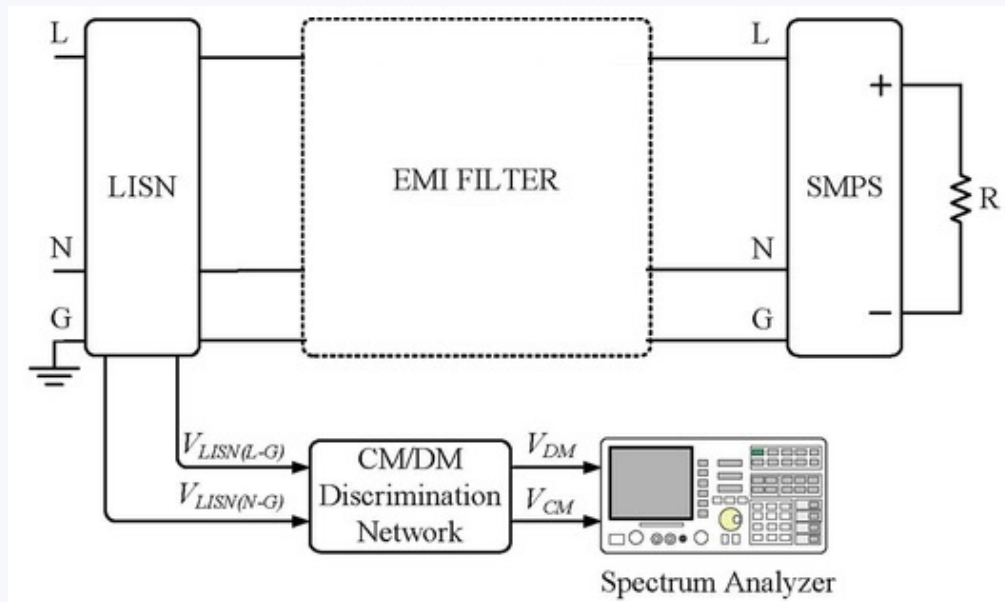
# Measurement of Conducted Emissions with LISNs (CM & DM)


- Spectrum analyser cannot distinguish between differential mode and common mode noise.
- CM/DM discrimination network can be placed between the LISN and the spectrum analyser to separate the differential mode voltage and the common mode energy.




K. Y. See, "Network for conducted EMI diagnosis," IEE Electron. Lett., vol. 35, no. 17, pp. 1446–1447, Aug. 1999.
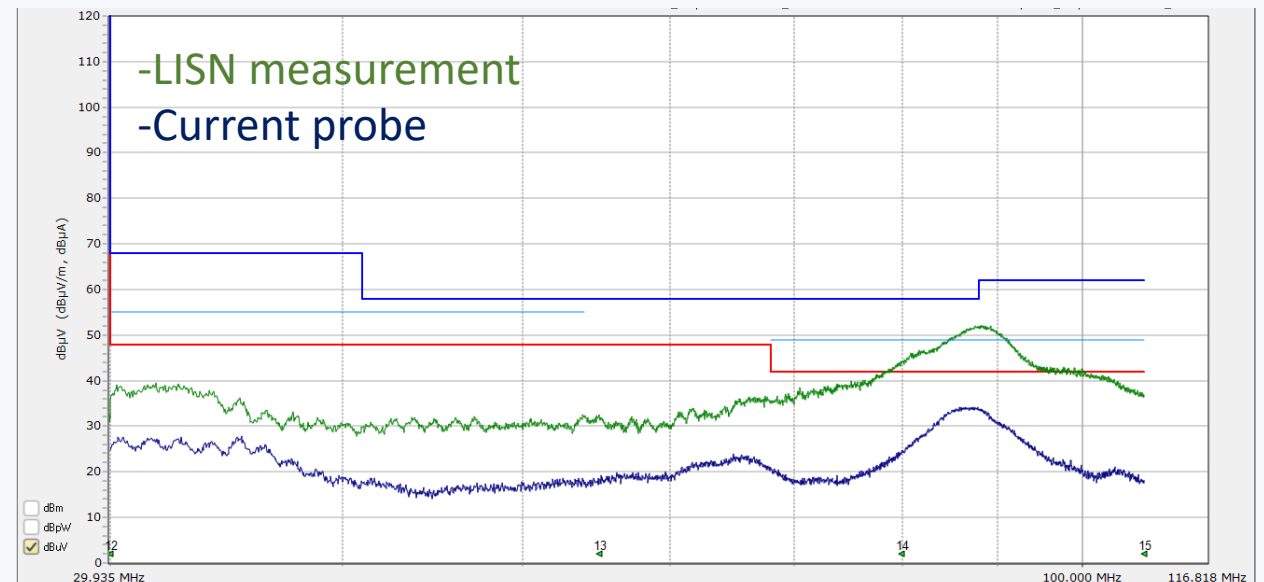
# Current Probe & LISN Measurement



- Current probe method and the voltage method yield very similar results in lower frequencies, below 5 MHz.
- Difference in results in higher frequencies, above 5MHz.



# Current Probe vs LISN Measurement

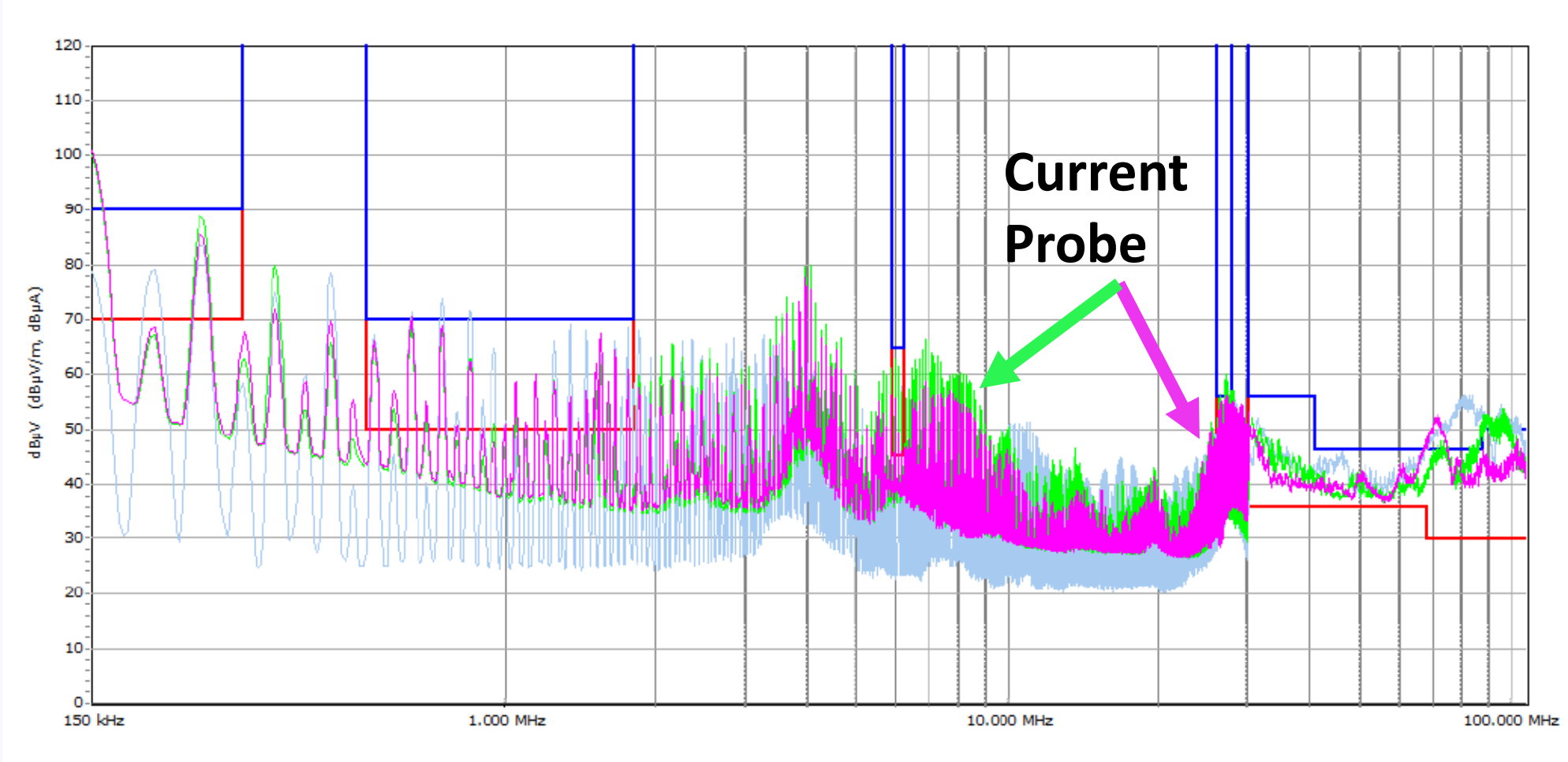

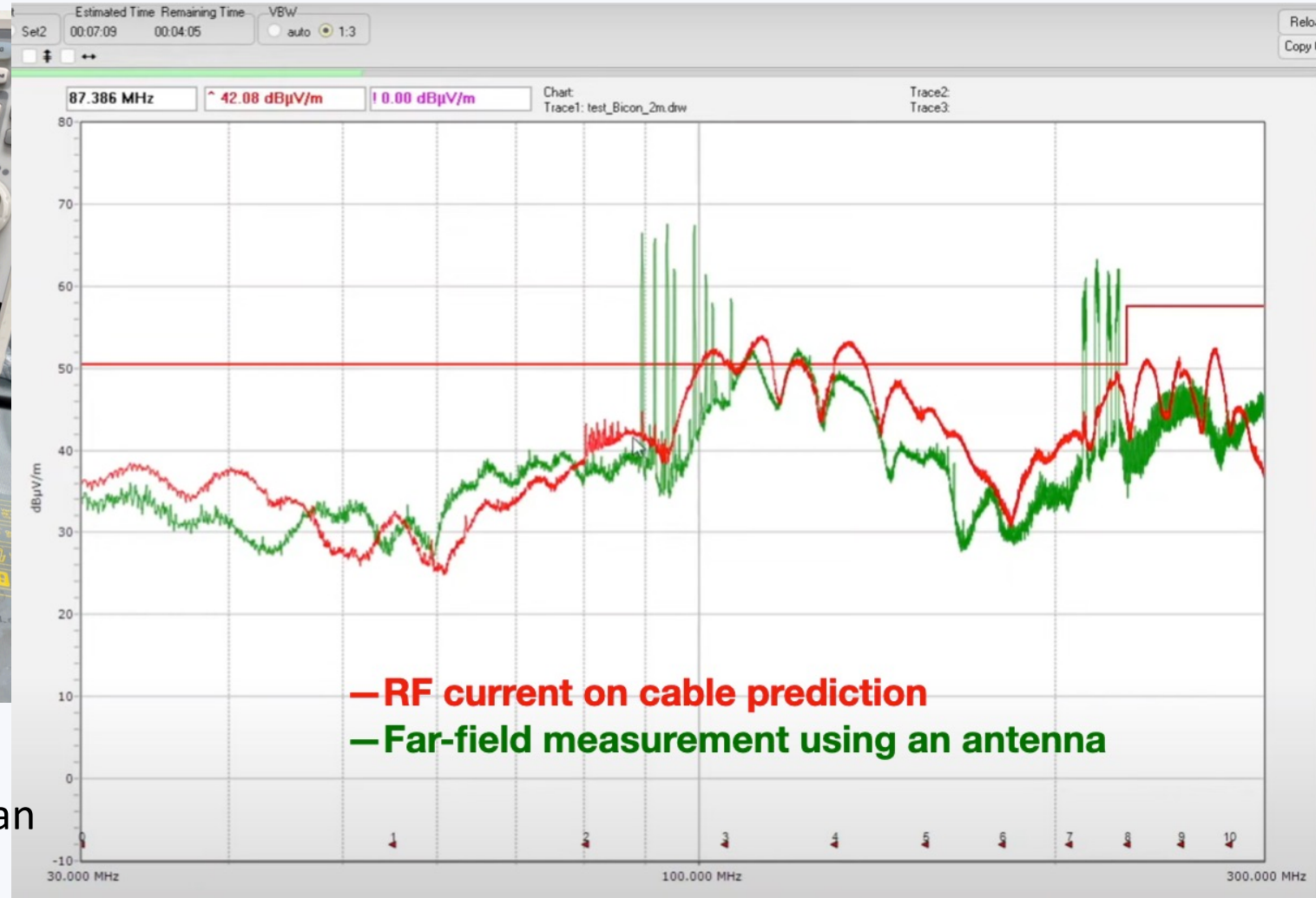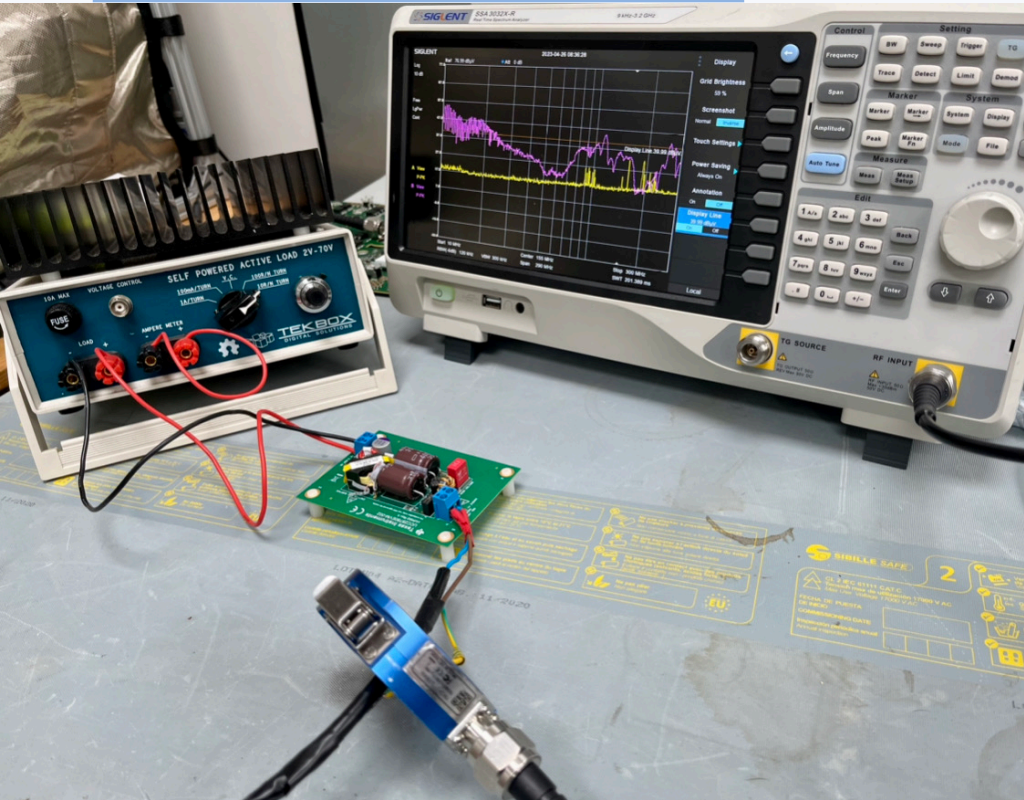
# Using Current Probe Results to Predict Far-field Emissions




- Using an RF current probe to measure common mode current, far-field emission can therefore be predicted to a good accuracy
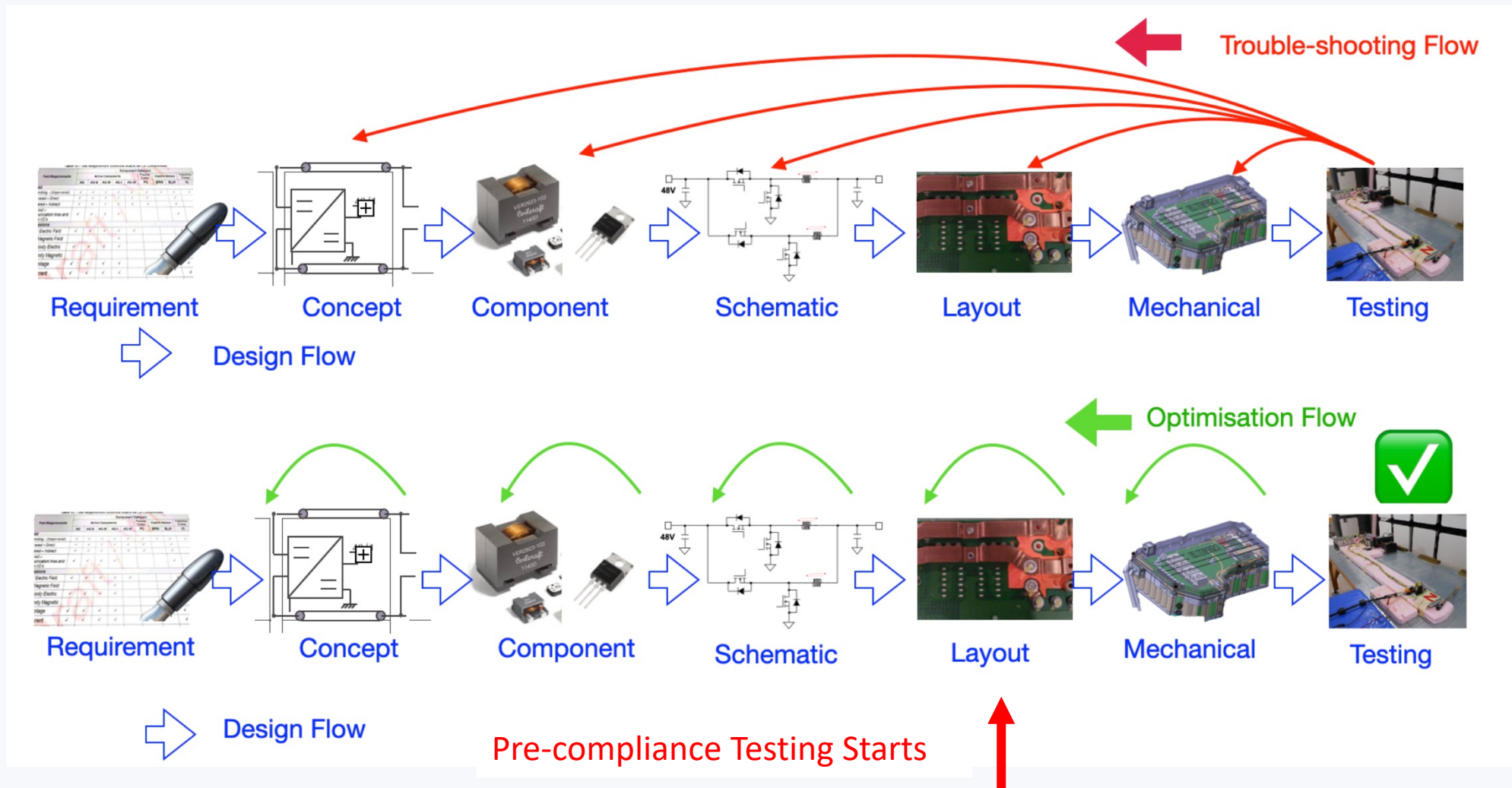
# Design Strategies – EMC Planning & Management



# Design Strategies – DC Link Design

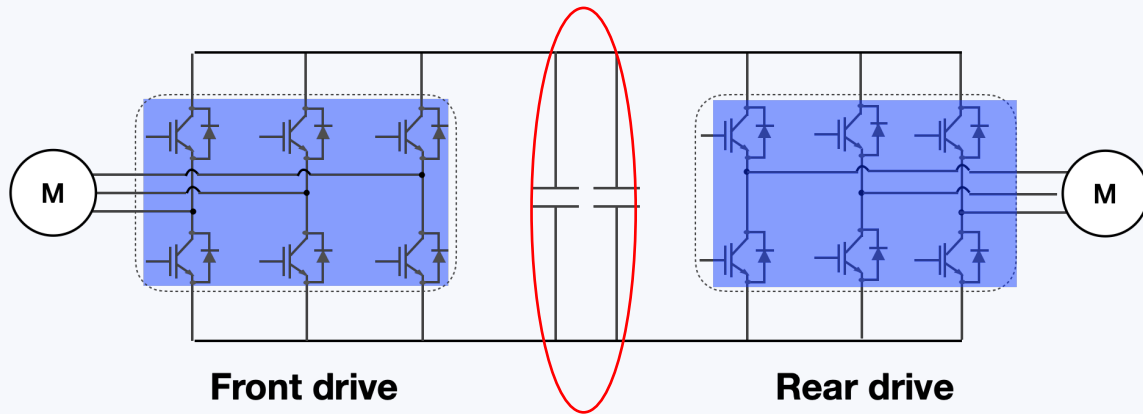

- Does my DC Link has the least impedance (i.e., the smallest loop that I could achieve)?




The DC link was on the top side board, and the switches were on the bottom.

# Design Strategies – Switching

Estimated 10 nH inductance introduced by the lead of the package.

|                         |               |
|-------------------------|---------------|
| <b>IRFP4468PbF</b>      |               |
| HEXFET® Power MOSFET    |               |
| $V_{DSS}$               | 100V          |
| $R_{DS(on)}$ typ.       | 2.0m $\Omega$ |
| $R_{DS(on)}$ max.       | 2.6m $\Omega$ |
| $I_D$ (Silicon Limited) | 290A          |
| $I_D$ (Package Limited) | 195A          |
| TO-247AC                |               |

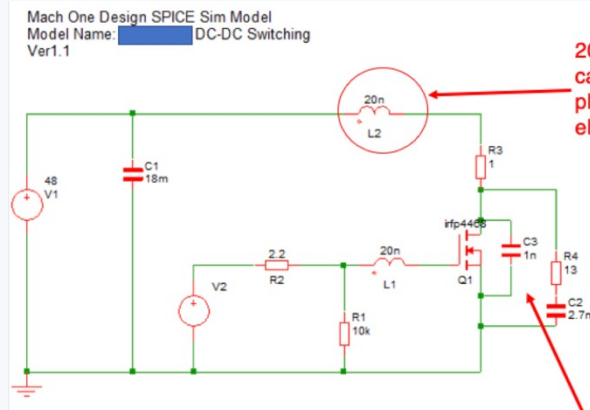Source: Infineon (International Rectifier)




20 nH loop inductance, including 10 nH caused by the long lead of the device plus 10 nH of PCB tracks to the electrolytic capacitor

1nF parasitic capacitor of the device based on its packaging and layout



Comments: We often prefer SPICE based simulation as it is quick to build, can run very fast and leads to good understanding of the circuit behavior. This is extremely useful for troubleshooting as can be seen later.

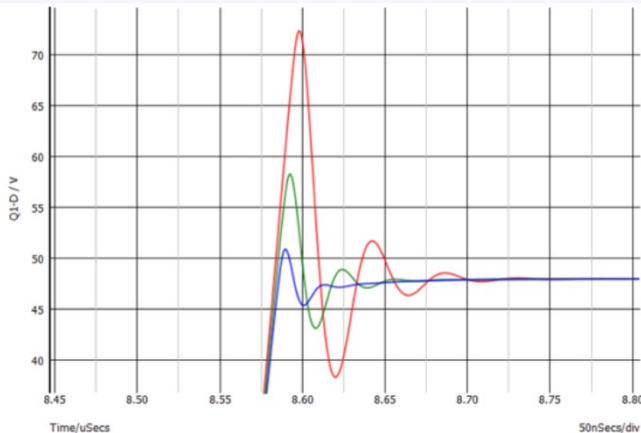- Through hole or SMD? - That is a question
- Soft switching or hard?
- Snubber?
- ZVS control?
- Spread spectrum or not?
- Covering the switch node with shielded inductor if applicable



Loop inductance L2  
 — 20 nH  
 — 10 nH  
 — 5 nH



Unshielded - Not suitable

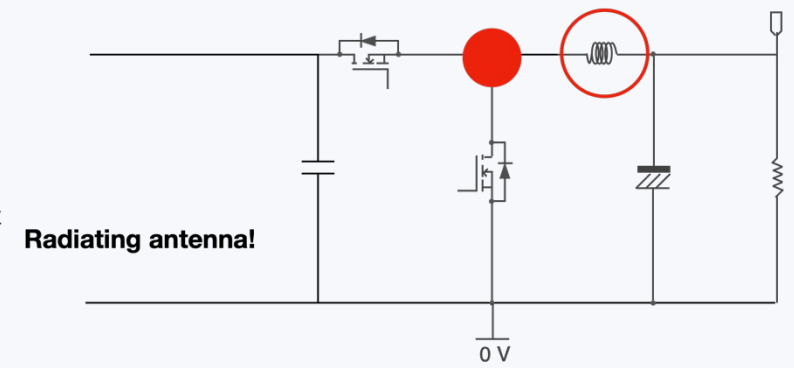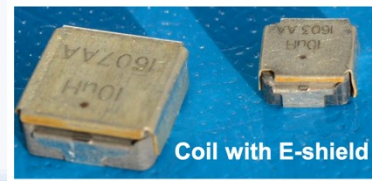

Use shielded inductor to shield the Switch Node





# Switching Frequency and Speed

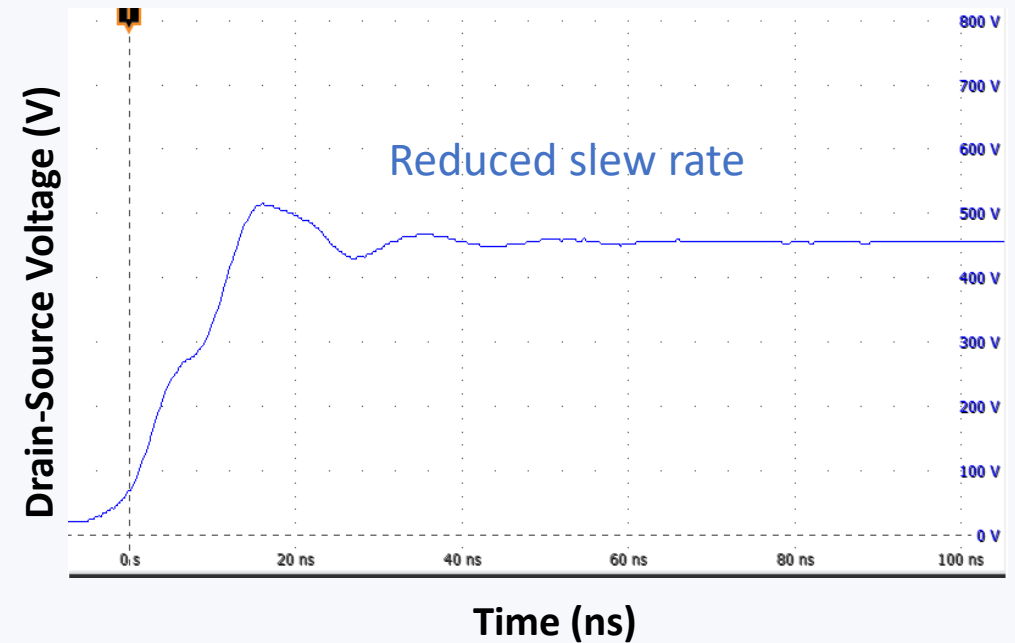
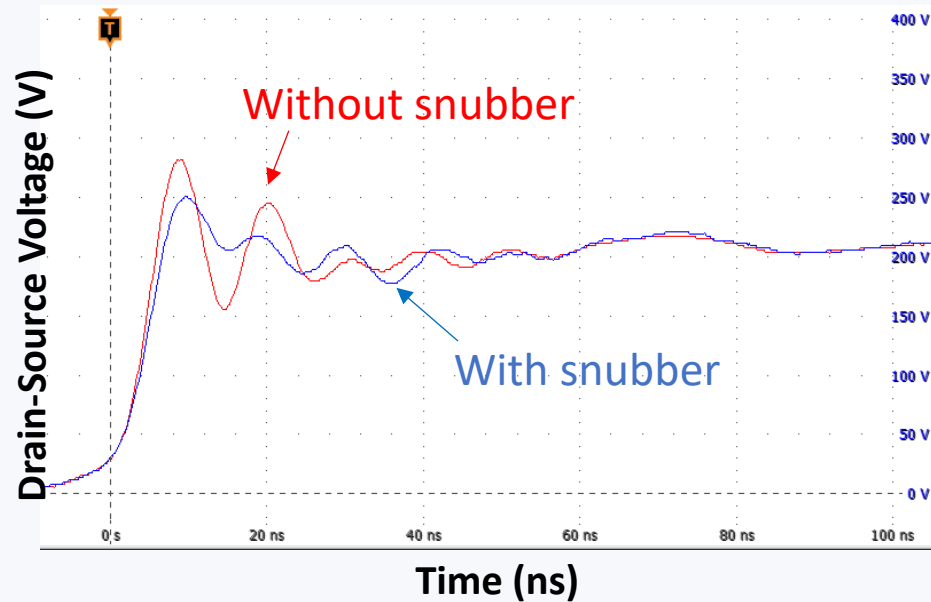


- Snubber damps the resonance of parasitic components
- Reduced ringing impacts EMI at the ringing frequency
- Spike killer noise suppression device (very lossy).
- Reduced slew rates impact EMI roll-off in the 30- to 200MHz band → effects efficiency

# Design Strategies – Filtering

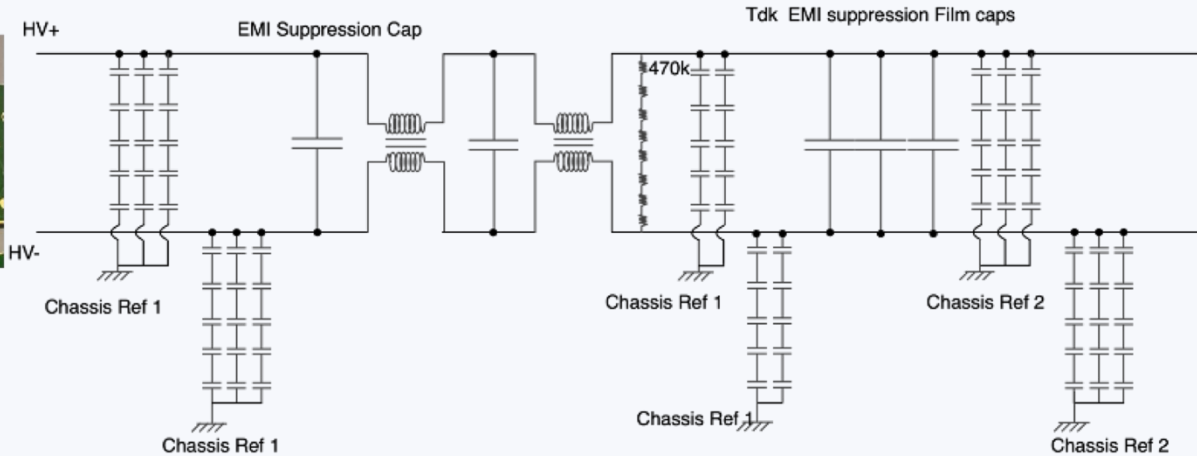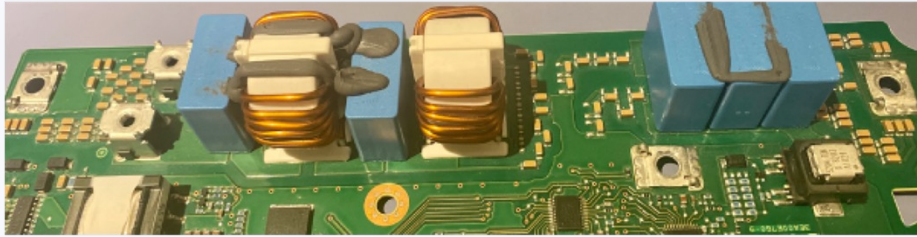


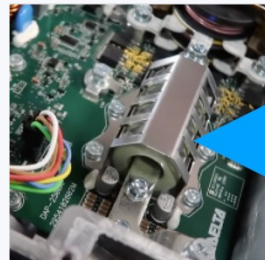
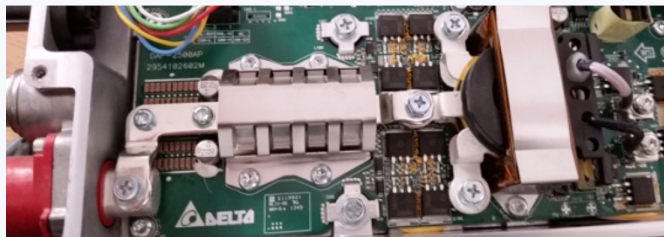
The input filter configuration in a DC-DC module used in Audi Eton - HV, current rating is not high.





It is easy to make a single-turn two cores (perhaps four cores) configuration. Put positive and negative on adjacent layers on the board, you can use wide track or plane and then it's a bit like winding a bifilar winding, all the magnetic field then flows in the small gap between the two planes and the only remaining flux is the high frequency common mode noise, and all you need to do is to put a core through the board or around the board.

The output filter in a DC-DC module used in Tesla Model S - LV, current is more than 200 Amps

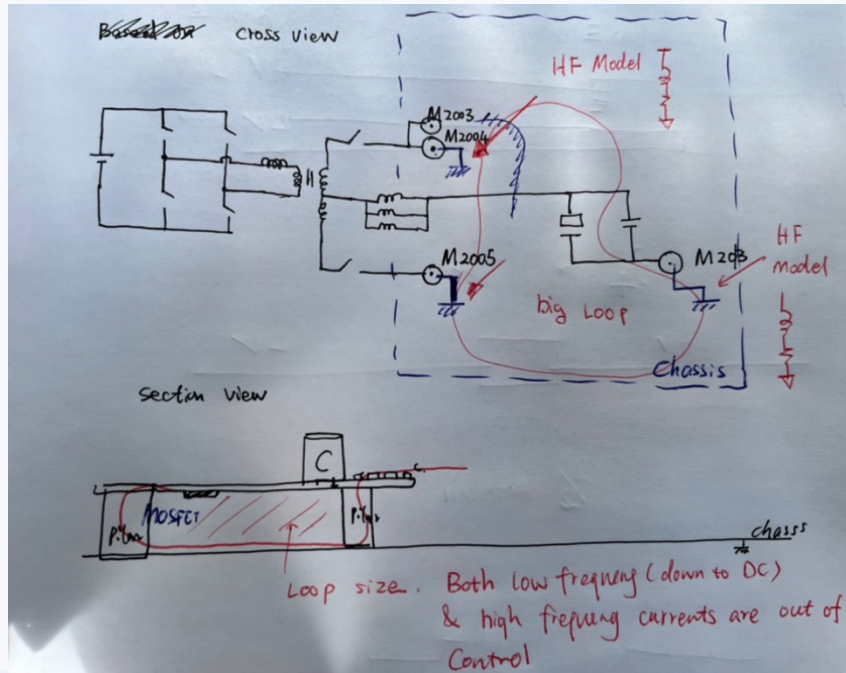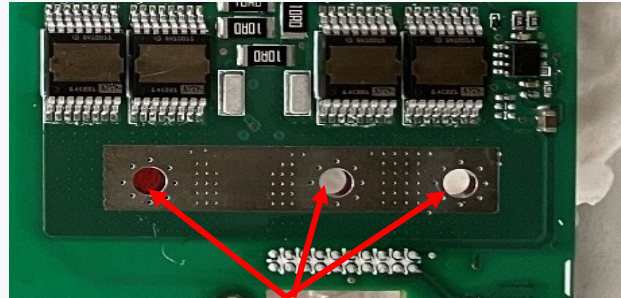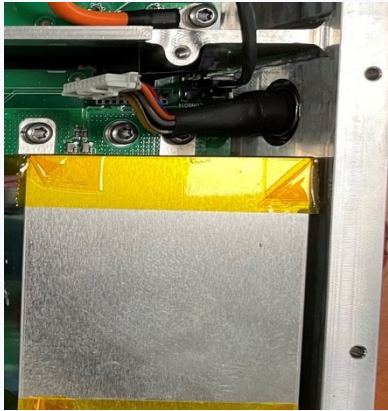
# Design Strategies – Grounding and Shielding



A seam is just another aperture

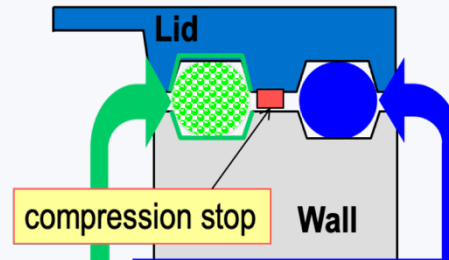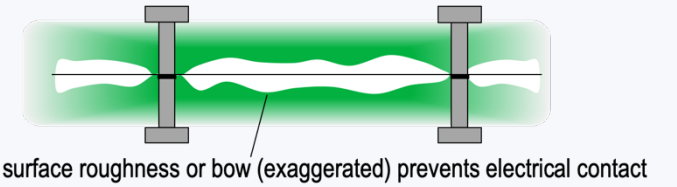

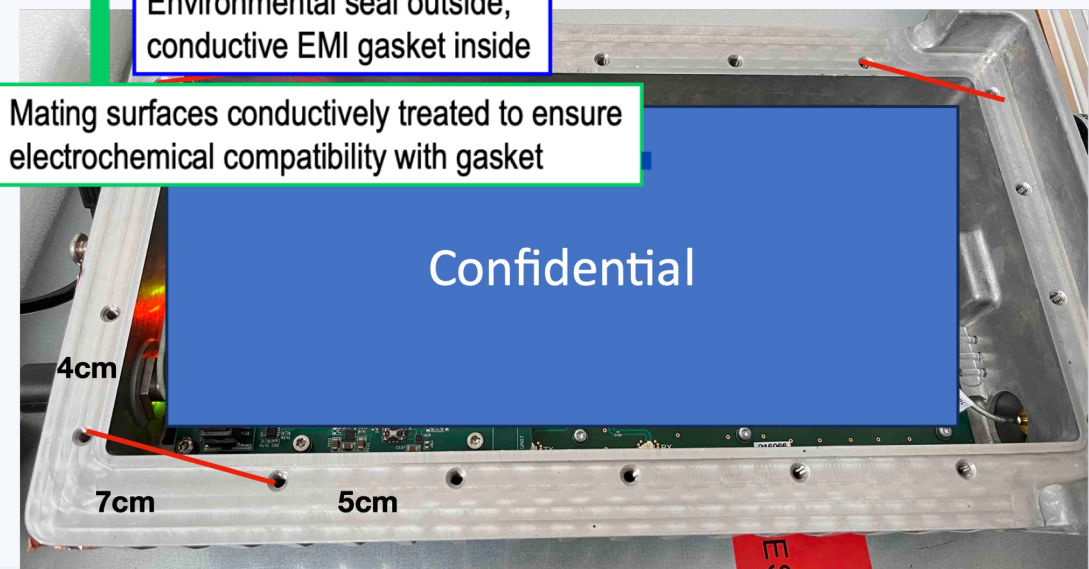Mating surfaces conductively treated to ensure electrochemical compatibility with gasket



# Design Strategies – Active Filtering


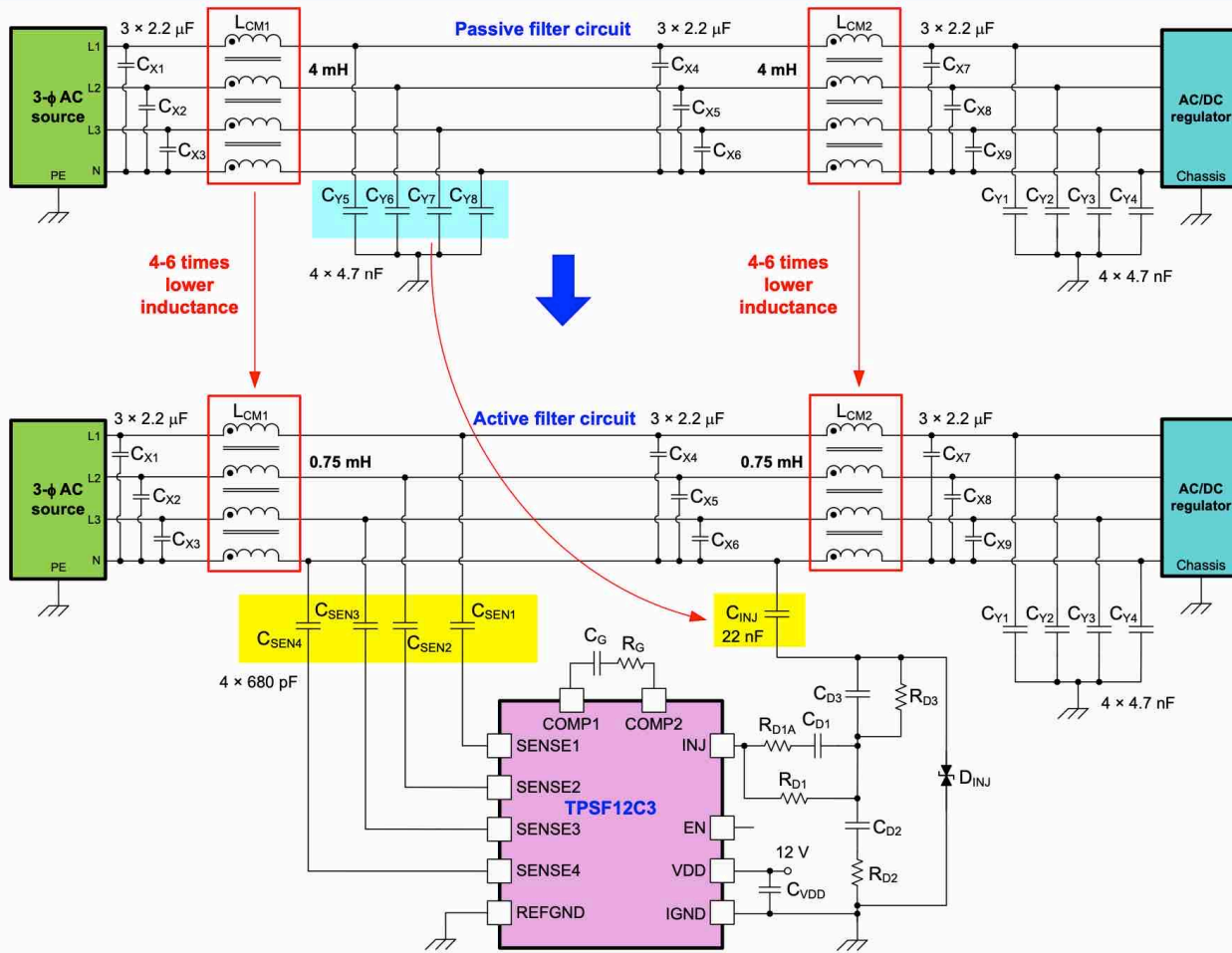


Figure 1-1. Three-Phase, Four-Wire Passive and Active Filter Schematics

Source: Texas instruments,

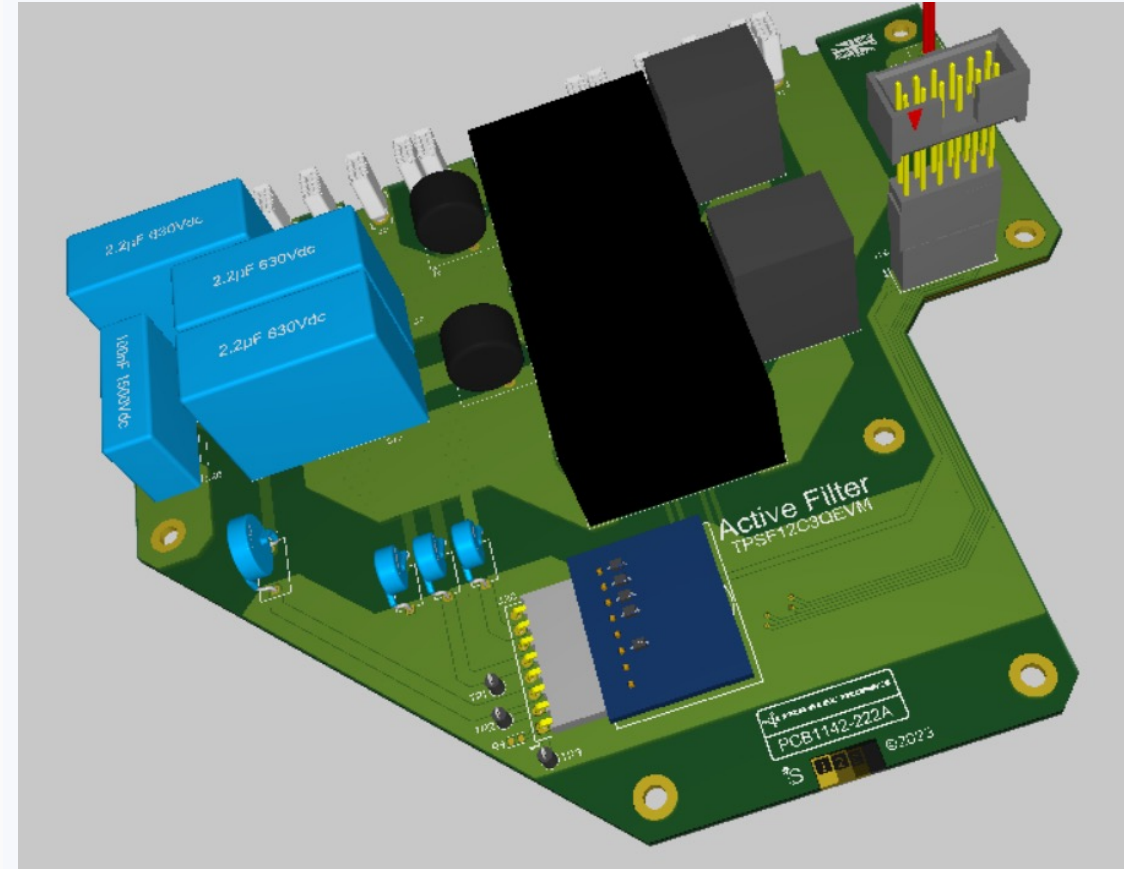


# Case Study: EMI Reduction on the HV Line

Since unshielded cables were used on the HV line, the focus was to design a multi-stage front end filter


Improves emissions in the FM band

Improves low frequency performance


Improves high frequency performance

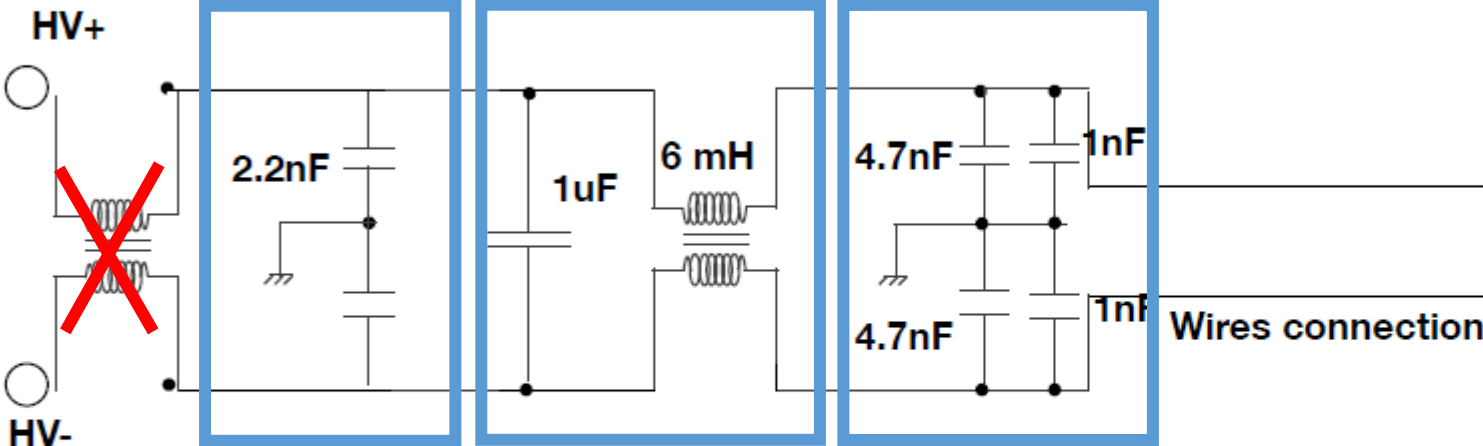



HV power PCB

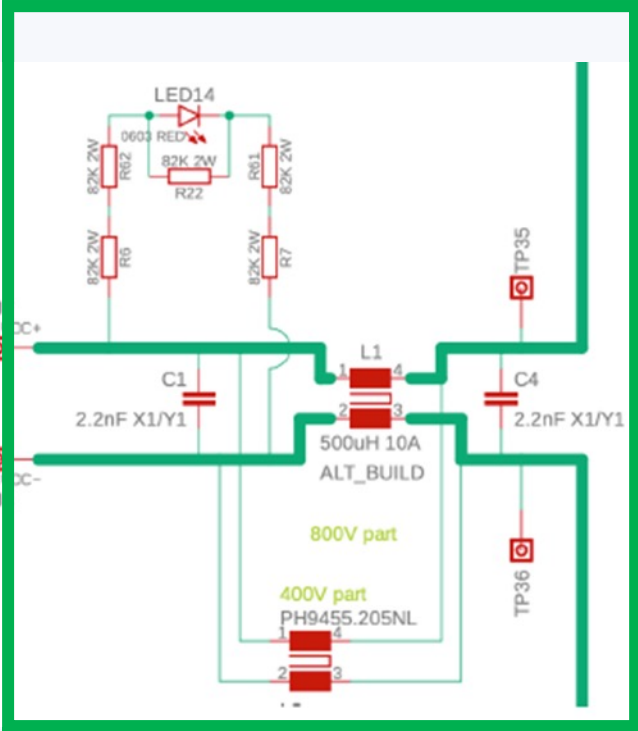



# Design a Multi-stage Filter PCB

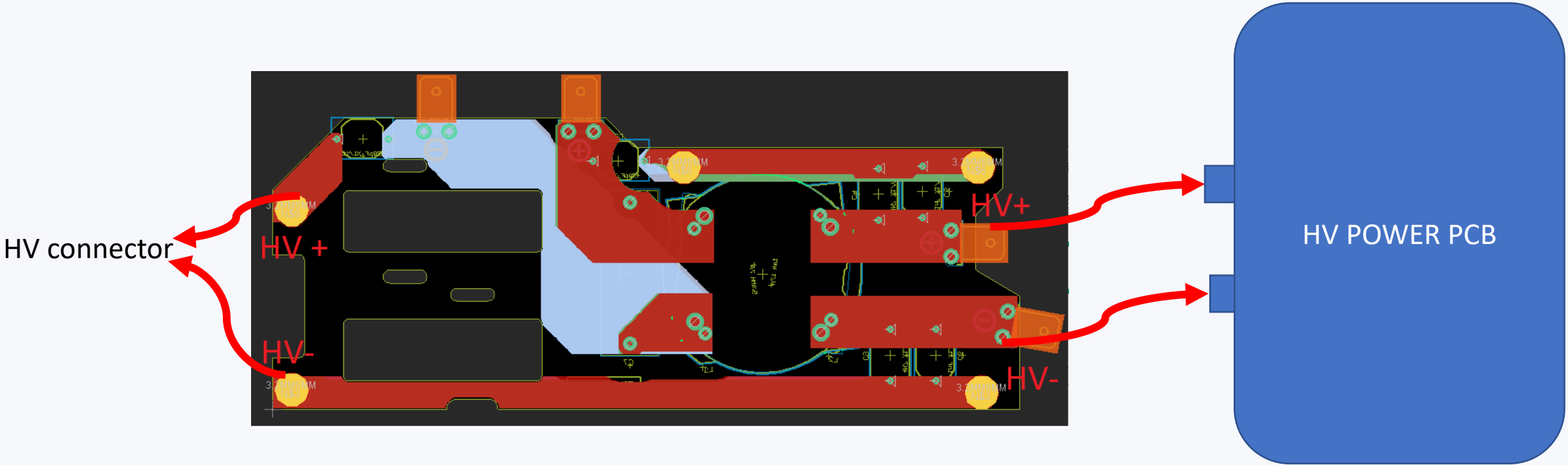
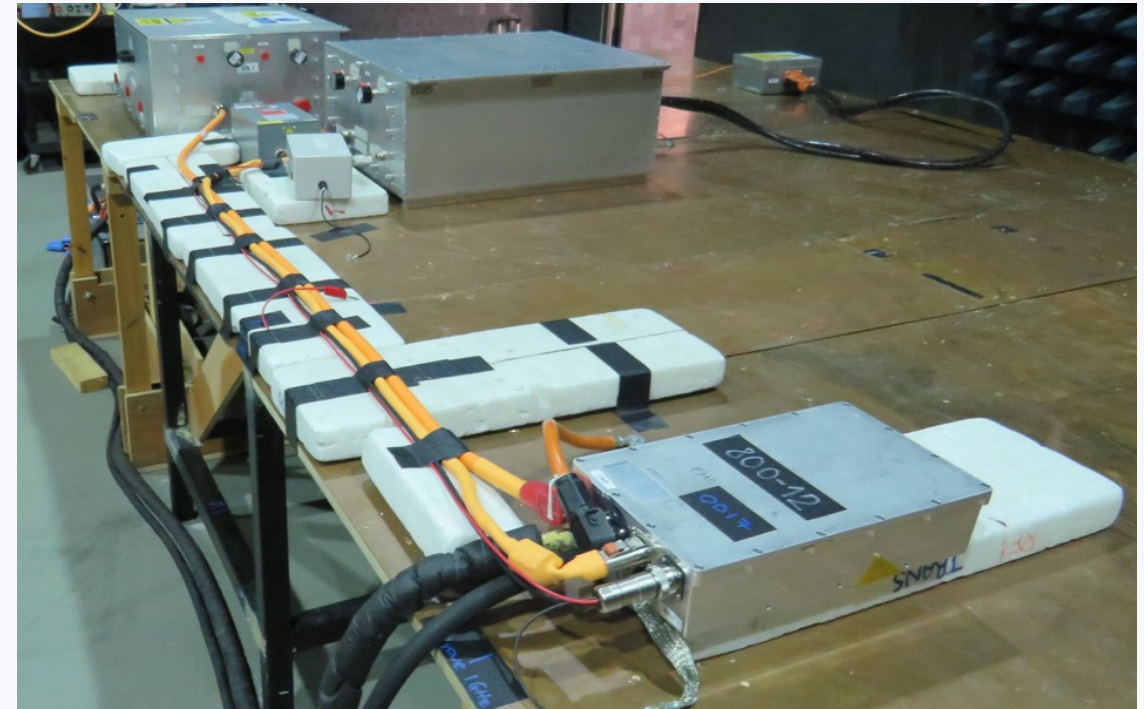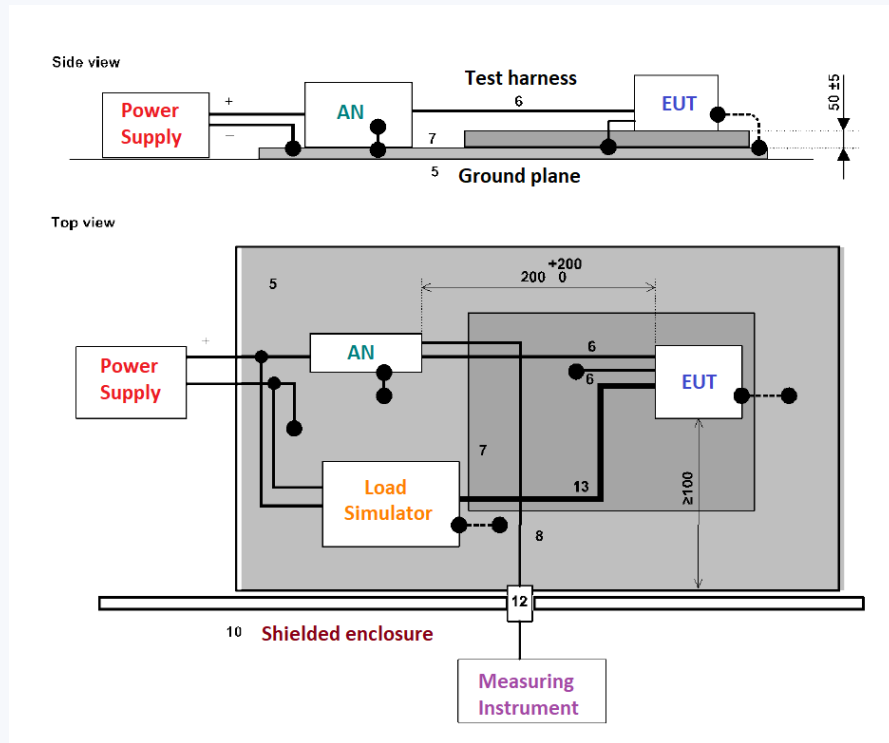
# Chamber EMC Testing: Conducted Emissions



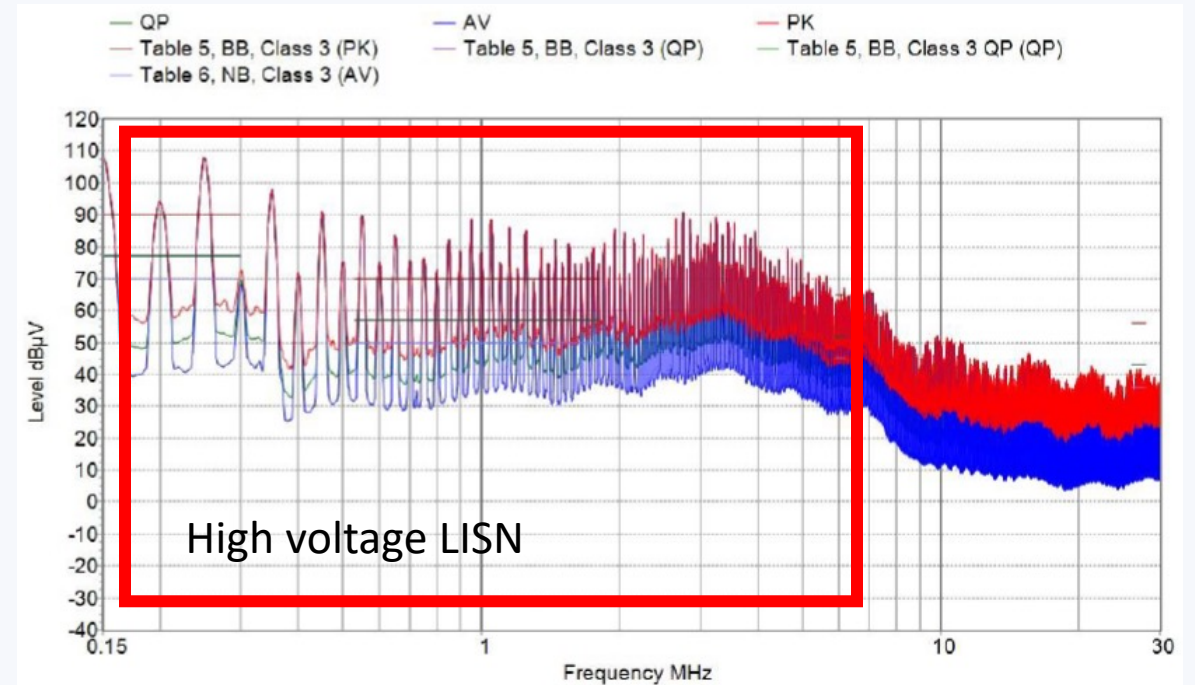
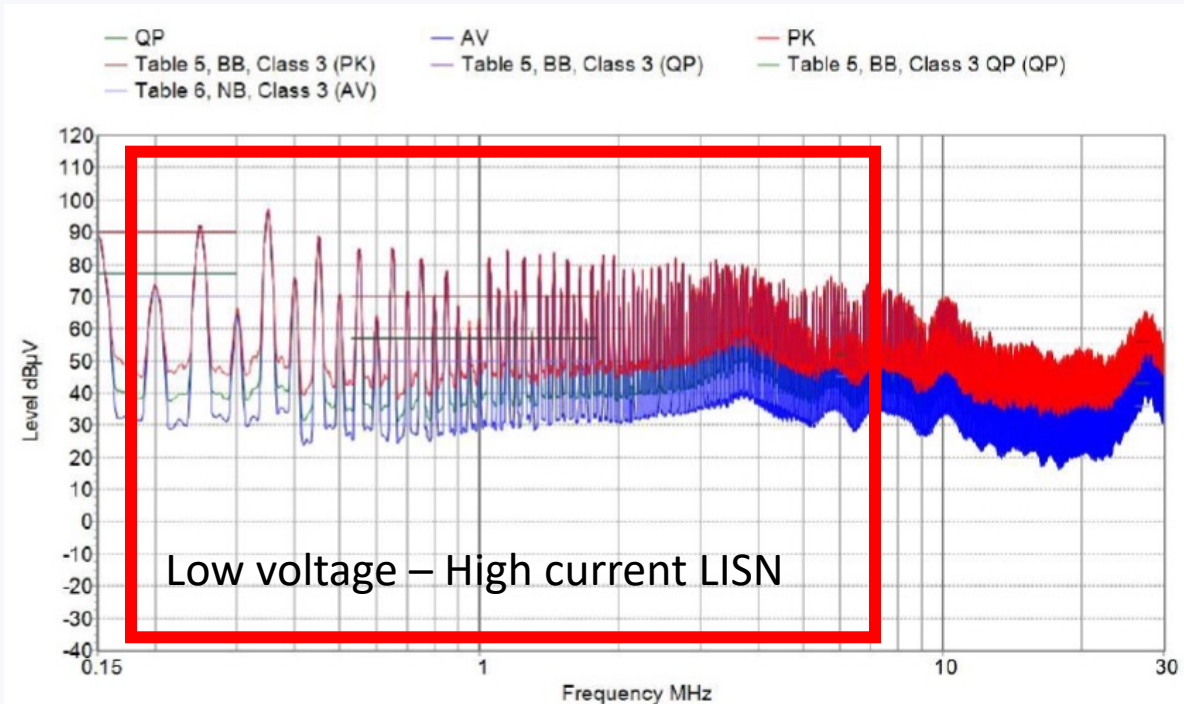
# Conducted emissions analysis: the HV Line



Switching frequency of the converter (50kHz) and its harmonics are the main frequency contents in the low frequency band



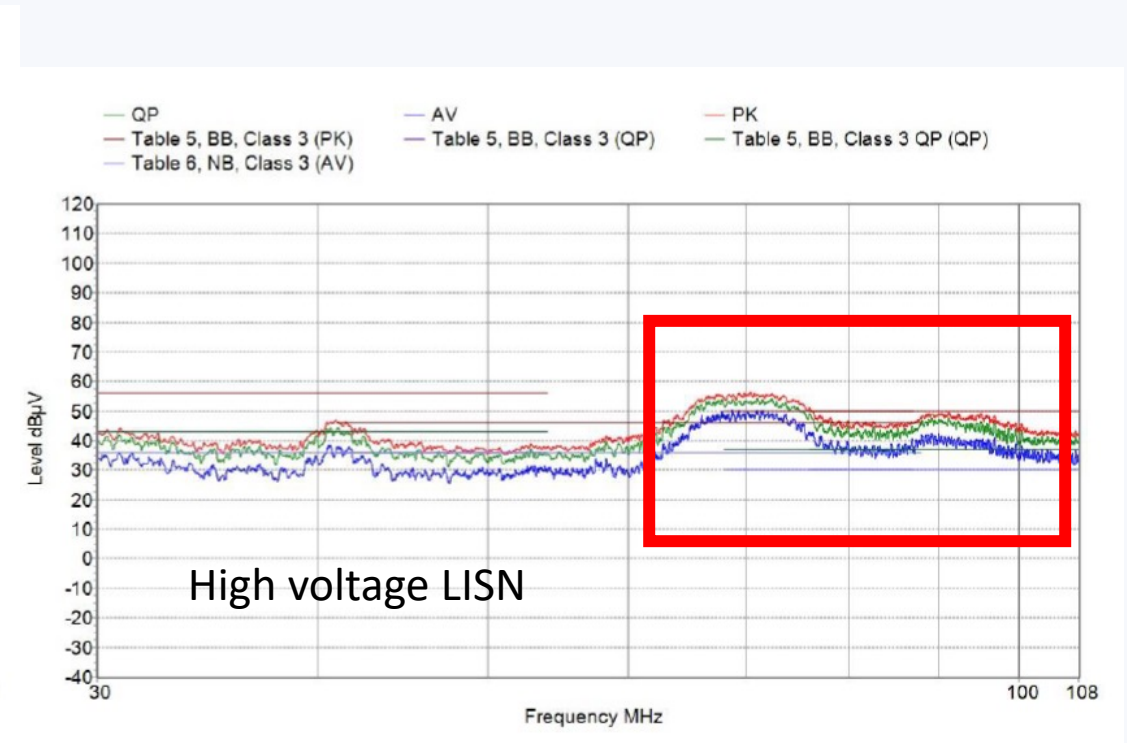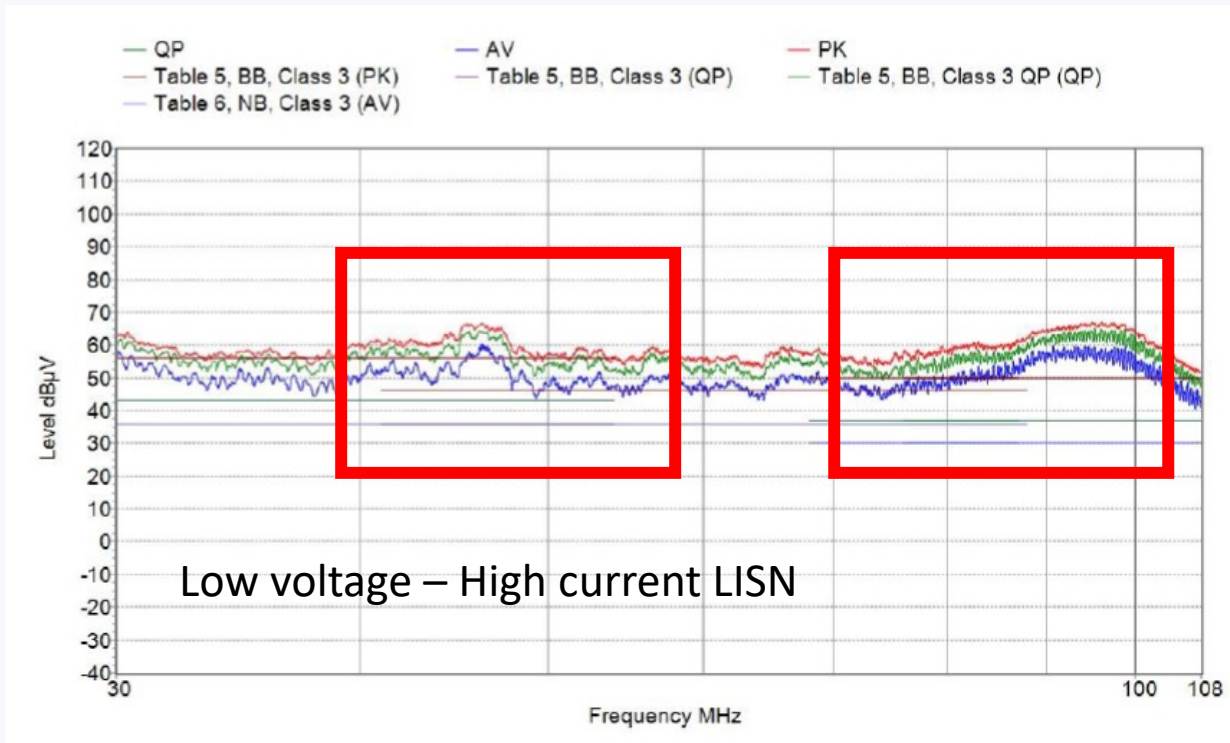
# Conducted emissions analysis: the HV Line




The conducted noise in this region will cause radiated emissions issue as the cables act as antennas.

# Improved Result: the HV Line

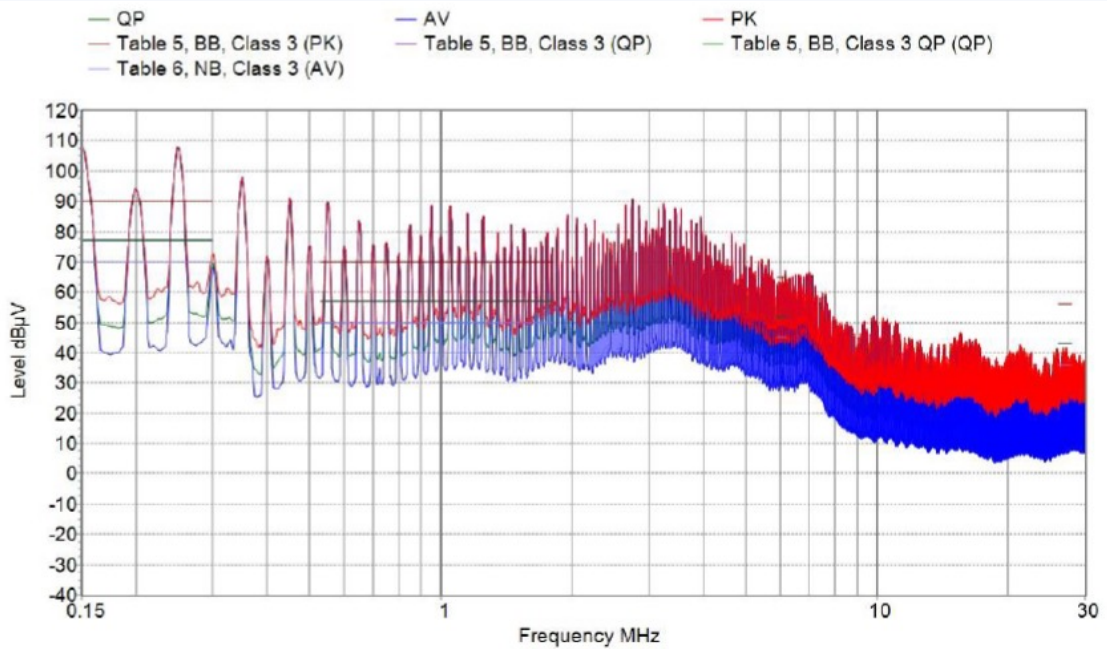


Without HV filter

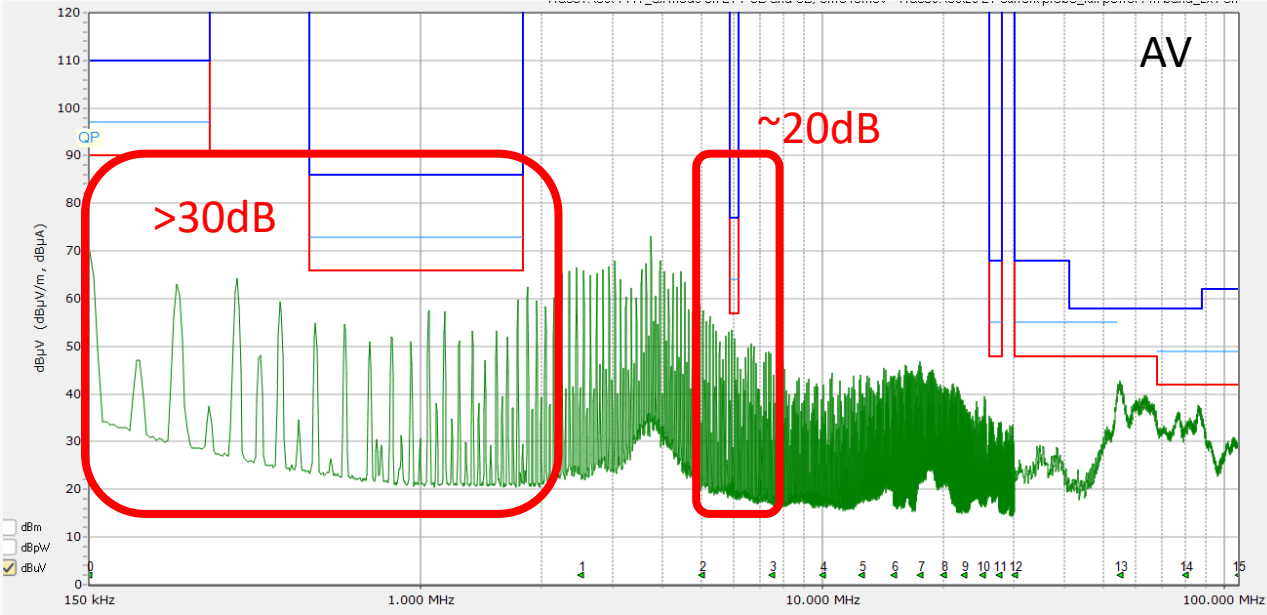

With HV filter
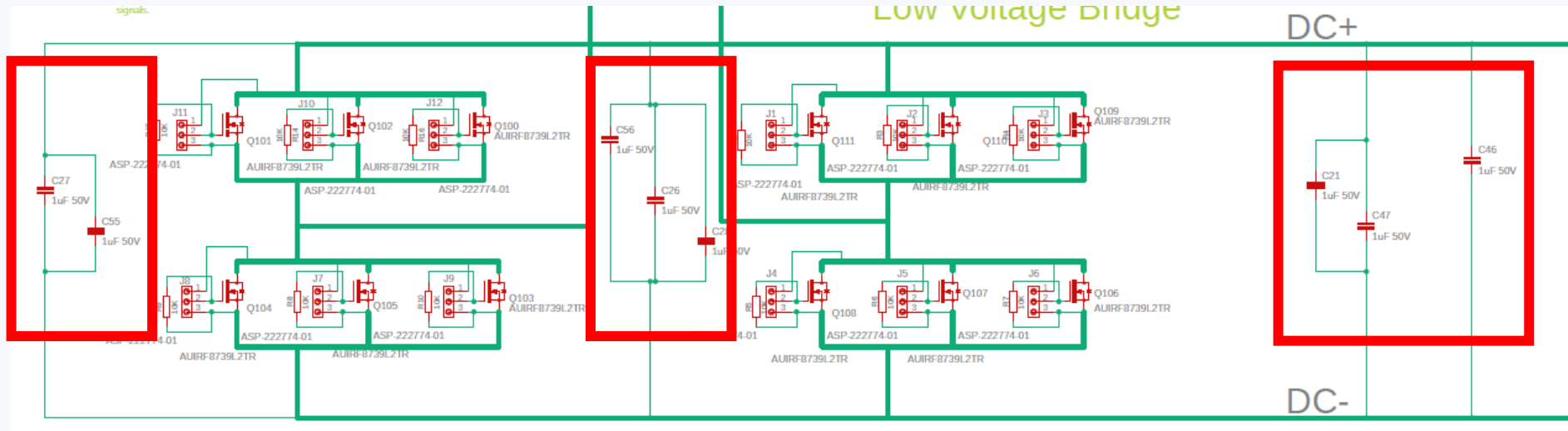
# EMI Reductions on the LV Line



- Due to very high current on the LV line, we could only apply capacitors between the LV rails and the vehicle chassis.
- The key is to limit the impedance caused by the connections.
- Parallel MOSFETs



- 3x 1μF capacitors for each half bridge

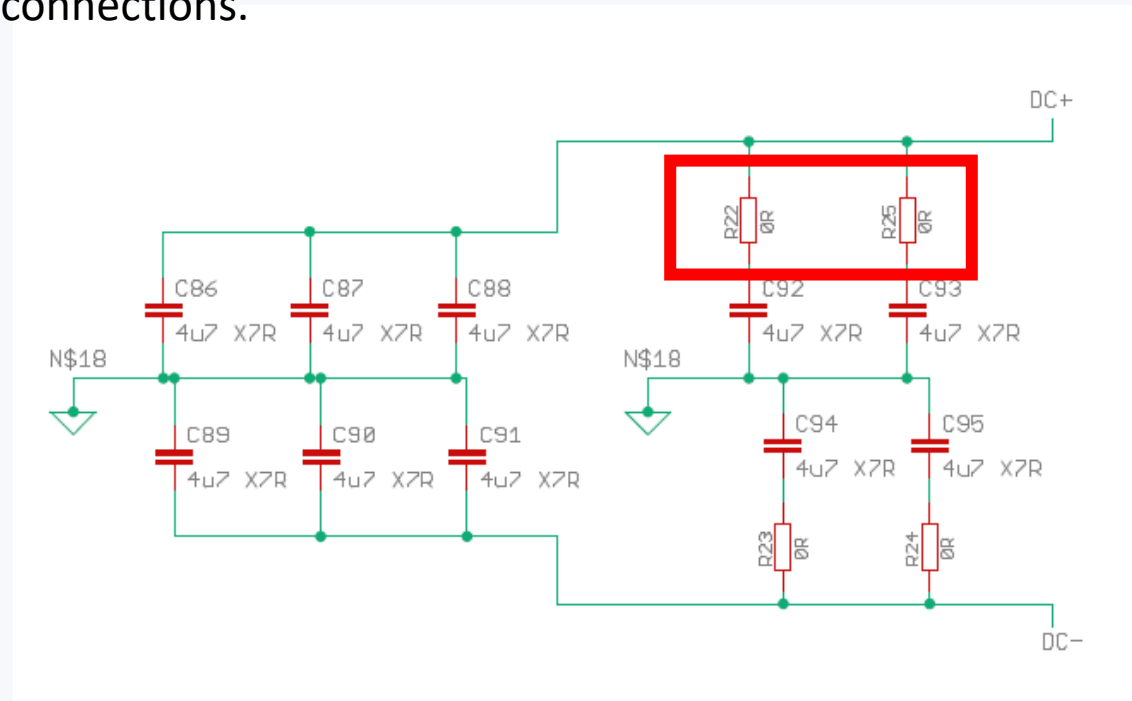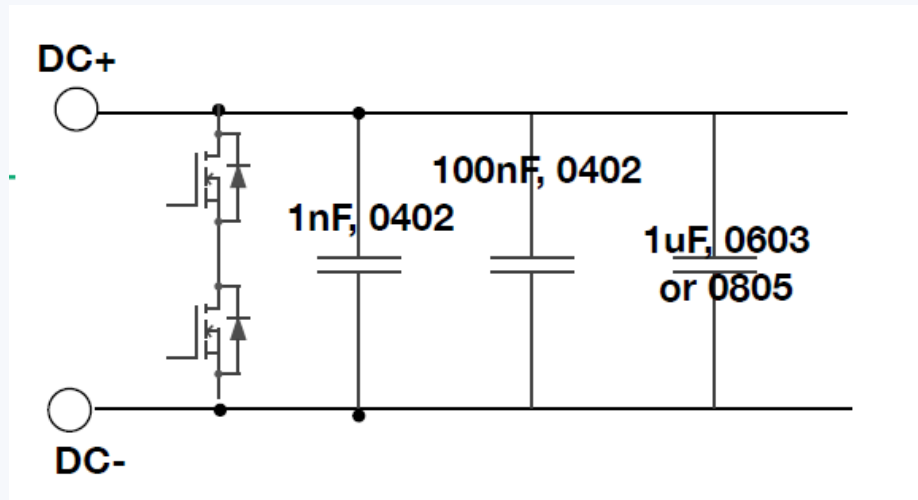
# EMI Reductions on the LV Line

- Due to very high current on the LV line, we could only apply capacitors between the LV rails and the vehicle chassis.
- The key is to limit the impedance caused by the connections.
- Parallel MOSFETs




- Use low ESL and ESR capacitors
- MLCC capacitor bank → Cover wide frequency band
- Avoid resonance → Damping
- Parasitic components increase with package size

# Improved Result: LV Line/High current

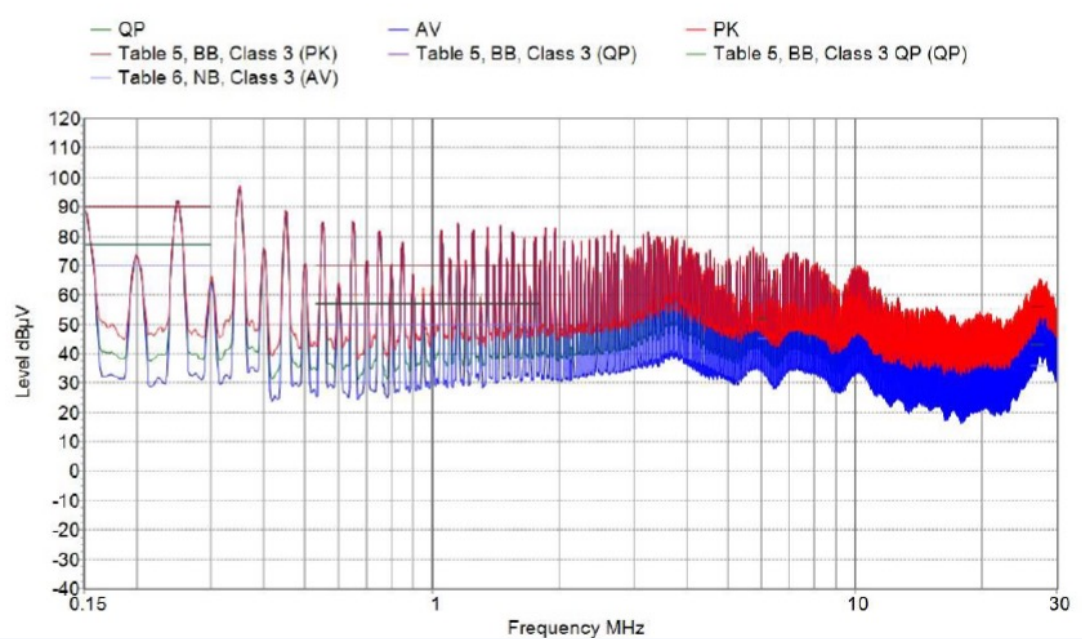


Before

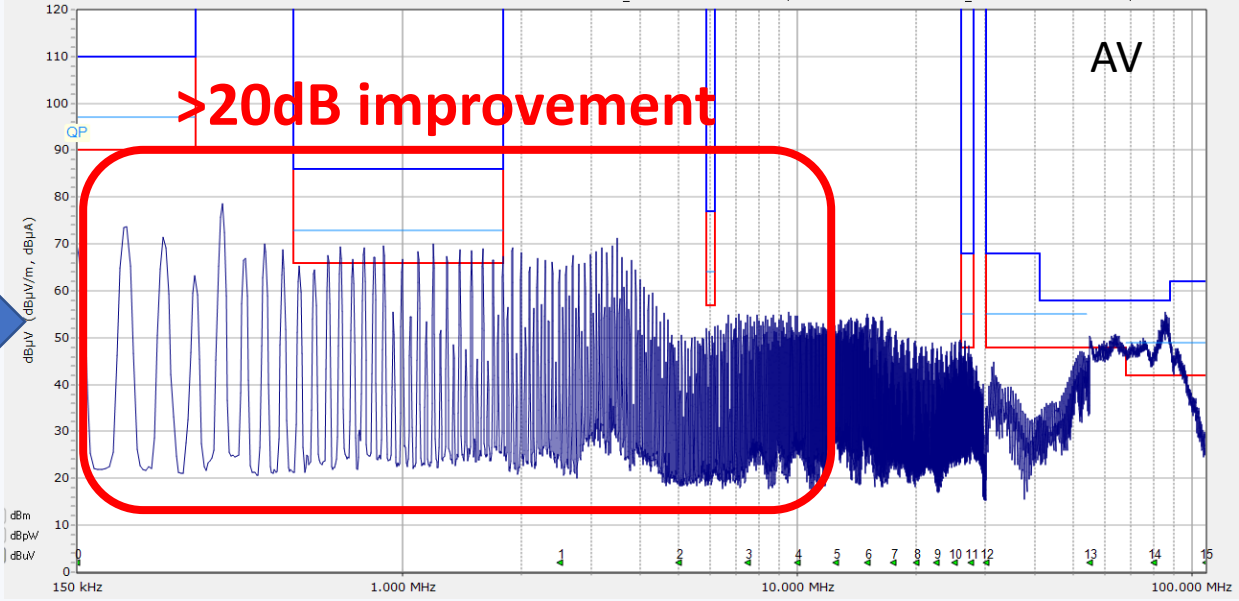


After

# Software Switching Techniques: HV & LV Lines




LV

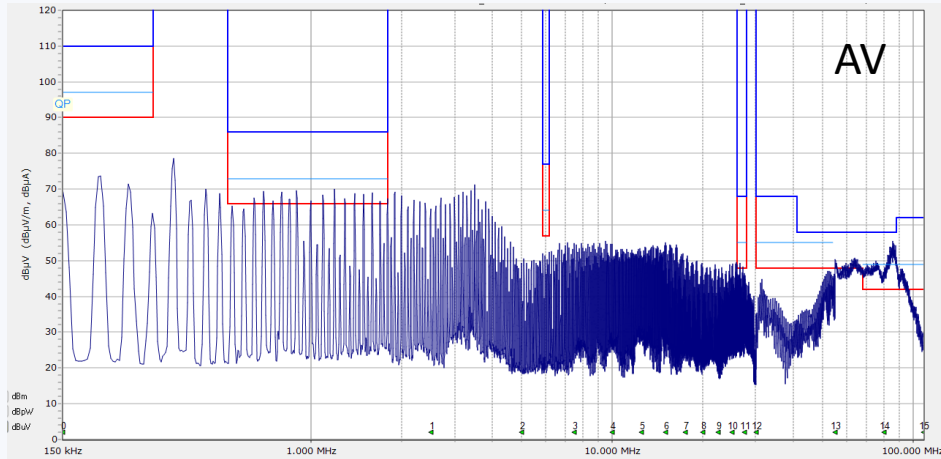

HV

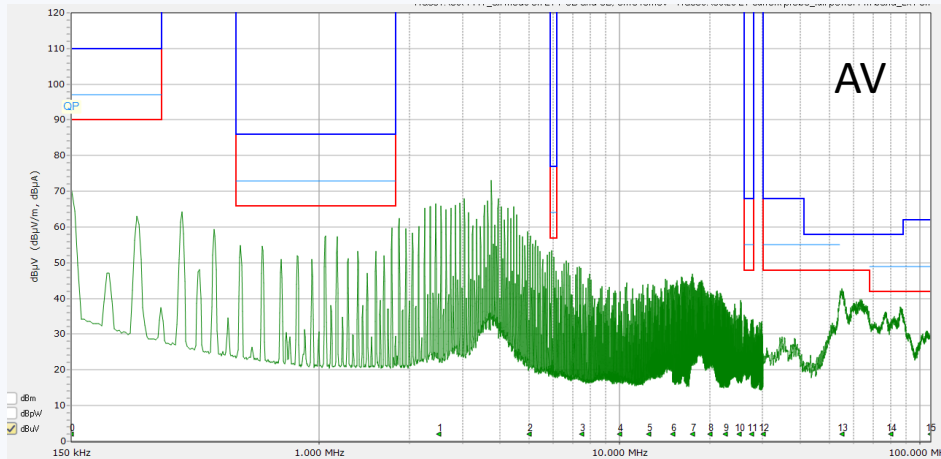

Before

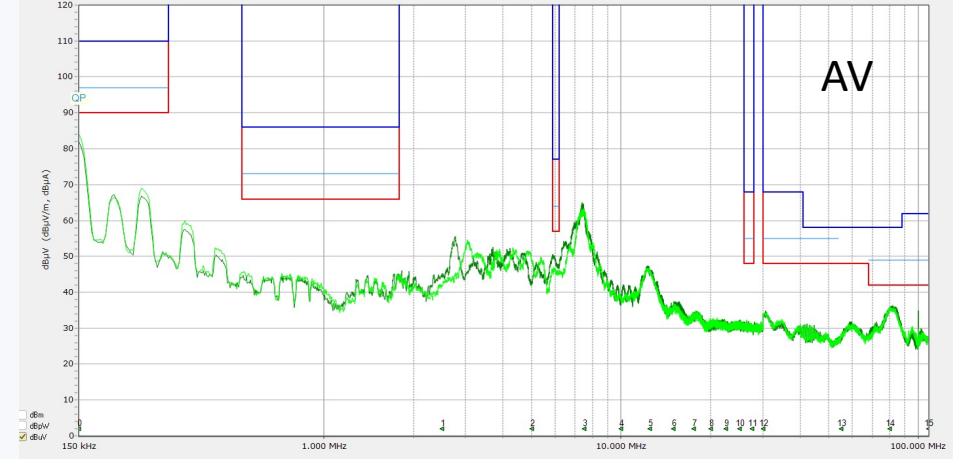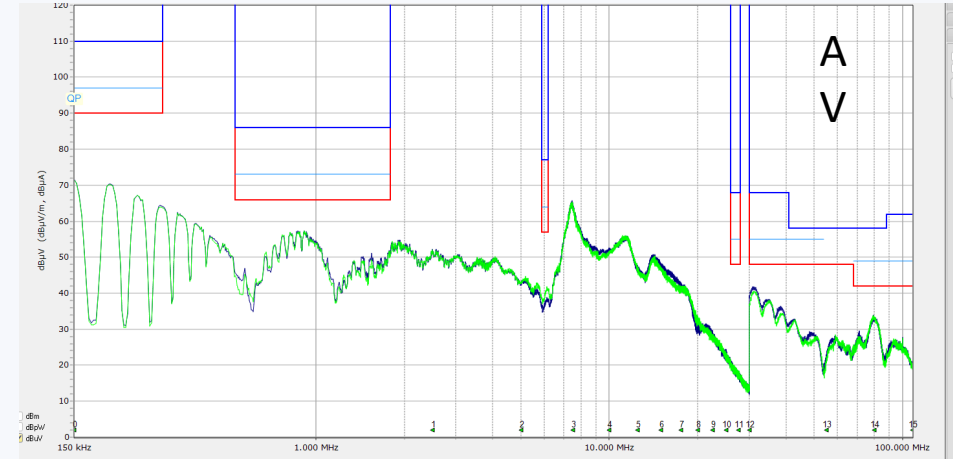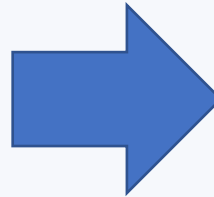


After

# PCB design considerations
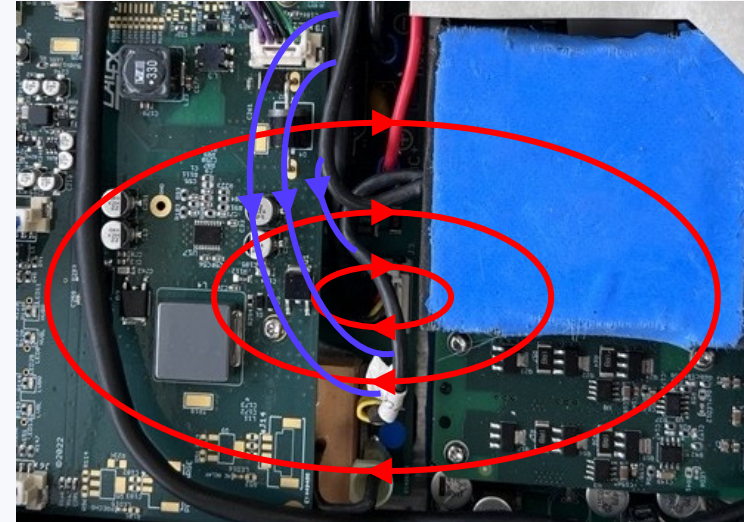
## 1. PCB design

- Select components and circuits with EMI in mind
- Design and enforce the ground system at the product definition stage
- Identify and label high di/dt circuits
- Component placement
- Careful PCB layout
- Minimise surface areas of nodes with high dv/dt



## 2. Cables



- Conducted path through cabling
- Cables can radiate



Pigtails here are a bad idea

## 3. Filters
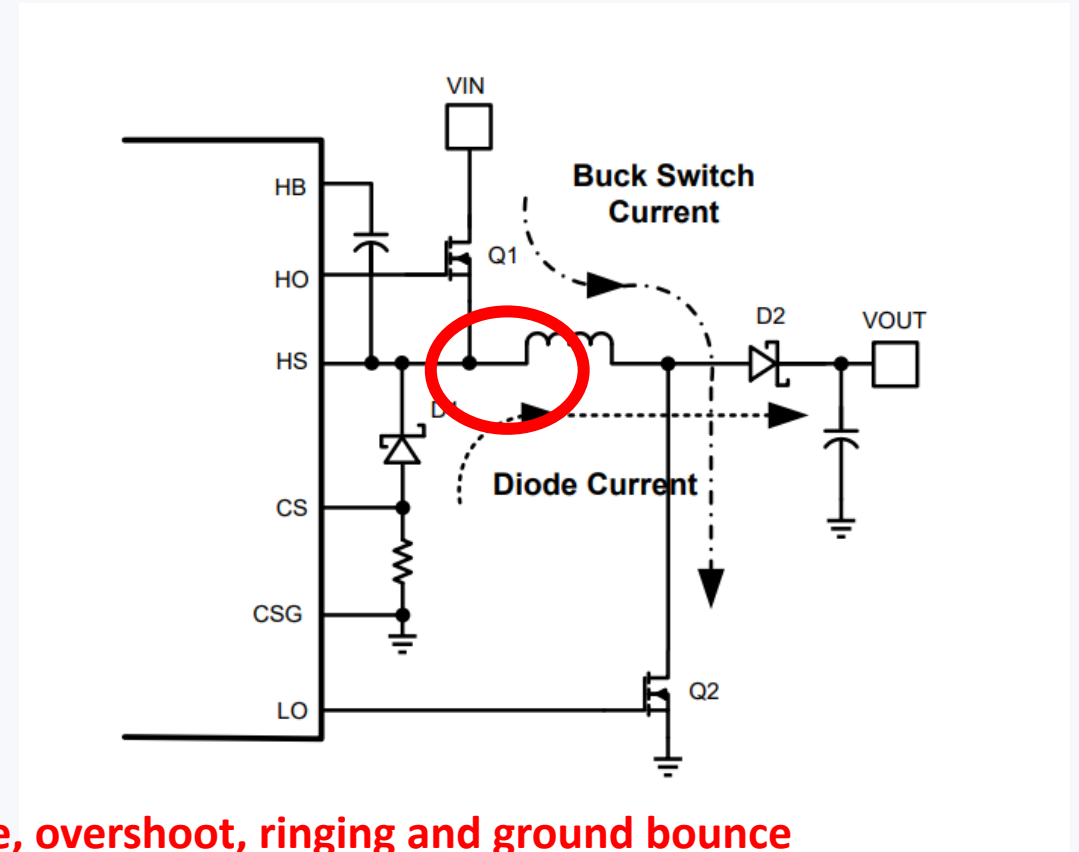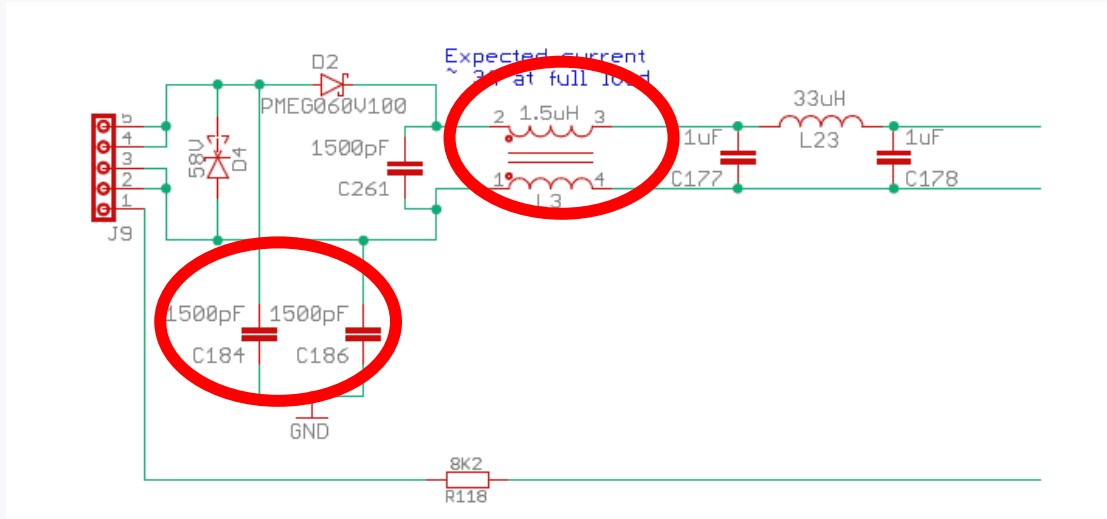
# Identify Critical Loops with High di/dt Currents




- Pinpoint high slew rate current (high di/dt) loops
- Identify layout-induced parasitic inductance that cause **noise, overshoot, ringing and ground bounce**
- “Shielded” inductor still emits significant EMI!
- Long connections from capacitors to chassis GND
- Improve buck-boost converter layout
- Replace common mode choke





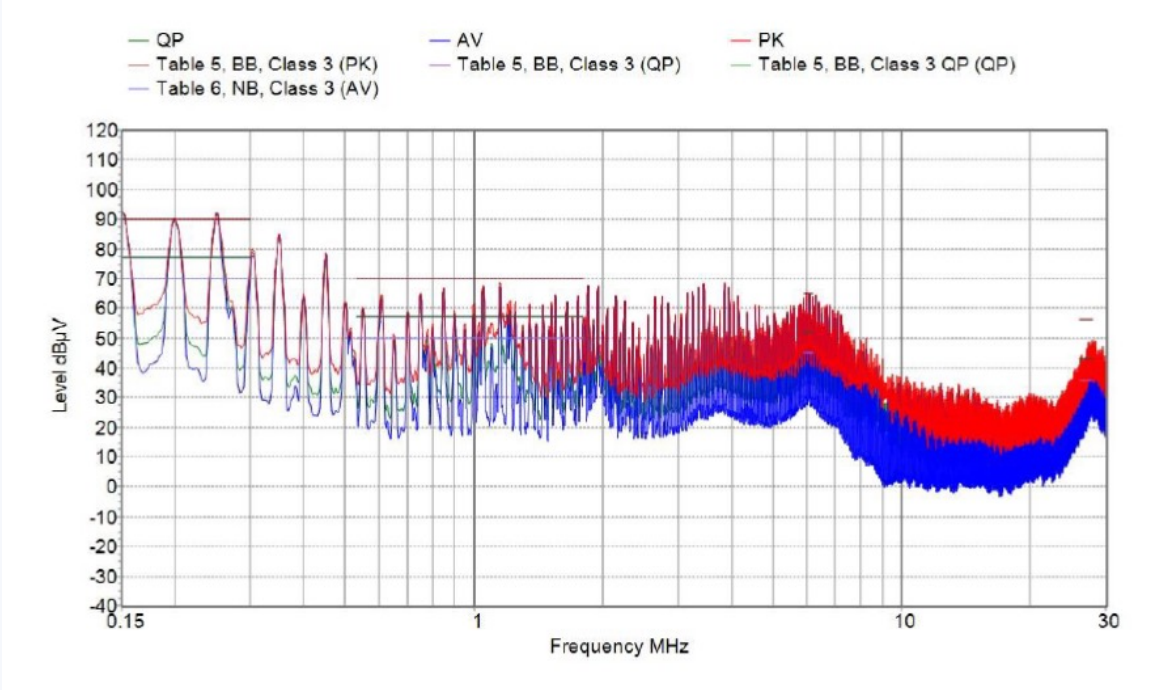
# Improved Result: Low Voltage/Low Current Line




Before


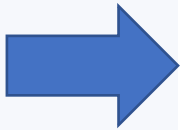


After



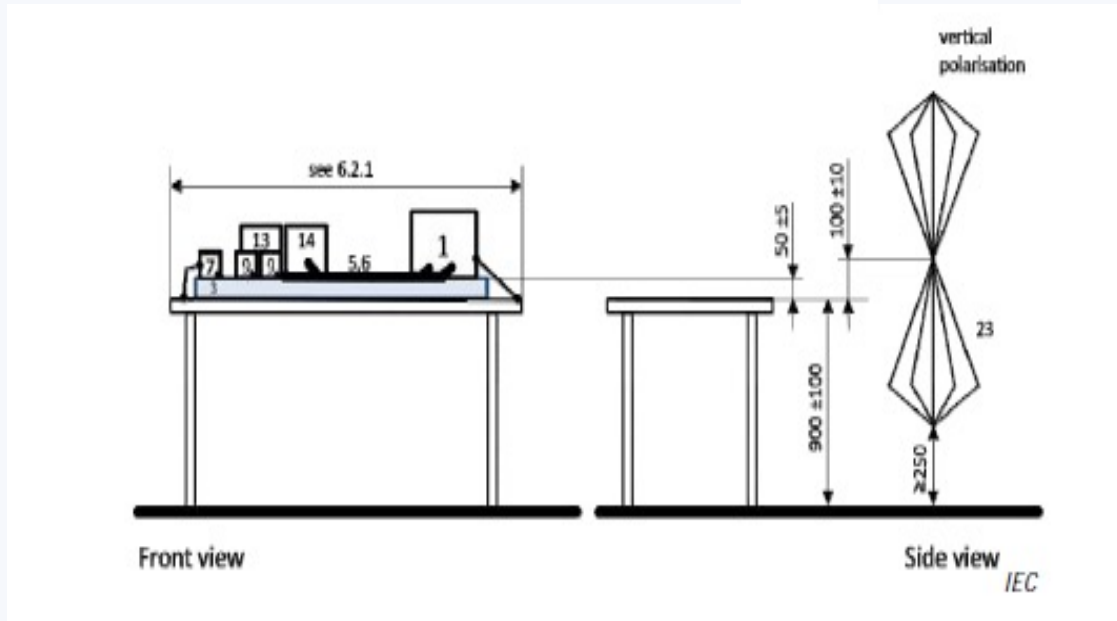
# Chamber EMC Testing: Radiated Emissions



# Radiated Emissions Test Results

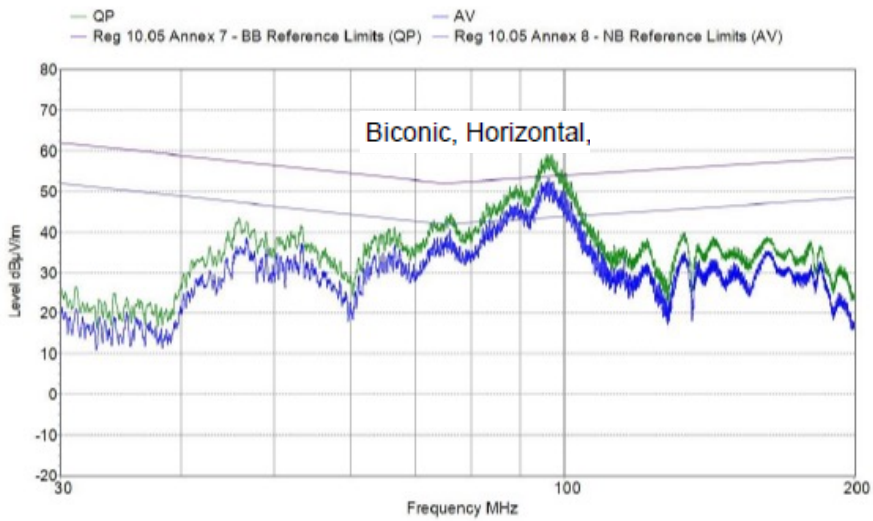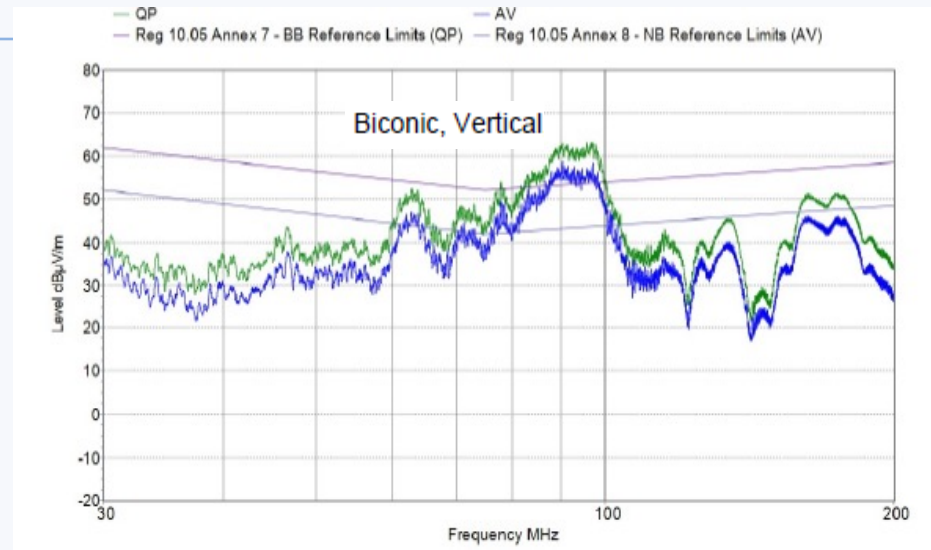

**BEFORE**

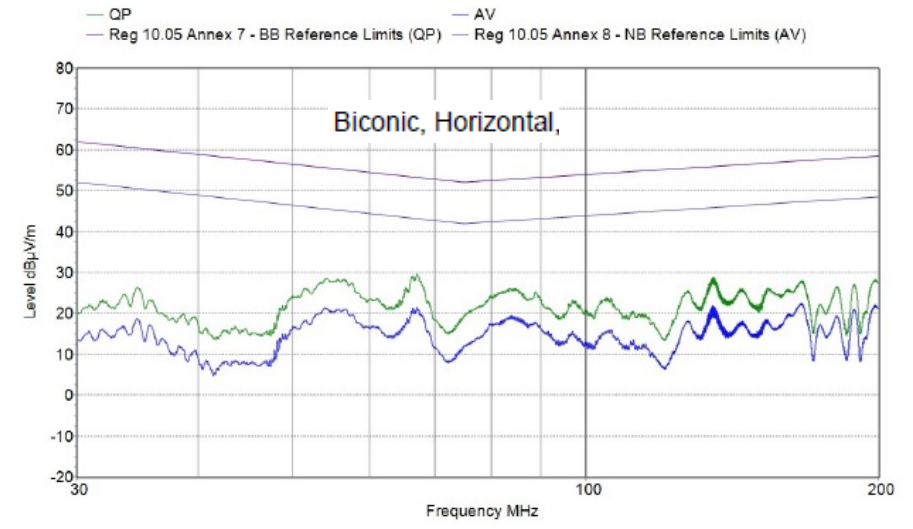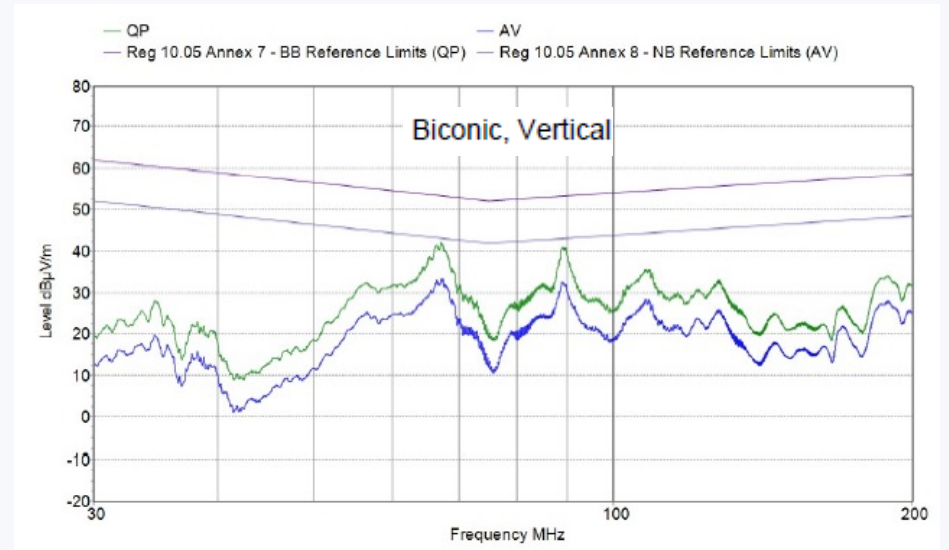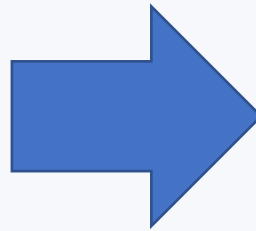

**AFTER**



# Thank you!

---

Any questions?

The logo for EMC & COMPLIANCE INTERNATIONAL features a green rectangular background at the top. Below this, a diagonal line divides the space into three colored sections: a red triangle on the left, a white triangle in the middle, and a blue triangle on the right. The text "EMC & COMPLIANCE INTERNATIONAL" is written in yellow, bold, uppercase letters across the green background.

**EMC &  
COMPLIANCE  
INTERNATIONAL**

<https://www.emcandci.com>

A promotional poster for EMC & CI 2024. The background is dark blue with a faint grid pattern. The text is in yellow and white. It includes the event title, a courtesy message from Min Zhang of Mach One Design Ltd, a 20% OFF discount code (MOD20), the dates (22nd and 23rd May, 2024), the location (Newbury Racecourse, RG14 7NZ, UK), and contact information (www.emcandci.com, info@emcandci.com). There are two logos on the right: the EMC & COMPLIANCE INTERNATIONAL logo and the MACHone logo.

**EMC & CI 2024**

Courtesy of Min Zhang,  
Mach One Design Ltd, visit Stand 7

**20% OFF**

Get 20% off the cost of the Training or Conference by  
using my discount code **MOD20** when registering

22<sup>nd</sup> and 23<sup>rd</sup> May, 2024  
Newbury Racecourse, RG14 7NZ, UK  
[www.emcandci.com](http://www.emcandci.com)  
[info@emcandci.com](mailto:info@emcandci.com)

**MACHone**  
Expertise Propels Excellence

 **LYRA ELECTRONICS**