



Another EMC resource  
from EMC Standards


13+14: Suppressing emissions of mains harmonics,  
voltage fluctuations and flicker

*Helping you solve your EMC problems*


emc14c+gs v2.1 All relevant safety requirements must be applied, but are not necessarily covered in these slides CCC

## Modules 13+14: Suppressing emissions of mains harmonics, voltage fluctuations and flicker

(covers the mains harmonics emitted by rectifier-capacitor AC-DC converters)



**CHERRY  
CLOUGH**  
CONSULTANTS LTD



**emc** STANDARDS

Keith Armstrong CEng, FIET, Senior MIEEE, ACGI, Eurlng(Gp1)  
phone/fax: +44 (0)1785 660 247  
keith.armstrong@cherryclough.com  
www.cherryclough.com www.emcstandards.co.uk

**13+14.0.1** Cherry Clough Consultants confidential training material 1 of 60

emc14c+gs v2.1 All relev CCC

## Good Electromagnetic (EM) Engineering...

- is cost-effective SI, PI and EMC engineering: well-proven to save time & money in all lifecycle stages, helping to increase profits & reduce financial risks...
- for PCBs, modules, sub-assemblies, devices, products, equipment, vehicles, sub-systems, systems, installations, etc., etc.; of any size, in all applications
- see *Module 1 especially 1.15 (also in Webinar 1c) and 1.16 (also in Webinar 1d)*

■ **This** Module contains many EM Engineering guidelines that should *also* be used as an initial design checklist: *any that can't or won't be followed identify a project risk!* see *Module 1, section 1.16 (also in Webinar 1d)*

- to adapt any  $\lambda$ -based design guidelines to different EMC standards, see *Module 1, section 1.18 (also in Webinar 1d)*

Cherry Clough Consultants confidential training material 2 of 60

emc14c+gs v2.1 All relevant safety requirements must be applied, but are not necessarily covered in these slides CCC

# Contents

- 13 Suppressing emissions of mains harmonics**
  - 13.1 The mains harmonic currents emitted by rectifier-capacitor AC-DC power converters**
  - 13.2 Smaller values of storage capacitor, and the “Valley Fill” method**
  - 13.3 Filters**
  - 13.4 DC chokes**
  - 13.5 Charge-pump switch-mode techniques**
  - 13.6 ‘Active’ PFC circuits**
  - 13.7 6-phase rectification**
  - 13.8 Active front end (AFE) rectification**

**13+14.0.2** Cherry Clough Consultants confidential training material 3 of 60

emc14c+gs v2.1 All relevant safety requirements must be applied, but are not necessarily covered in these slides CCC

# Contents continued...

- 14 Suppressing emissions of voltage fluctuations and flicker**
  - 14.1 Load current fluctuations cause the problems**
  - 14.2 Reducing the inrush current**
  - 14.3 Suppressing AC loads**
  - 14.4 Suppressing DC loads**
  - 14.5 Using Active PFC as an active filter**
- 13+14.1 Some useful references**

**13+14.0.3** Cherry Clough Consultants confidential training material 4 of 60

emc14c+gs v2.1 All relevant safety requirements must be applied, but are not necessarily covered in these slides CCC

# 13. Suppressing mains harmonics


## 13.1


### The mains harmonic currents emitted by rectifier-capacitor AC-DC power converters

13.1.1 Cherry Clough Consultants confidential training material 5 of 60


emc14c+gs v2.1 All relevant safety requirements must be applied, but are not necessarily covered in these slides CCC
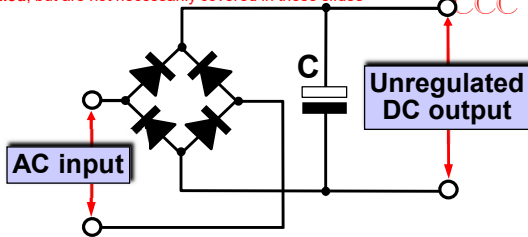
### Harmonic currents emitted by a rectifier-capacitor AC-DC converter




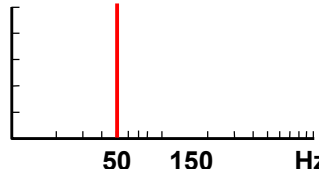


50 150 Hz

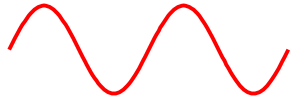

Sinewave supply voltage

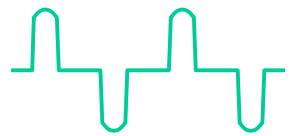

Supply current demand

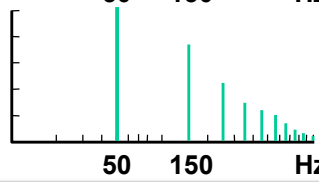

50 150 Hz

**Waveforms: rectifiers only charge the DC capacitor near supply voltage peaks**

**Frequency spectra: the current demand includes harmonics of the supply frequency**

13.1.2 Cherry Clough Consultants confidential training material 6 of 60

emc14c+gs v2.1 All relevant safety requirements must be applied, but are not necessarily covered in these slides CCC

## Power Factor (PF)

- **True PF = Total Watts / Total VA**
  - harmonic currents are not in phase with the supply voltage, so they increase the VA but not the Watts
    - ◆ design to reduce harmonic emissions is often known as Power Factor Correction (PFC)
  - don't get confused with 'Power Factor' as traditionally used by electrical supply engineers
    - ◆ which simply means the cosine of the phase angle between the sine-wave supply voltage and a sine-wave load current
      - only relevant for *linear* loads

13.1.3 Cherry Clough Consultants confidential training material 7 of 60

emc14c+gs v2.1 All relevant safety requirements must be applied, but are not necessarily covered in these slides CCC

# 13. Suppressing mains harmonics

## 13.2

### Smaller values of storage capacitor, and the "Valley Fill" method

13.2.1 Cherry Clough Consultants confidential training material 8 of 60

emc14c+gs v2.1 CCC

## Using smaller values of unregulated DC storage capacitor

- **Smaller values cause the capacitor to discharge more during each mains cycle...**
  - increasing the firing angle (on-time) of the rectifiers and so reduces the harmonic emissions...
    - ◆ but not by a large amount (the capacitor would have to be reduced to zero to achieve power factors approaching 1)...
  - **AND** the following circuit must operate correctly despite the increased ripple on the DC rail
- **This technique has been used in powerful variable-speed (i.e. inverter) AC motor drives**

13.2.2 Cherry Clough Consultants confidential training material 9 of 60

emc14c+gs v2.1 All relevant safety requirements must be applied, but are not necessarily covered in these slides CCC

### Using smaller values of unregulated DC storage capacitor continued...

AC input

Unregulated DC output with increased ripple

Smaller value

C

Supply current demand with large capacitor

Supply current demand with smaller capacitor – lower harmonic emissions


Current waveform

Spectrum of the current

50 150 Hz

50 150 Hz

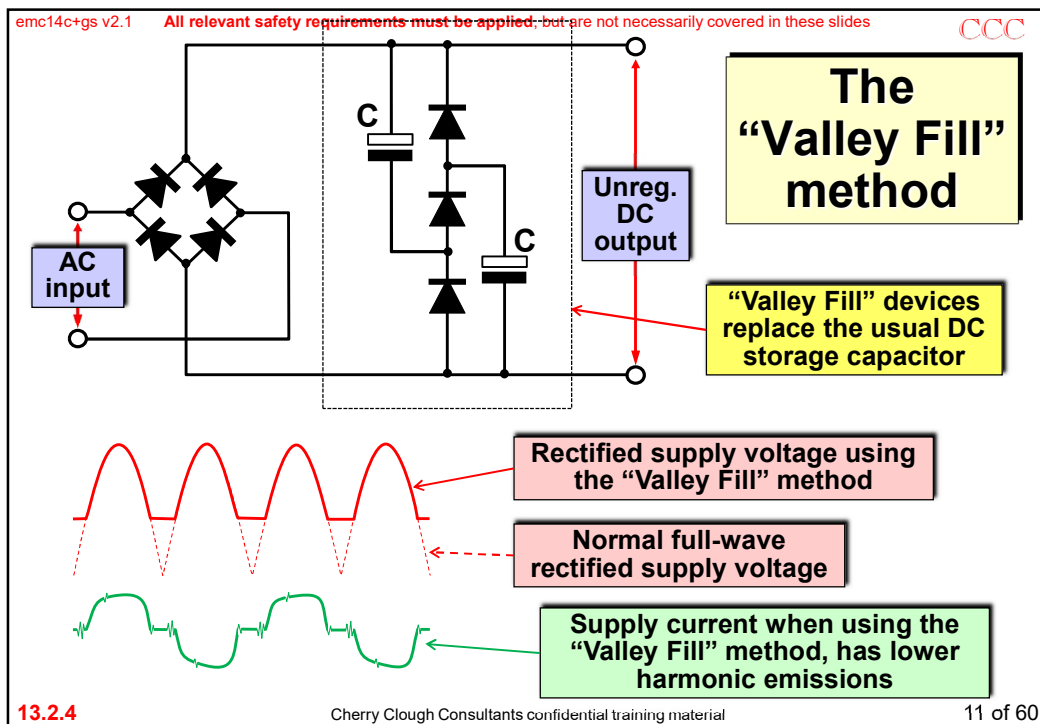13.2.3 Cherry Clough Consultants confidential training material 10 of 60



emc14c+gs v2.1 All relevant safety requirements must be applied, but are not necessarily covered in these slides CCC

**The “Valley Fill” method continued...**

- **Cannot achieve a power factor better than about 0.9**
- **Causes high ripple on the unregulated DC output...**
  - that the following circuit must be able to handle...
  - for example: has been recommended for use with Buck converters when driving low-voltage LED strings from the AC mains supply

13.2.5 Cherry Clough Consultants confidential training material 12 of 60